

Assignment 4: Put it all together.

"Whether you think you can, or you think you can't--you're right." — [Henry Ford](#)

You have come this far, getting the ALU built. Now, let's make a (student version of a) processor. This assignment is based on material in Chapter 5 of P&H 2nd edition. Given the instruction set in Table 1, the necessary components and datapath connecting them are shown in Fig. 5.33 (P&H 2e, reillustrated below). Summary of the steps taken to execute the given instructions is shown in Table 2.

MIPS core instruction	Format	Bits =	m/c code					
			6	5	5	5	5	6
add	add rd, rs, rt		0	rs	rt	rd	0	0x20
subtract	sub rd, rs, rt		0	rs	rt	rd	0	0x22
and	and rd, rs, rt		0	rs	rt	rd	0	0x24
or	or rd, rs, rt		0	rs	rt	rd	0	0x25
set on less than	slt rd, rs, rt		0	rs	rt	rd	0	0x2A
load word	lw rt, addr		0x23	rs	rt	offset		
store word	sw rt, addr		0x2B	rs	rt	offset		
branch on equal	beq rs, rt, label		4	rs	rt	offset		
jump	j target		2	target				

Table 1: an instruction set that we are going to implement a hardware for. Woohoo! sounds fun.

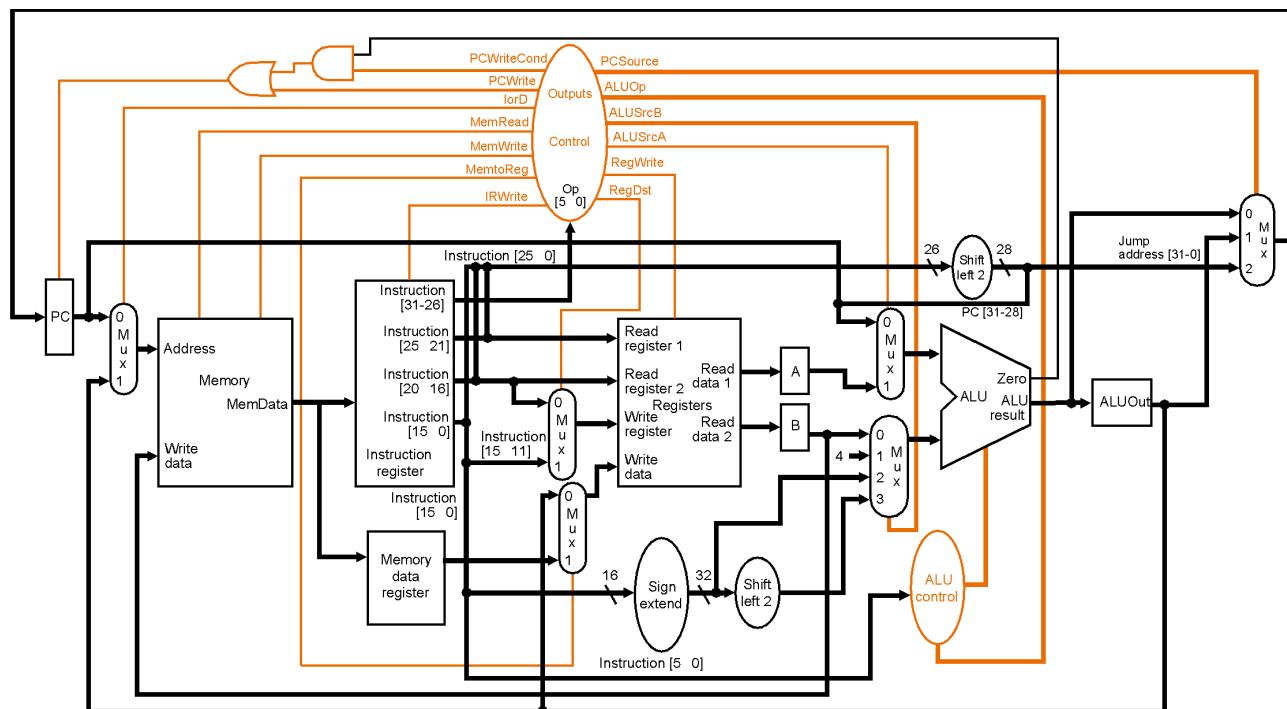


Fig. 5.33 (P&H 2e) The complete datapath for the multicycle implementation of the instruction set shown in Table 1.

Step	Action for R-type instructions	Action for memory-reference instructions		Action for branches	Action for jumps
1	IR <= Memory[PC] PC <= PC + 4 IorD = 0, MemRead, IRWrite ALUSrcA = 0, ALUSrcB = 01, ALUOp = 00, PCSource = 00, PCWrite				
2	A <= Reg[IR[25:21]] B <= Reg[IR[20:16]] ALUOut <= PC + (sign-extend (IR[15:0]) << 2) ALUSrcA = 0, ALUSrcB = 11, ALUOp = 00				
3	ALUOut <= A op B ALUSrcA = 1, ALUSrcB = 00, ALUOp = 10	ALUOut <= A + sign-extend (IR[15:0]) ALUSrcA = 1, ALUSrcB = 10, ALUOp = 00	if (A == B) PC <= ALUOut	if (A == B) PC <= {PC[31:28],(IR[25:0]),2'b00}	
4	Reg[IR[15:11]] <= ALUOut RegDst = 1, MemtoReg = 0, RegWrite	Load: MDR <= Memory[ALUOut]	Store: Memory[ALUOut] <= B		
5		Load: Reg[IR[20:16]] <= MDR RegDst = 0, MemtoReg = 1, RegWrite			

Table 2: Summary of the steps taken to execute any instruction class with corresponding control signals.

Tasks:

1. Study material in Section 5.4 (P&H 2e).

Be true to yourself. Integrity is one of the most important character traits.

2. Examine each component behavior.

Study behavior of each component. See how each component's outputs relate to their inputs. Check out how a state component, e.g. memory, behaves.

a) The word ALU.

Run `WordALU_tb` and verify that the component works correctly.

You should have the waveform look like below:

It is a good practice to verify results by hand, i.e. checking if the arithmetic operations were done correctly: the **result**, **overflow**, and **Zero** signals were as expected regarding to two operands and the operators.

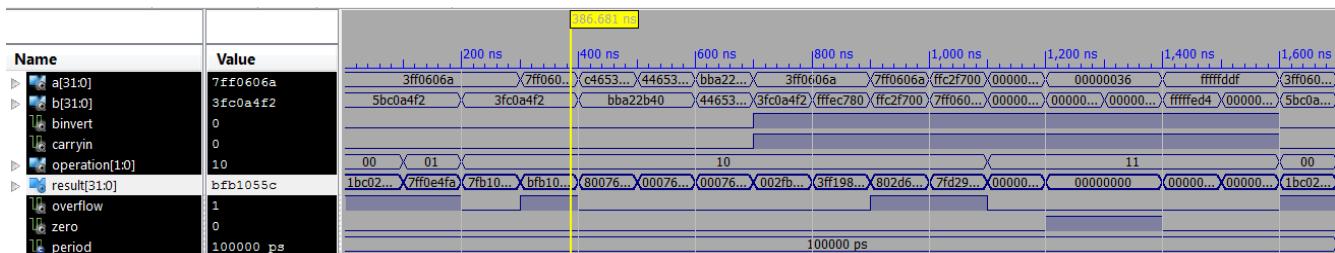


Figure 1: Waveform obtained from WordALU_tb.

(b) The register file.

Run regfile_tb and verify that the component works correctly.


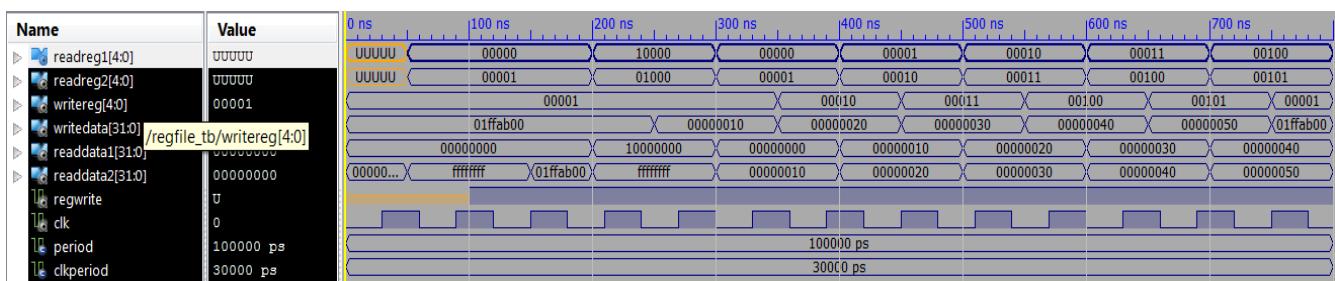


Figure 2: Waveform obtained from regfile_tb.

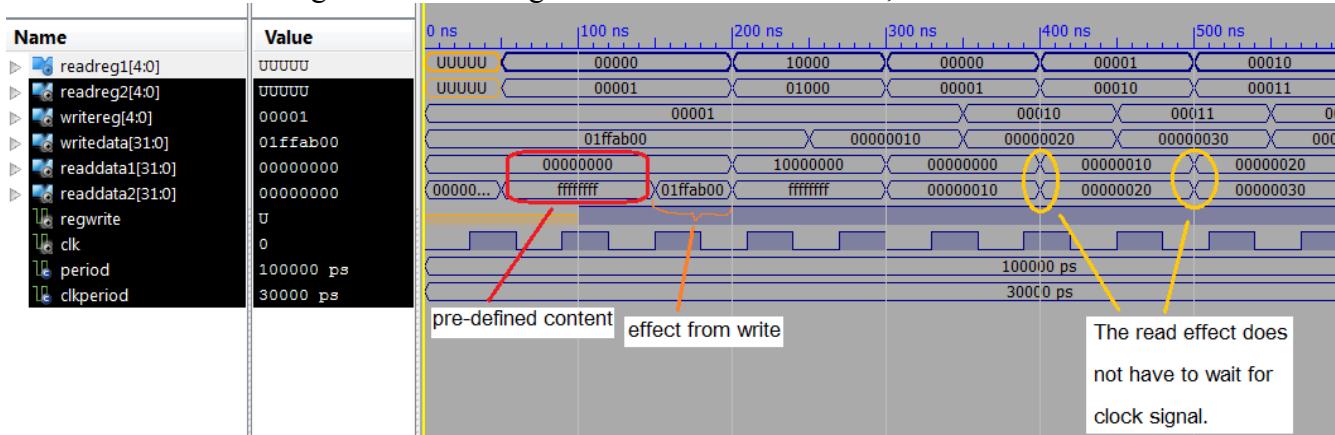It should be noted that the register file has pre-defined content. (See regfile.vhd for details.) The output signals, readdata1 and readdata2, respond immediately when readreg1 or readreg 2 changes, as illustrated in an enlarged version of Figure 2 with additional notes, as shown below.



(c) The one-word registers.

Run nbitregister_tb and verify that the component works correctly.

Asserting reload signal should make the register take in the input value and store until a next change from either a valid load or clear.

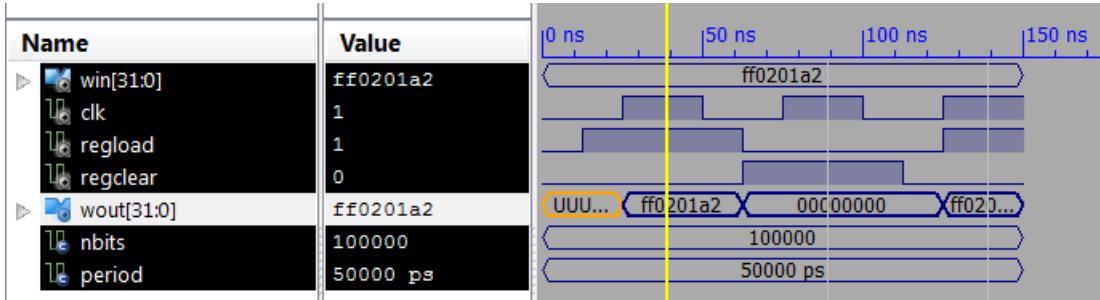


Figure 3: Waveform obtained from nbregister_tb.

(d) The multiplexors.

(d1) The 2-to-1 multiplexor.

Run mux2_tb and verify that the multiplexor works correctly.

The output of the multiplexor should be as the selected input.

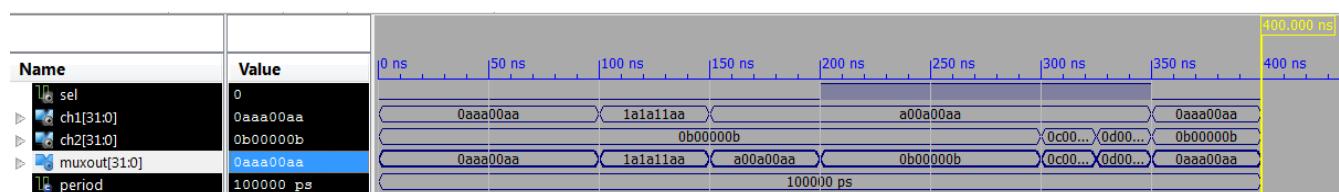


Figure 4: Waveform obtained from mux2_tb.

(d2) The 4-to-1 multiplexor.

Run mux4_tb and verify that the multiplexor works correctly.

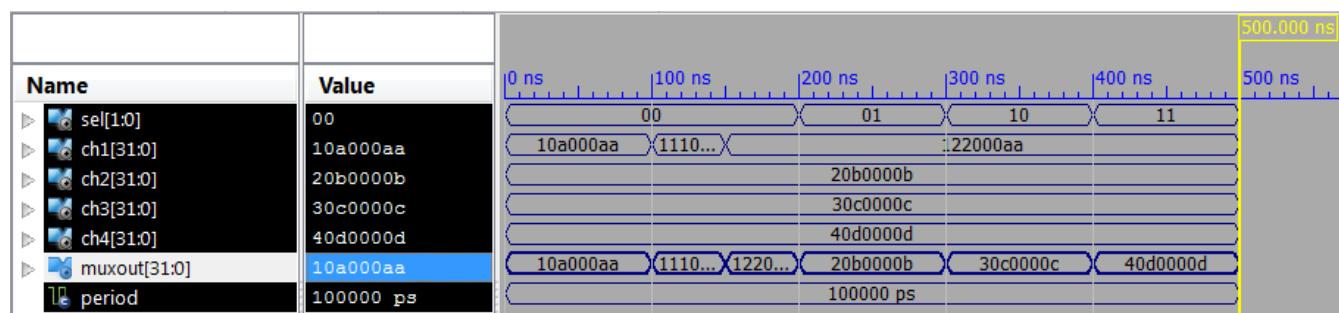


Figure 5: Waveform obtained from mux4_tb.

(e) The sign extension unit.

Run signextend_tb and verify that the component works correctly.

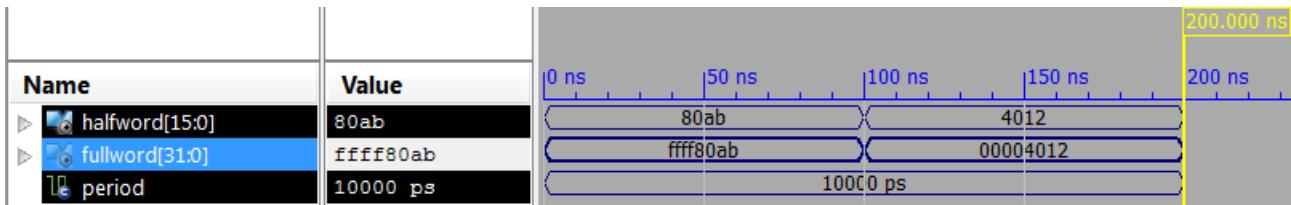


Figure 6: Waveform obtained from signextend_tb.

(f) The memory unit.

Run ch5mem_tb and verify that the component works correctly.

The program segment has written instruction loaded at startup being '1'. At addresses 0x10000000 and 0x10000004, the memory has (some) pre-defined content, which is loaded when the startup signal is '1'. The content can be rewritten with new value specified by data port, as shown during 120 to 160 ns. The effect of re-writing can be seen only when the content is read, as shown in value of q during 170 to 210 ns. Notice that outputs of the memory at addresses 00400000, 00400004, 00400008 and 0040000C contain the machine code of lw \$t0, 0(\$s0), lw \$t1, 4(\$s0), slt \$t2, \$t0, \$t1, and beq \$t2, 3, respectively.

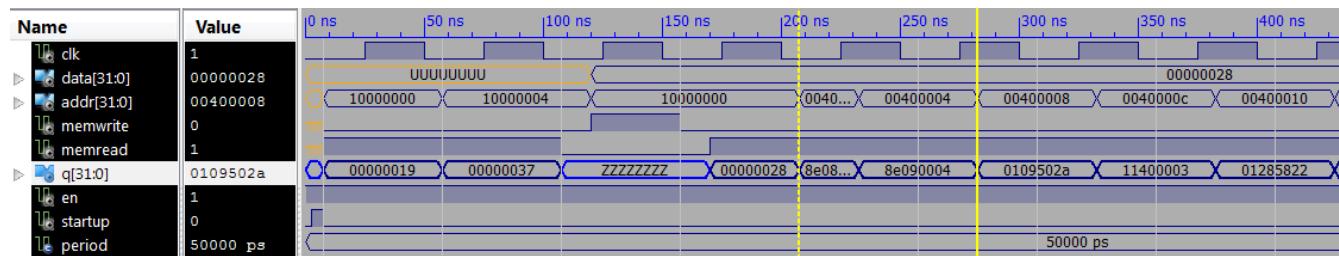


Figure 7: Waveform obtained from ch5mem_tb.

Questions:

* Bonus* f1. In the write mode, is this memory working on a rising or falling clock edge?

* Bonus* f2. How will you design an experiment to support your answer or find to out on which edge the write mode operates?

* Bonus* f3. Write a test bench code to provide waveform supporting your answer.

(g) ALU control unit.

The ALU control unit generates operations, and Binvert signals for the ALU, as well as providing appropriate CarryIn bit, based on ALUop signals and instruction bits from funct field. Instead of having the main control do everything, relegating this control to an ALU control unit leads to a less complicated main control circuit and indirectly improves the efficiency of the main control and the entire processor eventually.

Instruction	m/c code						binary				
	6	5	5	5	5	6	ALUop	funct field	Desired ALU action	ALU control input (Binvert, ALU operation)	Carryin of LSB

lw rt, addr	0x23	rs	rt	offset		00	xx xxxx	add	010	0
sw rt, addr	0x2B	rs	rt	offset		00	xx xxxx	add	010	0
beq rs, rt, label	4	rs	rt	offset		01	xx xxxx	subtract	110	1
add rd, rs, rt	0	rs	rt	rd	0	0x20	10	10 0000	add	010
sub rd, rs, rt	0	rs	rt	rd	0	0x22	10	10 0010	subtract	110
and rd, rs, rt	0	rs	rt	rd	0	0x24	10	10 0100	and	000
or rd, rs, rt	0	rs	rt	rd	0	0x25	10	10 0101	or	001
slt rd, rs, rt	0	rs	rt	rd	0	0x2A	10	10 1010	set on less than	111

Table 3 (Adapted from Fig 5.14 of P&H 2e): How the ALU control bits are set depends on the ALUop control bits and the different function codes for the R-type instruction. A value of "xxxxxx" means that we "don't care" about the value of the function code.

Questions:

g1. What signals are the inputs of the ALU control unit?

g2. What signals are the outputs of the ALU control unit?

g3. Given an instruction in hand is r-type (ALUop = "10"), fill in the logic table below.

ALUop		Funct field						specific instr.	Binvert	ALU operation (2 bits)	CarryIn of LSB
ALUop1	ALUop2	F5	F4	F3	F2	F1	F0				
1	0	1	0	0	0	0	0	add	0	10	0
1	0	1	0	0	0	1	0	subtract	1	10	1
1	0	1	0	0	1	0	0				
1	0	1	0	0	1	0	1				
1	0	1	0	1	0	1	0				

Since the ALUop does not use the encoding 11, either value x1 or 1x would not be ambiguous.

g4. Write boolean expressions for the following variables:

Binvert = _____

ALU operation(1) = _____

ALU operation(0) = _____

CarryIn_LSB = _____

g5. Run ALUControl1_tb and verify that the component works correctly.

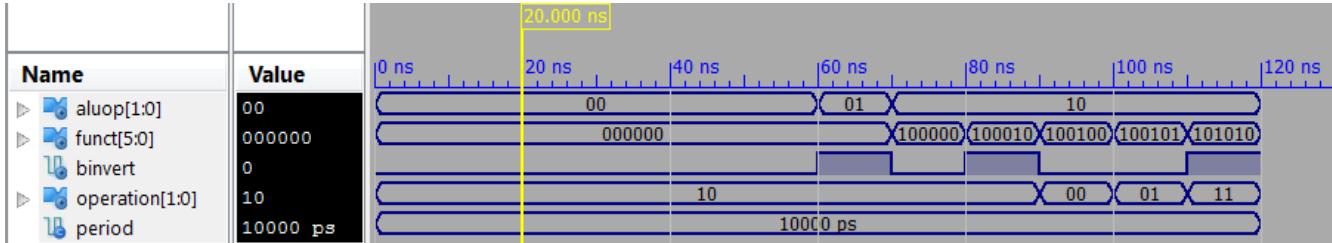


Figure 8: Waveform obtained from ALUControl_tb.

Bonus g6. Propose the alternative architecture of the ALU control to the given architecture (ALUControl process in datapath.vhd).

[Yes, there are alternatives to the given code. For example, you can use the boolean expressions in g4 with a multiplexor to define structural architecture of the ALU.]

Bonus g7. Write VHDL code to implement your proposal and make a test bench to verify its functionality.

Bonus g8. Discuss pros and cons of your proposal comparing to the given architecture.

(h) The main control unit.

Questions:

h1. Given the datapath in Fig. 5.33 (P&H 2e), what signals are the inputs of the main control unit?

h2. Given the datapath in Fig. 5.33 (P&H 2e), what signals are the outputs of the main control unit?

h3. Given the summary of the steps to execute instructions in Table 2, complete the logic table of the main control shown below:

step	instr.	opcode	PCWrite Cond	PCWrite	IorD	Mem Read	Mem Write	Mem toReg	IRWrite	PCSource	ALU Op	ALU SrcB	ALU SrcA	Reg Write	RegDst	
1	all	'xxxxxx	0	1	0	1	0	x	1	'00	'00	'01	0	0	x	
2	all	'xxxxxx	0	0	x	0	0	x	0	'xx	'00	'11	0	0	x	
3	r-type	'000000	0	0	x	0	0	x	0	'xx	'10	'00	1	0	x	
3	lw/sw	'10x011														
3	beq	'000100														
3	j	'000010														
4	r-type	'000000														
4	lw	'100011														
4	sw	'101011														
5	lw	'100011														

'x' (don't care) represents the logic whose value does not affect the processor functionality. All asserting signals are assumed to be active on '1'.

bonus h4. How do we implement keep track of the step shown in the table of question h3? (What component do we need? And, how many bits? Draw a diagram illustrating your idea.)

h5. Run `maincontrol_tb` and verify that the component works correctly.

Check all control signals.

What are signals stagein and stageout for?

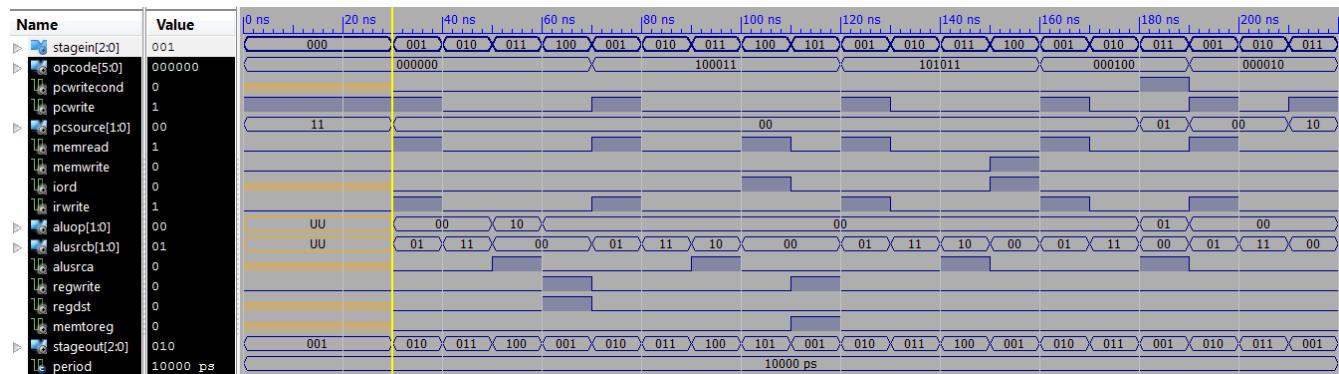


Figure 9: Waveform obtained from `maincontrol_tb`. The waveform here should be conformed to summary of control signals shown in Table 2. Stage 000 is added to add starting-up capability such that the PC will be loaded with 0x00400000 for starting address. The PCSource multiplexor (in Fig. 5.33 P&H 2e) is implemented with a 4-to-1 multiplexor and the starting address 0x00400000 is mounted at "11" position.

bonus h6. Propose the alternative architecture of the main control to the given architecture (MainControl process in `maincontrol.vhd`).

3. Examine how these components work together in each instruction class.

3.1) Examine simulation results of `Ch5path_tb.vhd`.

The signals shown in the waveform viewer reveal data flow and timing of control signals.

A memory preloaded program to calculate an absolute value of difference between two numbers is shown below.

The program is:

```

lw $t0, 0($s0)
lw $t1, 4($s0)
slt $t2, $t0, $t1
beq $t2, $zero, LAB_t1ELTt0
sub $t3, $t1, $t0
j LAB_SAVE
LAB_t1ELTt0: sub $t3, $t0, $t1
LAB_SAVE: sw $t3, 8($s0)
lw $t0, 8($s0) # to check if it is well-saved in memory

```

and it is hard-coded in `ch5mem.vhd` from address 0x00400000, which is the MIPS starting address for instructions.

You are encouraged to familiarize this program with SPIM. (I, myself, use QtSPIM in development of the program.) It should be noted that the different starting address of the program may lead to different machine code, especially the machine code for an instruction with absolute addressing mode, e.g. jump

(j).

The data flow of execution of instructions (1) `lw $t0, 0($s0)`, (2) `slt $t2, $t0, $t1`, (3) `beq $t2, $zero, LAB_t1ELTt0`, (4) `j LAB_SAVE`, and (5) `sw $t3, 8($s0)` are shown in Fig. 10 to 14, respectively. These five instructions are picked from instructions coded for the absolute difference calculation program such that each represents different instruction class.

Questions based on Fig. 5.33 (P&H 2e) and Table 2.

3.1.1) Given the PC content is 0x00400000 at stage 1 of any execution, what is the value at the address port of the memory at stage 1?

3.1.2) According to 3.1.1, what content of the PC will be at the end of stage 2?

3.1.3) Suppose the memory contains data as shown in the table below, after fetch and decode an instruction of the address 0x00400000, what value does the Instruction Register (IR) contain?

Address	Data
0x00400000	0x00
0x00400001	0x00
0x00400002	0x08
0x00400003	0x8e
:	:

3.1.4) According to 3.1.3, if the content of the IR is a valid MIPS instruction, what instruction is it?

! recommended bonus ! 3.1.5) Suppose we are to change the functionality of lw/sw instruction so that the offset field refers to a word, not a byte. This will free us from a tedious task of multiplying an index by 4, every time we want to go by word. It sounds good, right? How will you do it?

To have it more fun, you are allowed to change only the datapath, but leave all control signals untouched. No new component is allowed.

(You are pretty much left with options of re-routing signal or signals.)

What would you do?

[Hint: the answer may be much simpler than you think. Now you are forced to think about datapath.]

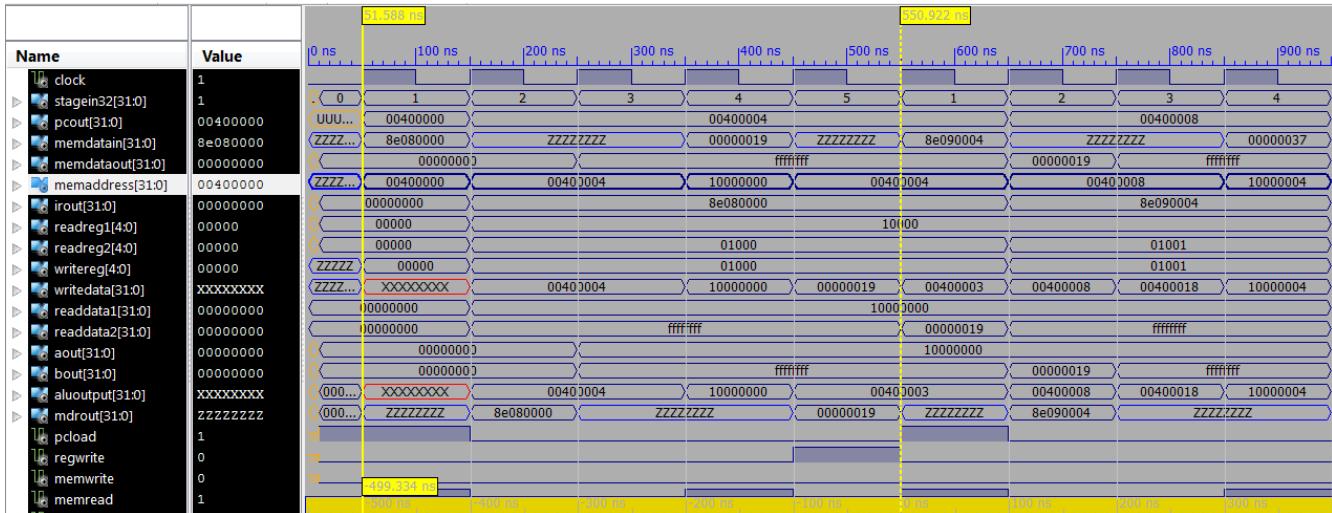


Figure 10: Waveform obtained from Ch5path_tb.vhd showing signal dynamic of the lw instruction. The second signal from top is **stagein32** indicating which stage the execution is going on. The **pcout** indicates the current value of the PC. The **memdatain**, **memdataout**, and **memaddress** indicate data obtained from the memory, data candidate to put in the memory, and the memory address, respectively. The **iorout** indicates the current value of the instruction register (IR). The **readreg1**, **readreg2**, **writereg**, **writedata**, **readdata1**, and **readdata2** are index and data ports of the register file. The **aout**, **bout**, and **aluoutput** indicate current values of registers A, B, and ALUOut respectively. The **mdroutr** indicates the current content of register MDR. The **pcload** is a signal enabling overwrite of PC content. [VHDL: **pcload** <= PCWrite or (PCWriteCond and Zero).] The **regwrite**, **memwrite**, and **memread** are signals controlling writing a content of the register file, writing a content of the memory, and reading a content of the memory, respectively. It should be noted that there are more control signals that are not shown here.

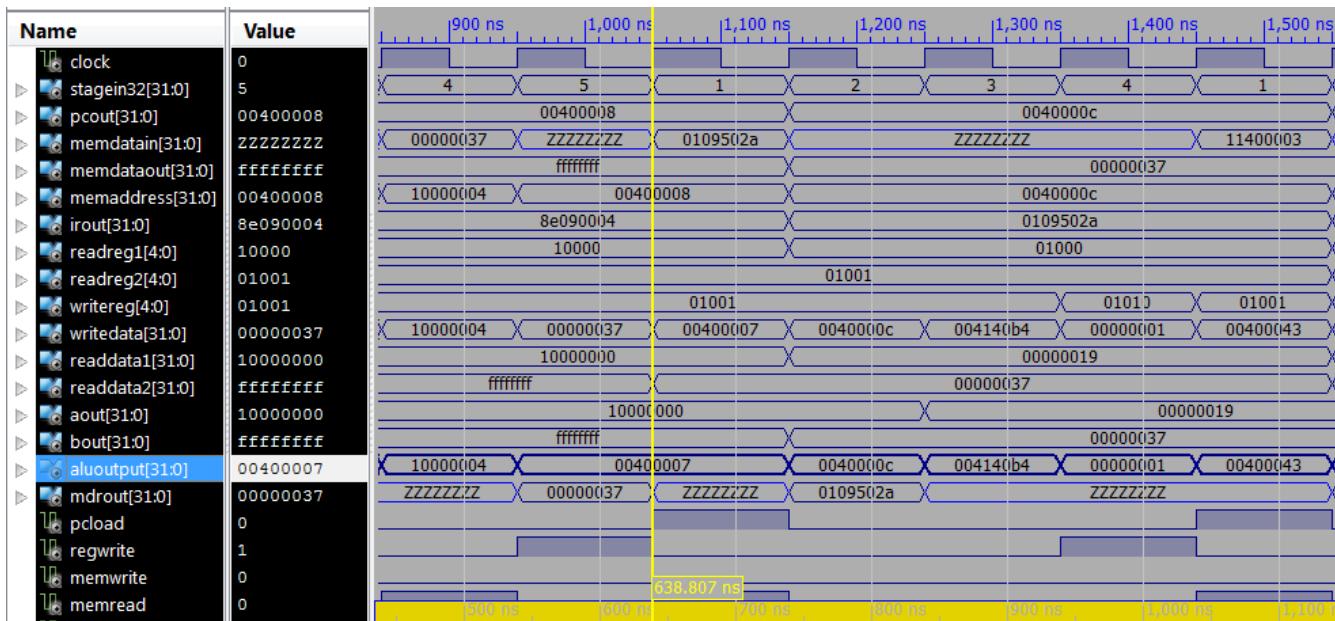


Figure 11: Data flow of the execution of slt instruction. The yellow line marks the beginning of the execution. In stage 1, instruction is fetched from the memory. The value is at **memdatain**. After stage 1, PC and IR values are updated. In stage 2, values of registers referred by decoded instruction are ready. See **readdata1** and **readdata2**. The contents of registers A and B (**aout** and **bout**) are ready for use in stage 3. The content of ALUOut (**aluoutput**) is ready for stage 4 and the **writedata** port of the register file is set to 0x00000001 in the stage 4 of the execution. An R-type instruction such as slt requires 4 stages to complete the execution.


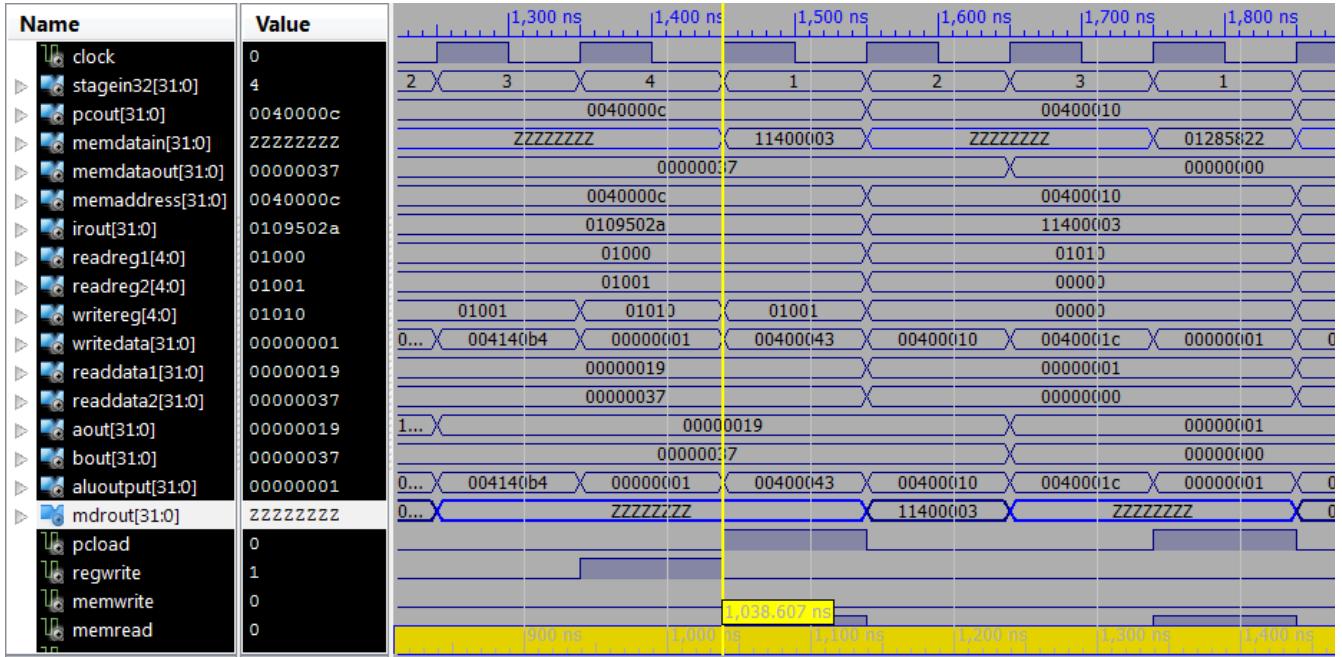


Figure 12: Data flow of the execution of beq instruction. The branch address calculated in stage 2 (0x0040001C) is ready in ALUOut for stage 3. The two values being compared, 0x00000001 and 0x00000000, are loaded into registers A and B whose contents are ready after stage 2. The compared values are not equal, so the branch is not taken and PC keeps its address.

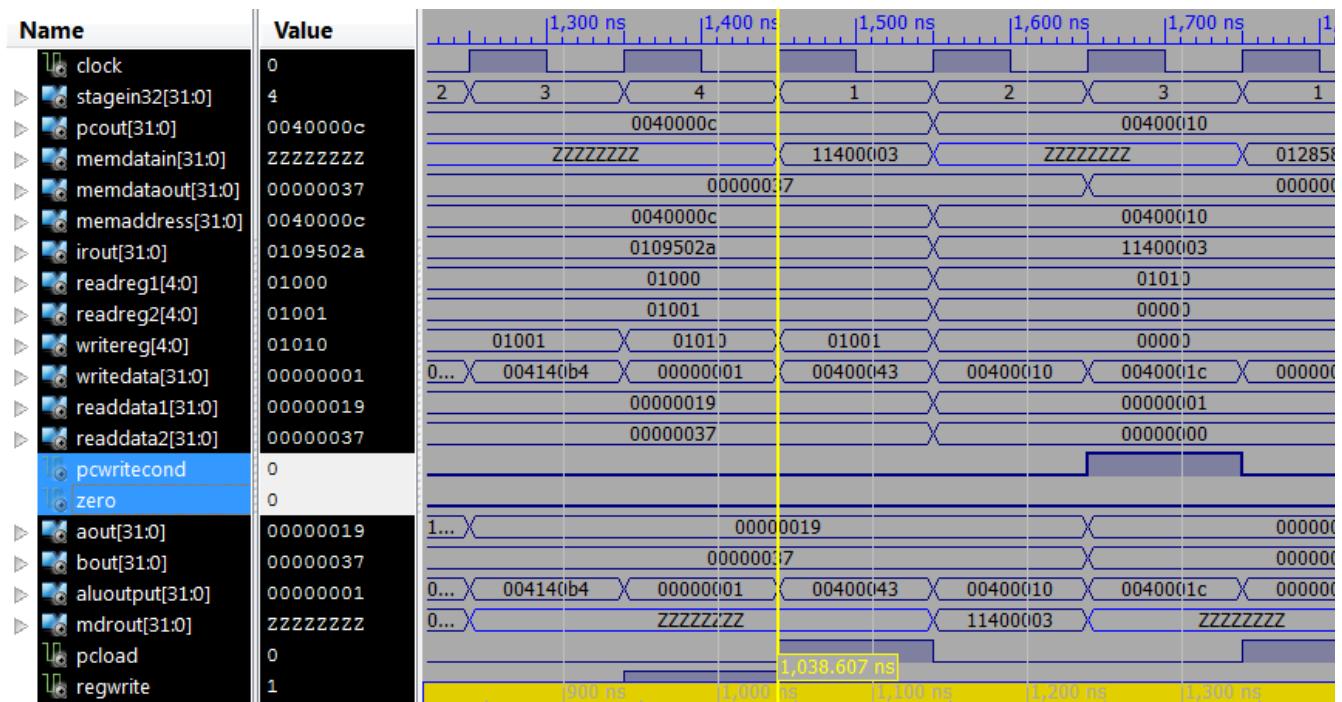

Supplement 1: Moving **pcwritecond** and **zero** signals upto the viewable area showing **pcwritecond** is asserted at stage 3 allowing change address of the PC if **zero** is '1'.

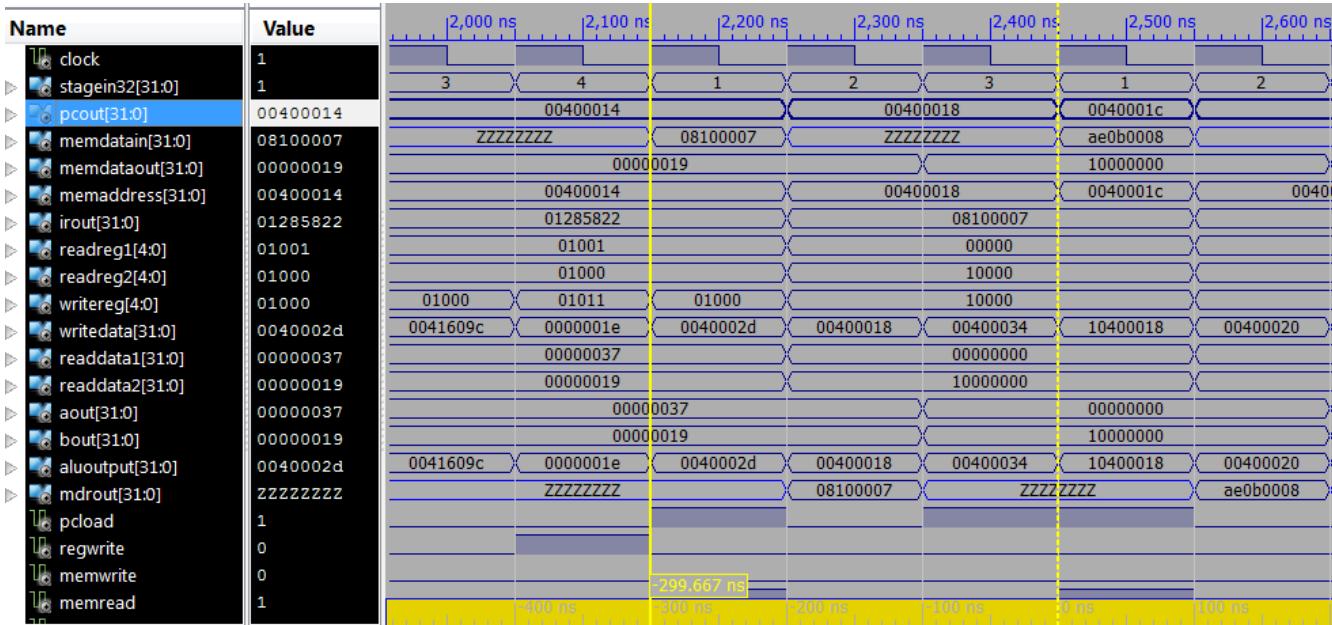


Figure 13: Data flow of the execution of *j* instruction. In stage 3, *pcload* is '1', because PCWrite, not shown here, is '1'. The PC is updated after the end of stage 3 and having its new address ready for the next execution, as seen by that 0x0040001C is a content of PC at stage 1 of the following instruction.

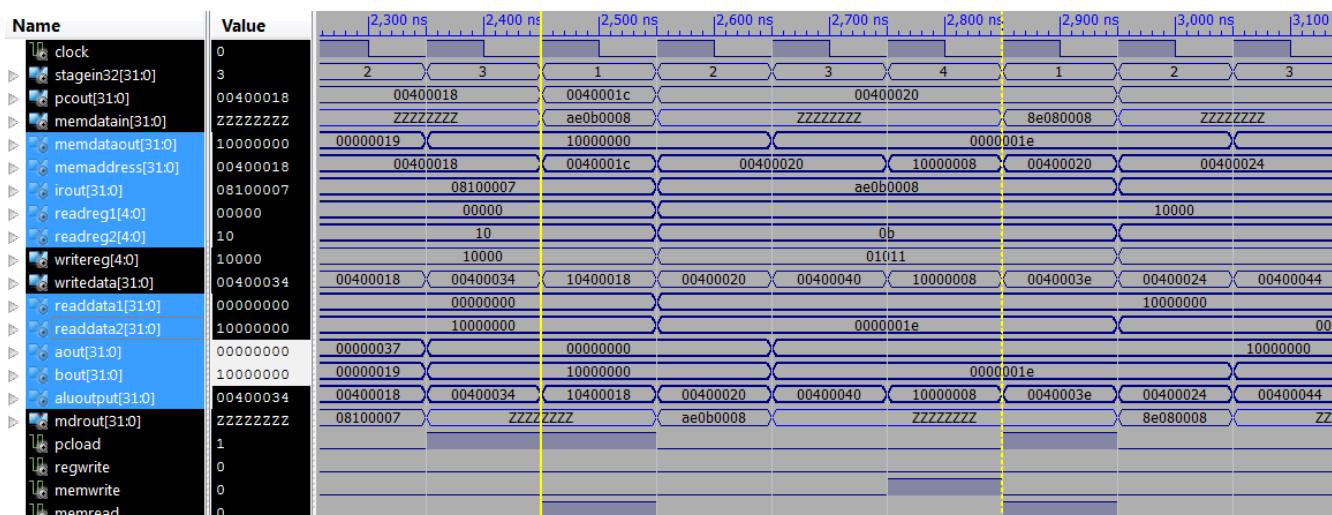


Figure 14: Data flow of the execution of *sw* instruction. After stage 2, values of registers A and B, indicated by *aout* and *bout* are 0x10000000 (the base address) and 0x0000001E (the value to be stored). The value of register B is connected to write data port of the memory (*memdataout*). After stage 3, ALUOut (*aluoutput*) is updated and its value is the target address. In stage 4, the address port of the memory is rerouted to the ALUOut and the *memwrite* signal is asserted to write the data into the memory.

3.2) Your task is to change contents of the memory at addresses 0x10000000 and 0x10000004 to be 0xFFFFFFF19 and 0xFFFFFFF37.

Questions

(3.2.1) What are the decimal values of 0xFFFFF19 and 0xFFFFF37, if they are in 2's complement format?

(3.2.2) With this change, will the branch be taken when we run the same program? Why? (or, if you think the branch will not be taken, why not?)

(3.2.3) With this data, what will be the value to be stored at the address 0x10000008?

(3.2.4) Run the simulation, report the result, and explain what is going on in each stage of the execution of the branch instruction.

(d1) How can you find the branch instruction in a long simulated waveform?

(d2) By looking at the waveform, how can you tell whether the branch is taken or not?

***Bonus* Extend what was given. It's your turn, Little engineer.**

B.1 What aspect of the given implementation do you want to improve? Why and how?
Propose your idea. You don't need to do the VHDL code.

B.2 Now, choose your contribution you like to work on this processor project. Code it in VHDL and make a test bench and verify that it functions as expected.

Hint: there are many things you can do, such as adding capacity to handle other instructions. This does not have to be implementation of your answer to B.1.

B.3 The function of the memory data register.

(a) What is the function of the memory data register (MDR)?

(b) Instead of sticking to the datapath in Fig. 5.33 (P&H 2e) and the control signals as shown in Table 2, what would happen if we bypass the MDR?

This is to connect the MemData directly to the multiplexor controlled with MemtoReg signal.

What are the pros and cons of doing this?

(c) Design experiments to support your answer in 2.2b.

(d) Run your designed experiments, present results, and provide conclusions.

"It's not about what happened in the past, or what you think might happen in the future. It's about the ride, for Christ's sake. There is no point in going through all this crap, if your are not going to enjoy the ride. And you know what... when you least expect something great might come along. Something better then you even planned for." - Irving Feffer, from Along Came Polly (2004).

== Want more? Try these out. ==

* <http://www.xilinx.com/itp/xilinx4/data/docs/xst/hlcode.html>

Closing note

It is a good practice to test every newly created component, so that any flaw in design will be spotted earlier in the development cycle. It's also easier to pin point an error in a single component than trouble shooting unexpected results of an entire system.

Appendix: VHDL codes

ch5path_tb

```
-- Company:      comp. engr. KKU.
-- Engineer:     TK
--
-- Create Date:   17:22:42 09/05/2011
--
-- Module Name:  ch5path_tb - Behavioral
-----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ch5path_tb is
end ch5path_tb;

architecture Behavioral of ch5path_tb is

-- output of datapath --
signal      clock           : std_logic;
signal      memdatain       : std_logic_vector(31 downto 0);
signal      memdataout      : std_logic_vector(31 downto 0);
signal      memaddress      : std_logic_vector(31 downto 0);
signal      memwrite        : std_logic;
signal      memread         : std_logic;
signal      startup         : std_logic;                                -- to
load a start-up setting
-----
-- test bench component --
component ch5mem is
port
(
    clock           : in std_logic;
    datain          : in std_logic_vector(31 downto 0);
    memaddress      : in std_logic_vector(31 downto 0);
    memwrite        : in std_logic;
    memread         : in std_logic;
    dataout         : out std_logic_vector(31 downto 0);
    enable          : in std_logic;
    startup         : in std_logic -- to load pre-written data
);
end component;
-- original components --
component WordALU is
    Port ( a, b : in std_logic_vector (31 downto 0);
           Binvert, CarryIn : in std_logic;
           Operation : in std_logic_vector (1 downto 0);
           Result : out std_logic_vector (31 downto 0);
           Overflow, Zero : out std_logic);
end component;
component mux2 is
port(
    sel:           in std_logic;
    ch1:           in std_logic_vector(31 downto 0);
    ch2:           in std_logic_vector(31 downto 0);
    muxout:        out std_logic_vector (31 downto 0)
);
end component;
```

```

component mux4 is
port(
    sel:          in std_logic_vector(1 downto 0);
    ch1:          in std_logic_vector(31 downto 0);
    ch2:          in std_logic_vector(31 downto 0);
    ch3:          in std_logic_vector(31 downto 0);
    ch4:          in std_logic_vector(31 downto 0);
    muxout: out std_logic_vector (31 downto 0)
);
end component;

component nbitregister is
    generic (n : integer := 32);
    Port (
        win:          in std_logic_vector (31 downto 0);
        clock:        in std_logic;
        regload:      in std_logic;
        regclear:     in std_logic;
        wout:         out std_logic_vector (31 downto 0)
);
end component;

component regfile is
port(
    readreg1:      in std_logic_vector (4 downto 0);      -- index referring to a specific
register
    readreg2:      in std_logic_vector (4 downto 0);      -- index referring to a specific
register
    writereg:     in std_logic_vector (4 downto 0);      -- index referring to a specific
register
    writedata:    in std_logic_vector (31 downto 0);      -- data to put in the specified
register's content
    readdata1:    out std_logic_vector (31 downto 0);      -- data contained in register indexed by
readreg1
    readdata2:    out std_logic_vector (31 downto 0);      -- data contained in register indexed by
readreg2
    RegWrite:     in std_logic;
    clock:        in std_logic
);
end component;

component signextend
port(
    halfword : in std_logic_vector(15 downto 0);
    fullword : out std_logic_vector(31 downto 0)
);
end component;

COMPONENT maincontrol
PORT(
    PCWriteCond : OUT std_logic;
    PCWrite      : OUT std_logic;
    PCSource     : OUT std_logic_vector(1 downto 0);
    MemRead      : OUT std_logic;
    MemWrite     : OUT std_logic;
    IorD         : OUT std_logic;
    IRWrite      : OUT std_logic;
    ALUOp        : OUT std_logic_vector(1 downto 0);
    ALUSrcB      : OUT std_logic_vector(1 downto 0);
    ALUSrcA      : OUT std_logic;
    RegWrite     : OUT std_logic;
    RegDst       : OUT std_logic;
    MemtoReg    : OUT std_logic;
    stagein     : IN std_logic_vector(2 downto 0);
    opcode       : IN std_logic_vector(5 downto 0);
    stageout     : OUT std_logic_vector(2 downto 0)
);
END COMPONENT;

```

```

component ALUControl
  port(
    ALUOp      : in  std_logic_vector(1 downto 0);
    funct      : in  std_logic_vector(5 downto 0);
    Binvert     : out std_logic;
    Operation   : out std_logic_vector(1 downto 0)
  );
end component;

-----
-- signals --
-----

signal clk      : std_logic;

-- register file --
signal readreg1 : std_logic_vector (4 downto 0);
signal readreg2 : std_logic_vector (4 downto 0);
signal writereg : std_logic_vector (4 downto 0);           -- we use only 4 bits, but this would allow it for being
used with a 32-bit mux.
signal writedata: std_logic_vector (31 downto 0);
signal readdata1: std_logic_vector (31 downto 0);
signal readdata2: std_logic_vector (31 downto 0);

-- alu --
signal a, b          : std_logic_vector (31 downto 0);
signal Binvert, CarryIn : std_logic;
signal Operation      : std_logic_vector (1 downto 0);
signal Result         : std_logic_vector (31 downto 0);
signal Overflow, Zero : std_logic;

-- registers --
signal PCin           : std_logic_vector (31 downto 0);
signal PCload          : std_logic;
signal PCout, I Rout, MDRout, Aout, Bout, ALUoutput       : std_logic_vector (31 downto 0);

-- main control signals --
signal RegWrite : std_logic;
signal IRWrite    : std_logic;
signal ALUSrcB   : std_logic_vector (1 downto 0);
signal PCSource  : std_logic_vector (1 downto 0);
signal IorD, RegDst, MemtoReg, ALUSrcA : std_logic;
signal ALUOp      : std_logic_vector (1 downto 0);
signal PCWriteCond : std_logic;

-- pathway signals --

signal SignEx        : std_logic_vector (31 downto 0);

signal adapterMX0     : std_logic_vector (31 downto 0);
signal adapterMX1     : std_logic_vector (31 downto 0);
signal adapterMXout    : std_logic_vector (31 downto 0);

signal jaddr          : std_logic_vector (31 downto 0);
signal beqoffset: std_logic_vector (31 downto 0);

signal PCSourceOut    : std_logic_vector (31 downto 0);

signal stagein32, stageout32 : std_logic_vector (31 downto 0);

-- simulation variables --
-- Clock period definitions
constant clock_period : time := 100 ns;

begin

```

```

clk <= clock;

regs: regfile
port map (
    readreg1      => readreg1,
    readreg2      => readreg2,
    writereg      => writereg,
    writedata     => writedata,
    readdata1     => readdata1,
    readdata2     => readdata2,
    RegWrite      => RegWrite,
    clock         => clk);

alu: WordALU
port map (
    a => a,
    b => b,
    Binvert => Binvert,
    CarryIn => CarryIn,
    Operation => Operation,
    Result => Result,
    Overflow => Overflow,
    Zero => Zero);

PC: nbitregister
port map (
    win => PCin,
    clock => clk,
    regload => PCload,
    regclear => '0',
    wout => PCout);

IR: nbitregister
port map (
    win => memdatain,
    clock => clk,
    regload => IRWrite,
    regclear => startup,
    wout => IROUT);

MDR: nbitregister
port map (
    win => memdatain,
    clock => clk,
    regload => '1',
    regclear => startup,
    wout => MDRout);

Areg: nbitregister
port map (
    win => readdata1,
    clock => clk,
    regload => '1',
    regclear => startup,
    wout => Aout);

Breg: nbitregister
port map (
    win => readdata2,
    clock => clk,
    regload => '1',
    regclear => startup,
    wout => Bout);

ALUout: nbitregister
port map (
    win => Result,
    clock => clk,
    regload => '1',

```

```

    regclear => startup,
    wout => ALUoutput);

mxsrcB: mux4
port map (
    sel      => ALUSrcB,
    ch1      => Bout,
    ch2      => x"00000004",
    ch3      => SignEx,
    ch4      => beqoffset,
    muxout  => b);

beqoffset <= SignEx(29 downto 0) & "00";

mxsrcPC: mux4
port map (
    sel      => PCSource,
    ch1      => Result,
                -- PC <= PC + 4
    ch2      => ALUoutput,
                -- beq
    ch3      => jaddr,
                -- j
    ch4      => x"00400000",
                -- boot up address
    muxout  => PCSourceOut);

jaddr <= PCOut(31 downto 28) & I Rout(25 downto 0) & "00";

mxIorD: mux2
port map (
    sel      => IorD,
    ch1      => PCout,           -- instruction access
    ch2      => ALUOutput,       -- memory access (lw/sw)
    muxout  => memaddress);

mxRegDst: mux2
port map (
    sel      => RegDst,
    ch1      => adapterMX0,   -- lw
    ch2      => adapterMX1,   -- R-type
    muxout  => adapterMXout);

adapterMX0 <= "00000000000000000000000000000000" & I Rout(20 downto 16);
adapterMX1 <= "00000000000000000000000000000000" & I Rout(15 downto 11);
writereg <= adapterMXout(4 downto 0);

mxMemtoReg: mux2
port map (
    sel      => MemtoReg,
    ch1      => ALUOutput,     -- R-type
    ch2      => MDRout,        -- lw
    muxout  => writedata);

mxsrcA: mux2
port map (
    sel      => ALUSrcA,
    ch1      => PCout,         -- PC increment / branch address
    ch2      => Aout,          -- R-type, lw, sw
    muxout  => a);

PCin <= PCSourceOut;

SE: signextend
port map (
    halfword => I Rout(15 downto 0),
    fullword => SignEx);

```

```

alucon: ALUControl
port map (
    ALUOp => ALUOp,
    funct => I Rout(5 downto 0),
    Binvert => Binvert,
    Operation => Operation);

    CarryIn <= Binvert;      -- Both Binvert and CarryIn indicate subtraction (of sub, slt, and comparing for
beq) when set.          -- Both are reset for other operations.

maincon: maincontrol
port map (
    PCWriteCond => PCWriteCond,
    PCWrite => PCWrite,
    PCSource => PCSource,
    MemRead => MemRead,
    MemWrite => MemWrite,
    IorD => IorD,
    IRWrite => IRWrite,
    ALUop => ALUop,
    ALUSrcB => ALUSrcB,
    ALUSrcA => ALUSrcA,
    RegWrite => RegWrite,
    RegDst => RegDst,
    MemtoReg => MemtoReg,
    stagein => stagein32(2 downto 0),
    opcode => I Rout(31 downto 26),
    stageout => stageout32(2 downto 0));

stageout32(31 downto 3) <= "00000000000000000000000000000000";

statereg: nbitregister
port map (
    win => stageout32,
    clock => clk,
    regload => '1',
    regclear => startup,
    wout => stagein32);

-- nodes --
memdataout <= Bout;

readreg1 <= I Rout(25 downto 21);
readreg2 <= I Rout(20 downto 16);

PCload <= PCWrite or (PCWriteCond and Zero);

-- Simulation part --

mem: ch5mem
port map (
    clock      => clock,
    datain     => memdataout,
    memaddress => memaddress,
    memwrite   => memwrite,
    memread   => memread,
    dataout     => memdatain,
    enable     => '1',
    startup    => startup);

-- Clock process definitions
clock_process :process
begin
    clock <= '0';
    wait for clock_period/2;
    clock <= '1';
    wait for clock_period/2;

```

```

end process;

-- Stimulus process
stim_proc: process
begin
    startup <= '0';
    wait for clock_period/10;

    startup <= '1';
    wait for clock_period/10;

    startup <= '0';
    wait;
end process;

-- simulation time = 4000 ns
end Behavioral;

```

ALUControl_tb

```

-----
-- Company:
-- Engineer:
--
-- Create Date: 08:59:04 09/06/2011
-- Design Name:
-- Module Name: C:/xilinx_tutorial/Ch05/ALUControl_tb.vhd
-- Project Name: Ch05
-- Target Device:
-- Tool versions:
-- Description:
--
-- VHDL Test Bench Created by ISE for module: ALUControl
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-- Notes:
-- This testbench has been automatically generated using types std_logic and
-- std_logic_vector for the ports of the unit under test. Xilinx recommends
-- that these types always be used for the top-level I/O of a design in order
-- to guarantee that the testbench will bind correctly to the post-implementation
-- simulation model.
-----
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
-- USE ieee.numeric_std.ALL;

ENTITY ALUControl_tb IS
END ALUControl_tb;

ARCHITECTURE behavior OF ALUControl_tb IS
    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT ALUControl
    PORT(
        ALUOp : IN  std_logic_vector(1 downto 0);
        funct : IN  std_logic_vector(5 downto 0);
        Binvert : OUT std_logic;
    
```

```

        Operation : OUT  std_logic_vector(1 downto 0)
    );
END COMPONENT;

--Inputs
signal ALUOp : std_logic_vector(1 downto 0) := (others => '0');
signal funct : std_logic_vector(5 downto 0) := (others => '0');

--Outputs
signal Binvert : std_logic;
signal Operation : std_logic_vector(1 downto 0);
-- No clocks detected in port list. Replace <clock> below with
-- appropriate port name

constant period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: ALUControl PORT MAP (
        ALUOp => ALUOp,
        funct => funct,
        Binvert => Binvert,
        Operation => Operation
    );

    -- Stimulus process
    stim_proc: process
    begin
        -- hold reset state for 50 ns.
        wait for 50 ns;

        -- lw/sw: add --
        ALUOp <= "00";
        wait for period;

        -- beq: sub --
        ALUOp <= "01";
        wait for period;

        -- R-type --
        ALUOp <= "10";           funct <= "100000";
        wait for period;

        ALUOp <= "10";           funct <= "100010";
        wait for period;

        ALUOp <= "10";           funct <= "100100";
        wait for period;

        ALUOp <= "10";           funct <= "100101";
        wait for period;

        ALUOp <= "10";           funct <= "101010";
        wait for period;

        wait;
    end process;
END;

```

maincontrol_tb

```
-- Company:
-- Engineer:
```

```

-- Create Date: 08:08:24 09/06/2011
-- Design Name:
-- Module Name: C:/xilinx_tutorial/Ch05/maincontrol_tb.vhd
-- Project Name: Ch05
-- Target Device:
-- Tool versions:
-- Description:
--
-- VHDL Test Bench Created by ISE for module: maincontrol
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-- Notes:
-- This testbench has been automatically generated using types std_logic and
-- std_logic_vector for the ports of the unit under test. Xilinx recommends
-- that these types always be used for the top-level I/O of a design in order
-- to guarantee that the testbench will bind correctly to the post-implementation
-- simulation model.
-----
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

ENTITY maincontrol_tb IS
END maincontrol_tb;

ARCHITECTURE behavior OF maincontrol_tb IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT maincontrol
        PORT(
            PCWriteCond : OUT std_logic;
            PCWrite : OUT std_logic;
            PCSrc : OUT std_logic_vector(1 downto 0);
            MemRead : OUT std_logic;
            MemWrite : OUT std_logic;
            IorD : OUT std_logic;
            IRWrite : OUT std_logic;
            ALUOp : OUT std_logic_vector(1 downto 0);
            ALUSrcB : OUT std_logic_vector(1 downto 0);
            ALUSrcA : OUT std_logic;
            RegWrite : OUT std_logic;
            RegDst : OUT std_logic;
            MemtoReg : OUT std_logic;
            stagein : IN std_logic_vector(2 downto 0);
            opcode : IN std_logic_vector(5 downto 0);
            stageout : OUT std_logic_vector(2 downto 0)
        );
    END COMPONENT;

    --Inputs
    signal stagein : std_logic_vector(2 downto 0) := (others => '0');
    signal opcode : std_logic_vector(5 downto 0) := (others => '0');

    --Outputs
    signal PCWriteCond : std_logic;
    signal PCWrite : std_logic;
    signal PCSrc : std_logic_vector(1 downto 0);
    signal MemRead : std_logic;

```

```

signal MemWrite : std_logic;
signal IorD : std_logic;
signal IRWrite : std_logic;
signal ALUop : std_logic_vector(1 downto 0);
signal ALUSrcB : std_logic_vector(1 downto 0);
signal ALUSrcA : std_logic;
signal RegWrite : std_logic;
signal RegDst : std_logic;
signal MemtoReg : std_logic;
signal stageout : std_logic_vector(2 downto 0);
-- No clocks detected in port list. Replace <clock> below with
-- appropriate port name

constant period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: maincontrol PORT MAP (
        PCWriteCond => PCWriteCond,
        PCWrite => PCWrite,
        PCSource => PCSource,
        MemRead => MemRead,
        MemWrite => MemWrite,
        IorD => IorD,
        IRWrite => IRWrite,
        ALUop => ALUop,
        ALUSrcB => ALUSrcB,
        ALUSrcA => ALUSrcA,
        RegWrite => RegWrite,
        RegDst => RegDst,
        MemtoReg => MemtoReg,
        stagein => stagein,
        opcode => opcode,
        stageout => stageout
    );

    -- Stimulus process
    stim_proc: process
    begin
        -- hold reset state for 100 ns.
        wait for 20 ns;

        stagein <= "000";
        wait for period;

        -- r-type --
        opcode <= "000000";

        stagein <= "001";
        wait for period;

        stagein <= "010";
        wait for period;

        stagein <= "011";
        wait for period;

        stagein <= "100";
        wait for period;

        -- lw --
        opcode <= "100011";

        stagein <= "001";
        wait for period;

        stagein <= "010";
        wait for period;

```

```

        stagein <= "011";
wait for period;

        stagein <= "100";
wait for period;

        stagein <= "101";
wait for period;

        -- SW --
opcode  <= "101011";

        stagein <= "001";
wait for period;

        stagein <= "010";
wait for period;

        stagein <= "011";
wait for period;

        stagein <= "100";
wait for period;

        -- beq --
opcode  <= "000100";

        stagein <= "001";
wait for period;

        stagein <= "010";
wait for period;

        stagein <= "011";
wait for period;

        -- j --
opcode  <= "000010";

        stagein <= "001";
wait for period;

        stagein <= "010";
wait for period;

        stagein <= "011";
wait for period;

        -- simulation time = 300 ns --
wait;
end process;

END;

```

WordALU_tb

```

-- Company:          comp. engr. KKU.
-- Engineer:         TK
--
-- Create Date:     09:55:02 08/22/2011
-- Design Name:
-- Module Name:    WordALU_tb - Behavioral
--
-- Dependencies:
--
-- Revision:

```

```

-- Revision 0.01 - File Created
-- Additional Comments:
--   "If you think you can do a thing or think you can't do a thing, you're right."
--   - Henry Ford

-----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity WordALU_tb is
end WordALU_tb;

architecture Behavioral of WordALU_tb is

component WordALU is
  Port ( a, b : in STD_LOGIC_VECTOR (31 downto 0);
         Binvert, CarryIn : in STD_LOGIC;
         Operation : in STD_LOGIC_VECTOR (1 downto 0);
         Result : out STD_LOGIC_VECTOR (31 downto 0);
         Overflow, Zero : out STD_LOGIC);
end component;

signal a, b : STD_LOGIC_VECTOR (31 downto 0);
signal Binvert, CarryIn : STD_LOGIC;
signal Operation : STD_LOGIC_VECTOR (1 downto 0);
signal Result : STD_LOGIC_VECTOR (31 downto 0);
signal Overflow, Zero : STD_LOGIC;

constant PERIOD : time := 100 ns;

begin

  walu: WordALU
  port map (
    a => a,
    b => b,
    Binvert => Binvert,
    CarryIn => CarryIn,
    Operation => Operation,
    Result => Result,
    Overflow => Overflow,
    Zero => Zero);

  PROCESS
BEGIN

  Binvert <= '0';
  CarryIn <= '0';

  -- AND --
  Operation <= "00";      -- 00: AND, 01: OR, 10: ADDITION, 11: Less (slt)
  a           <= "001111111100000110000001101010";
  b           <= "01011011110000001010010011110010";
  -- expect: "0001101111000000010000001100010" = '0x1bc02062'
  WAIT FOR PERIOD;

  -- OR --
  Operation <= "01";      -- 00: AND, 01: OR, 10: ADDITION, 11: Less (slt)
  a           <= "001111111100000110000001101010";

```

```

b           <= "0101101111000001010010011110010";
-- expect: "011111111110000111001001111010" = '0x7ff0e4fa'
WAIT FOR PERIOD;

-- ADDITION --
-- A + B; A > 0, B > 0, no overflow

Binvert <= '0';      -- A + B
CarryIn <= '0';
Operation <= "10";   -- 00: AND, 01: OR, 10: ADDITION, 11: Less (slt)

a           <= "001111111110000011000001101010";
b           <= "001111111000001010010011110010";
-- expect:    "011111110110001000010101011100" = 0x7fb1055c

WAIT FOR PERIOD;

-- A + B; A > 0, B > 0, overflow

Binvert <= '0';      -- A + B
CarryIn <= '0';
Operation <= "10";   -- 00: AND, 01: OR, 10: ADDITION, 11: Less (slt)

a           <= "011111111110000011000001101010";
b           <= "001111111000001010010011110010";
-- expect:    "1011111110110001000010101011100" = 0xbfb1055c

WAIT FOR PERIOD;

-- A + B; A < 0, B < 0, no overflow

Binvert <= '0';      -- A + B
CarryIn <= '0';
Operation <= "10";   -- 00: AND, 01: OR, 10: ADDITION, 11: Less (slt)

a           <= "11000100011001010011011000000000"; -- = 0xc4653600 = -1000000000
b           <= "10111011101000100010101101000000"; -- = 0xbbba22b40 = -1147000000
-- expect: "d1000000000001110110000101000000"; -- = 0x80076140 = -2147000000

WAIT FOR PERIOD;

-- A + B; A > 0, B < 0

Binvert <= '0';      -- A + B
CarryIn <= '0';
Operation <= "10";   -- 00: AND, 01: OR, 10: ADDITION, 11: Less (slt)

a           <= "01000100011001010011011000000000"; -- = 0x44653600 = 1147483648
b           <= "10111011101000100010101101000000"; -- = 0xbbba22b40 = -1147000000
-- expect: "?0000000000001110110000101000000"; -- = 0x00076140 = 483648

WAIT FOR PERIOD;

-- A + B; A < 0, B > 0

Binvert <= '0';      -- A + B
CarryIn <= '0';
Operation <= "10";   -- 00: AND, 01: OR, 10: ADDITION, 11: Less (slt)

a           <= "101110111010001000101011010000000"; -- = 0xbbba22b40 = -1147000000
b           <= "01000100011001010011011000000000"; -- = 0x44653600 = 1147483648
-- expect: "?0000000000001110110000101000000"; -- = 0x00076140 = 483648

WAIT FOR PERIOD;

-- A - B; A > 0, B > 0

Binvert <= '1';      -- A - B
CarryIn <= '1';

```

```

Operation <= "10";      -- 00: AND, 01: OR, 10: ADDITION, 11: Less (slt)

a                  <= "0011111111100000110000001101010"; -- = 0x3ff0606a = 1072717930
b                  <= "00111111110000001010010011110010"; -- = 0xfc0a4f2 = 1069589746
-- expect:        "0000000000101111011101101111000"           = 0x002fbb78 = 3128184

WAIT FOR PERIOD;

-- A - B; A > 0, B < 0, no overflow

Binvert <= '1';      -- A - B
CarryIn <= '1';
Operation <= "10";      -- 00: AND, 01: OR, 10: ADDITION, 11: Less (slt)

a                  <= "0011111111100000110000001101010"; -- = 0x3ff0606a = 1072717930
b                  <= "11111111111101100011110000000"; -- = 0xffffec780 = -80000
-- expect:        "0011111111100011001100011101010"           = 0x3ff198ea = 1072797930

WAIT FOR PERIOD;

-- A - B; A > 0, B < 0, overflow

Binvert <= '1';      -- A - B
CarryIn <= '1';
Operation <= "10";      -- 00: AND, 01: OR, 10: ADDITION, 11: Less (slt)

a                  <= "0111111111100000110000001101010"; -- = 0x7ff0606a = 2146459754
b                  <= "11111111110000101111011100000000"; -- = 0xffc2f700 = -4000000
-- expect:        "1000000001011010110100101101010"           = 0x802d696a ; 2150459754

WAIT FOR PERIOD;

-- A - B; A < 0, B < 0

-- <input code for this test case>

-- A - B; A < 0, B > 0, no overflow

-- <input code for this test case>

-- A - B; A < 0, B > 0, overflow

Binvert <= '1';      -- A - B
CarryIn <= '1';
Operation <= "10";      -- 00: AND, 01: OR, 10: ADDITION, 11: Less (slt)

a                  <= "11111111110000101111011100000000"; -- = 0xffc2f700 = -4000000
b                  <= "011111111110000110000001101010"; -- = 0x7ff0606a =
2146459754
-- expect:        "?0111111110100101001011010010110"           = 0x7fd29696 ; -2150459754

WAIT FOR PERIOD;

-- LESS (slt) --

Operation <= "11";      -- 00: AND, 01: OR, 10: ADDITION, 11: Less (slt)

-- a < b
a                  <= "00000000000000000000000000000000101"; -- 5
b                  <= "0000000000000000000000000000000011100"; -- 28
WAIT FOR PERIOD;

-- a = b
a                  <= "00000000000000000000000000000000110110"; -- 54
b                  <= "00000000000000000000000000000000110110"; -- 54
WAIT FOR PERIOD;

-- a > b
a                  <= "00000000000000000000000000000000110110"; -- 54

```

```

        b      <= "000000000000000000000000000011100"; -- 28
WAIT FOR PERIOD;

-- a < b, a < 0, b < 0
a      <= "1111111111111111111101110111111"; -- -545
b      <= "11111111111111111111011010100"; -- -300
WAIT FOR PERIOD;

-- a < b, a < 0, b > 0
a      <= "1111111111111111111101110111111"; -- -545
b      <= "000000000000000000000000100101100"; -- 300
WAIT FOR PERIOD;

-- simulation time: 1600 + 100 ns

END PROCESS;

```

end Behavioral;

regfile_tb

```

-- Company:          comp. engr. KKU.
-- Engineer:         TK
--
-- Create Date:      08:27:46 09/01/2011
-- Design Name:     regfile_tb - Behavioral
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
-- "Memory can change the shape of a room; it can change the color of a car.
-- And memories can be distorted. They're just an interpretation, they're not a record,
-- and they're irrelevant if you have the facts." - Leonard Shelby in Memento (2000)

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.numeric_std.ALL;

entity regfile_tb is
end regfile_tb;

architecture Behavioral of regfile_tb is

component regfile is
port(
    readreg1:           in std_logic_vector (4 downto 0);      -- index referring to a specific
register
    readreg2:           in std_logic_vector (4 downto 0);      -- index referring to a specific
register
    writereg:          in std_logic_vector (4 downto 0);      -- index referring to a specific
register
    writedata:          in std_logic_vector (31 downto 0);    -- data to put in the specified
register's content
    readdatal:          out std_logic_vector (31 downto 0);   -- data contained in register indexed by
readreg1
    readdatal:          out std_logic_vector (31 downto 0);   -- data contained in register indexed by
readreg2
    RegWrite:           in std_logic;
    clock:              in std_logic
);
end component;

signal readreg1 : std_logic_vector (4 downto 0);      -- index referring to a specific register

```

```

signal readreg2 : std_logic_vector (4 downto 0);
signal writereg : std_logic_vector (4 downto 0);
signal writedata: std_logic_vector (31 downto 0);
signal readdata1: std_logic_vector (31 downto 0);
signal readdata2: std_logic_vector (31 downto 0);
signal RegWrite : std_logic;
signal clk           : std_logic;

constant PERIOD      : time := 100 ns;
constant clkperiod   : time := 30 ns;

begin

    regs: regfile
    port map (
        readreg1      => readreg1,
        readreg2      => readreg2,
        writereg      => writereg,
        writedata     => writedata,
        readdata1     => readdata1,
        readdata2     => readdata2,
        RegWrite      => RegWrite,
        clock         => clk);

    process
    begin
        clk <= '0';
        wait for clkperiod;
        clk <= '1';
        wait for clkperiod;
    end process;

    process
    variable regidx: integer :=0;
    begin

        writedata      <= X"01FFAB00";
        writereg       <= "00001";
        wait for PERIOD/2;

        readreg1 <= "00000";
        readreg2 <= "00001";
        wait for PERIOD/2;

        RegWrite      <= '1';
        writedata     <= X"01FFAB00";
        writereg      <= "00001";
        wait for PERIOD/2;

        readreg1 <= "00000";
        readreg2 <= "00001";
        wait for PERIOD/2;

        readreg1 <= "10000";
        readreg2 <= "01000";
        wait for PERIOD/2;

        checkreg0: for regidx in 1 to 5 loop

            writereg <= std_logic_vector(to_unsigned(regidx, writereg'length));
            writedata <= std_logic_vector(to_unsigned(regidx*16, writedata'length));
            wait for PERIOD/2;

            readreg1 <= std_logic_vector(to_unsigned(regidx - 1, writereg'length));
            readreg2 <= std_logic_vector(to_unsigned(regidx, writereg'length));
            wait for PERIOD/2;

        end loop checkreg0;
    end;

```

```

-- simulation time = 800 ns

end process;

end Behavioral;

nbitregister_tb

-----
-- Company:          comp. engr. KKU.
-- Engineer:         TK
--
-- Create Date:     12:15:13 08/29/2011
-- Design Name:    nbitregister_tb - Behavioral
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity nbitregister_tb is
end nbitregister_tb;

architecture Behavioral of nbitregister_tb is

constant Nbits : integer := 32;

component nbitregister is
    generic (n : integer := Nbits);
    Port (
        win:           in std_logic_vector (Nbts-1 downto 0);
        clock:         in std_logic;
        regload:       in std_logic;
        regclear:      in std_logic;
        wout:          out std_logic_vector (Nbts-1 downto 0));
end component;

signal win:           std_logic_vector (Nbts-1 downto 0);
signal clk:          std_logic;
signal regload:      std_logic;
signal regclear:     std_logic;
signal wout:          std_logic_vector (Nbts-1 downto 0);

constant PERIOD : time := 50 ns;

begin

reg: nbitregister
port map (
    win => win,
    clock => clk,
    regload => regload,
    regclear => regclear,
    wout => wout);

PROCESS
BEGIN
    clk <= '0';
    wait for PERIOD/2;
    clk <= '1';
    wait for PERIOD/2;
END PROCESS;

```

```

PROCESS
BEGIN
    win          <= "1111111000000100000000110100010";
    regload <= '0';
    regclear<= '0';
    wait for PERIOD/4;

    regload <= '1';
    wait for PERIOD;

    regload <= '0';
    regclear<= '1';
    wait for PERIOD;

    -- simulation time = 150 ns

END PROCESS;

```

end Behavioral;

--

mux2_tb

```

--
-----
-- Company:           comp. engr. KKU.
-- Engineer:          TK
--
-- Create Date:       16:27:46 09/01/2011
-- Design Name:      mux2_tb - Behavioral
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
-- "Memory can change the shape of a room; it can change the color of a car.
-- And memories can be distorted. They're just an interpretation, they're not a record,
-- and they're irrelevant if you have the facts." - Leonard Shelby in Memento (2000)
-----
```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mux2_tb is
end mux2_tb;

architecture Behavioral of mux2_tb is

component mux2 is
port(
    sel:      in std_logic;
    ch1:      in std_logic_vector(31 downto 0);
    ch2:      in std_logic_vector(31 downto 0);
    muxout: out std_logic_vector (31 downto 0)
);
end component;

signal sel:      std_logic;
signal ch1:      std_logic_vector(31 downto 0);
signal ch2:      std_logic_vector(31 downto 0);
signal muxout: std_logic_vector (31 downto 0);

constant PERIOD      : time := 100 ns;

begin

    mux: mux2

```

```

port map (
    sel          => sel,
    ch1         => ch1,
    ch2         => ch2,
    muxout     => muxout);

process
begin
    ch1 <= X"0AAA00AA";
    ch2 <= X"0B00000B";

    sel <= '0';
    wait for PERIOD;
    ch1 <= X"1A1A11AA";
    wait for PERIOD/2;
    ch1 <= X"A00A00AA";
    wait for PERIOD/2;

    sel <= '1';
    wait for PERIOD;
    ch2 <= X"0C00000C";
    wait for PERIOD/4;
    ch2 <= X"0D00000D";
    wait for PERIOD/4;

    -- simulation time = 400 ns
end process;

```

```
end Behavioral;
```

```
--
```

mux4_tb

```

--
-----
-- Company:           comp. engr. KKU.
-- Engineer:          TK
--
-- Create Date:       12:34:46 09/02/2011
-- Design Name:      mux4_tb - Behavioral
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
-- "You cannot dream yourself into a character; you must hammer and forge yourself one."
-- - By the English historian, James Anthony Froude (1818-1894) from his book, The Nemesis of Faith.
-----
```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mux4_tb is
end mux4_tb;

architecture Behavioral of mux4_tb is

component mux4 is
port(
    sel:      in std_logic_vector(1 downto 0);
    ch1:      in std_logic_vector(31 downto 0);
    ch2:      in std_logic_vector(31 downto 0);
    ch3:      in std_logic_vector(31 downto 0);
    ch4:      in std_logic_vector(31 downto 0);
    muxout: out std_logic_vector (31 downto 0)
);

```

```

end component;

signal sel:          std_logic_vector(1 downto 0);
signal ch1:          std_logic_vector(31 downto 0);
signal ch2:          std_logic_vector(31 downto 0);
signal ch3:          std_logic_vector(31 downto 0);
signal ch4:          std_logic_vector(31 downto 0);
signal muxout: std_logic_vector (31 downto 0);

constant PERIOD      : time := 100 ns;

begin

    mux: mux4
    port map (
        sel           => sel,
        ch1          => ch1,
        ch2          => ch2,
        ch3          => ch3,
        ch4          => ch4,
        muxout      => muxout);

    process
    begin
        ch1 <= X"10A000AA";
        ch2 <= X"20B0000B";
        ch3 <= X"30C0000C";
        ch4 <= X"40D0000D";

        sel <= "00";
        wait for PERIOD;

        ch1 <= X"111000AA";
        wait for PERIOD/2;

        ch1 <= X"122000AA";
        wait for PERIOD/2;

        sel <= "01";
        wait for PERIOD;

        sel <= "10";
        wait for PERIOD;

        sel <= "11";
        wait for PERIOD;

        -- simulation time = 500 ns
    end process;

end Behavioral;
--



signextend_tb

-- 
----- 
-- Company:
-- Engineer:
-- 
-- Create Date:  00:25:00 09/05/2011
-- Design Name:
-- Module Name: C:/xilinx_tutorial/Ch05/signextend_tb.vhd
-- Project Name: Ch05
-- Target Device:
-- Tool versions:
-- Description:

```

```

-- VHDL Test Bench Created by ISE for module: signextend
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-- Notes:
-- This testbench has been automatically generated using types std_logic and
-- std_logic_vector for the ports of the unit under test. Xilinx recommends
-- that these types always be used for the top-level I/O of a design in order
-- to guarantee that the testbench will bind correctly to the post-implementation
-- simulation model.

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

ENTITY signextend_tb IS
END signextend_tb;

ARCHITECTURE behavior OF signextend_tb IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT signextend
    PORT(
        halfword : IN  std_logic_vector(15 downto 0);
        fullword : OUT  std_logic_vector(31 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal halfword : std_logic_vector(15 downto 0) := (others => '0');

    --Outputs
    signal fullword : std_logic_vector(31 downto 0);
    -- No clocks detected in port list. Replace <clock> below with
    -- appropriate port name

    constant PERIOD : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: signextend PORT MAP (
        halfword => halfword,
        fullword => fullword
    );

    -- Stimulus process
    stim_proc: process
    begin

        halfword <= x"80AB";
        wait for 100 ns;

        halfword <= x"4012";
        wait for 100 ns;

    end process;

END;

```

```

-- 
ch5mem_tb

-- 
-----  

-- Company:  

-- Engineer:  

--  

-- Create Date: 21:05:13 09/04/2011  

-- Design Name:  

-- Module Name: ch5mem_tb - Behavioral  

-- Project Name:  

-- Target Devices:  

-- Tool versions:  

-- Description:  

--  

-- Dependencies:  

--  

-- Revision:  

-- Revision 0.01 - File Created  

-- Additional Comments:  

--  

-----  

library IEEE;  

use IEEE.STD_LOGIC_1164.ALL;  

entity ch5mem_tb is  

end ch5mem_tb;  

architecture Behavioral of ch5mem_tb is  

component ch5mem is
    port
    (
        clock          : in std_logic;
        datain         : in std_logic_vector(31 downto 0);
        memaddress    : in std_logic_vector(31 downto 0);
        memwrite       : in std_logic;
        memread        : in std_logic;
        dataout        : out std_logic_vector(31 downto 0);
        enable         : in std_logic;
        startup        : in std_logic -- to load pre-written data
    );
end component;  

signal clk          : std_logic;
signal data         : std_logic_vector(31 DOWNTO 0);
signal addr         : std_logic_vector(31 DOWNTO 0);
signal memwrite     : std_logic;
signal memread      : std_logic;
signal q            : std_logic_vector(31 DOWNTO 0);
signal en           : std_logic;
signal startup      : std_logic;  

constant PERIOD : time := 50 ns;  

begin
    mem: ch5mem
    port map (
        clock      => clk,
        datain     => data,
        memaddress => addr,
        memwrite   => memwrite,
        memread    => memread,
        dataout    => q,

```

```

enable      => en,
startup     => startup);

process
begin
    clk <= '0';
    wait for PERIOD/2;
    clk <= '1';
    wait for PERIOD/2;
end process;

PROCESS
BEGIN
    en      <= '1';

--        startup <= '1';
--        wait for PERIOD/10;
--        startup <= '0';
--        wait for PERIOD/20;
--        startup <= '1';
--        wait for PERIOD/10;
--        startup <= '0';

-- test read pre-written data --
memread <= '1';
memwrite <= '0';

addr <= x"10000000";
wait for PERIOD;

addr <= x"10000004";
wait for PERIOD;

-- test write memory --
memread <= '0';
wait for PERIOD/4;

memwrite <= '1';
addr <= x"10000000";
data <= x"00000028";
wait for PERIOD * 3/4;

-- test read memory after re-written --
memwrite <= '0';
wait for PERIOD/4;

memread <= '1';
addr <= x"10000000";
wait for PERIOD * 3/4;

-- test read pre-written program --
memread <= '1';
addr <= x"00400000";
wait for PERIOD/2;

addr <= x"00400004";
wait for PERIOD;

addr <= x"00400008";
wait for PERIOD;

addr <= x"0040000C";
wait for PERIOD;

addr <= x"00400010";
wait for PERIOD;

addr <= x"00400014";

```

```

    wait for PERIOD;

    addr <= x"00400018";
    wait for PERIOD;

    addr <= x"0040001C";
    wait for PERIOD;

    addr <= x"00400020";
    wait for PERIOD;

    -- test overwrite program segment --
    memread <= '0';

    addr <= x"00400000";
    data <= x"00000000";
    wait for PERIOD/4;

    memwrite <= '1';
    wait for PERIOD * 3/4;

    memwrite <= '0';
    wait for PERIOD/4;

    memread <= '1';
    wait for PERIOD * 3/4;

    addr <= x"00400004";
    wait for PERIOD/2;

    en <= '0';
    wait for PERIOD/2;

    -- set simulation time to 950ns

END PROCESS;

end Behavioral;
--
```

Components

regfile.vhd

```

--
-----
-- Company:          comp. eng. KKU.
-- Engineer:         TK
--
-- Create Date:     14:46:23 08/31/2011
-- Module Name:     regfile - Behavioral
-- Description:    register file
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

entity regfile is
```

```

port(
    readreg1:           in std_logic_vector (4 downto 0);      -- index referring to a specific
register
    readreg2:           in std_logic_vector (4 downto 0);      -- index referring to a specific
register
    writereg:          in std_logic_vector (4 downto 0);      -- index referring to a specific
register
    writedata:          in std_logic_vector (31 downto 0);     -- data to put in the specified
register's content
    readdata1:          out std_logic_vector (31 downto 0);    -- data contained in register indexed by
readreg1
    readdata2:          out std_logic_vector (31 downto 0);    -- data contained in register indexed by
readreg2
    RegWrite:           in std_logic;
    clock:              in std_logic
);
end regfile;

architecture Behavioral of regfile is
    TYPE registers IS ARRAY(0 TO 2 ** 5 - 1) OF std_logic_vector(31 DOWNTO 0);

    SIGNAL reg_block : registers := (
        0 => x"00000000",
        1 => x"FFFFFFFF",
        2 => x"FFFFFFFF",
        3 => x"FFFFFFFF",
        4 => x"FFFFFFFF",
        5 => x"FFFFFFFF",
        6 => x"FFFFFFFF",
        7 => x"FFFFFFFF",
        8 => x"FFFFFFFF",
        9 => x"FFFFFFFF",
        10 => x"FFFFFFFF",
        11 => x"FFFFFFFF",
        12 => x"FFFFFFFF",
        13 => x"FFFFFFFF",
        14 => x"FFFFFFFF",
        15 => x"FFFFFFFF",
        16 => x"10000000", -- base address for data segment
        17 => x"FFFFFFFF",
        18 => x"FFFFFFFF",
        19 => x"FFFFFFFF",
        20 => x"FFFFFFFF",
        21 => x"FFFFFFFF",
        22 => x"FFFFFFFF",
        23 => x"FFFFFFFF",
        24 => x"FFFFFFFF",
        25 => x"FFFFFFFF",
        26 => x"FFFFFFFF",
        27 => x"FFFFFFFF",
        28 => x"FFFFFFFF",
        29 => x"FFFFFFFF",
        30 => x"FFFFFFFF",
        31 => x"FFFFFFFF");
BEGIN
    PROCESS (clock, readreg1, readreg2)
    BEGIN
        readdata1 <= reg_block(to_integer(unsigned(readreg1)));
        readdata2 <= reg_block(to_integer(unsigned(readreg2)));

        IF (RegWrite = '1') THEN
            reg_block(to_integer(unsigned(writereg))) <= writedata;
        END IF;
    END PROCESS;
END Behavioral;

```

--

WordALU.vhd

```
--  
-- Company:  
-- Engineer:  
--  
-- Create Date: 08:54:36 08/22/2011  
-- Design Name:  
-- Module Name: WordALU - Behavioral  
-- Project Name:  
-- Target Devices:  
-- Tool versions:  
-- Description:  
--  
-- Dependencies:  
--  
-- Revision:  
-- Revision 0.01 - File Created  
-- Additional Comments:  
--  
-----  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
  
-- Uncomment the following library declaration if using  
-- arithmetic functions with Signed or Unsigned values  
--use IEEE.NUMERIC_STD.ALL;  
  
-- Uncomment the following library declaration if instantiating  
-- any Xilinx primitives in this code.  
--library UNISIM;  
--use UNISIM.VComponents.all;  
  
entity WordALU is  
    Port ( a : in STD_LOGIC_VECTOR (31 downto 0);  
           b : in STD_LOGIC_VECTOR (31 downto 0);  
           Binvert : in STD_LOGIC;  
           CarryIn : in STD_LOGIC;  
           Operation : in STD_LOGIC_VECTOR (1 downto 0);  
           Result : out STD_LOGIC_VECTOR (31 downto 0);  
           Overflow : out STD_LOGIC;  
           Zero : out STD_LOGIC);  
end WordALU;  
  
architecture Behavioral of WordALU is  
  
COMPONENT BitALU  
Port ( a, b, cin, Binvert, Lessin : in STD_LOGIC;  
      Qo, cout : out STD_LOGIC;  
      operation : in STD_LOGIC_VECTOR (1 downto 0)  
      );  
END COMPONENT;  
  
component MSBALU  
port (  
      a, b, cin, Binvert, Lessin : in STD_LOGIC;  
      Qo, set, overflow : out STD_LOGIC;  
      operation : in STD_LOGIC_VECTOR (1 downto 0)  
      );  
end component;  
  
signal c: STD_LOGIC_VECTOR (31 downto 0);  
signal set : STD_LOGIC;  
signal qr: STD_LOGIC_VECTOR (31 downto 0);
```

```

begin

    c(0) <= CarryIn;

    bit0: BitALU port map(
        a => a(0),
        b => b(0),
        cin => c(0),
        Binvert => Binvert,
        Lessin => set,
        Qo => qr(0),
        cout => c(1),
        operation => Operation
    );

    bits1to30: for i in 1 to 30 generate
        ibit: BitALU port map(
            a => a(i),
            b => b(i),
            cin => c(i),
            Binvert => Binvert,
            Lessin => '0',
            Qo => qr(i),
            cout => c(i+1),
            operation => Operation
        );
    end generate;

    bit31: MSBALU port map (
        a => a(31),
        b => b(31),
        cin => c(31),
        Binvert => Binvert,
        Lessin => '0',
        Qo => qr(31),
        set => set,
        overflow => Overflow,
        operation => Operation
    );

    Result <= qr;

    Zero <= not (
        qr(0) or qr(1) or qr(2) or qr(3) or
        qr(4) or qr(5) or qr(6) or qr(7) or
        qr(8) or qr(9) or qr(10) or qr(11) or
        qr(12) or qr(13) or qr(14) or qr(15) or
        qr(16) or qr(17) or qr(18) or qr(19) or
        qr(20) or qr(21) or qr(22) or qr(23) or
        qr(24) or qr(25) or qr(26) or qr(27) or
        qr(28) or qr(29) or qr(30) or qr(31) );
    );
end Behavioral;
--
```

nbitregister.vhd

```

--
-----
-- Company:          comp. engr. KKU.
-- Engineer:         TK
--
-- Create Date:     11:53:57 08/29/2011
-- Design Name:
-- Module Name:    nbitregister - Behavioral
-- Description:
--     adapted from http://esd.cs.ucr.edu/labs/tutorial/register.vhd, retrieved on Aug, 29th, 2011.
--
```

```

-- 
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments: "Attitude is a little thing that makes a big difference." - Winston Churchill
-- 

-----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity nbitregister is
generic(n: integer := 32);
port(
    win:          in std_logic_vector (n-1 downto 0);
    clock:        in std_logic;
    regload:      in std_logic;
    regclear:     in std_logic;
    wout:         out std_logic_vector (n-1 downto 0)
);
end nbitregister;

architecture Behavioral of nbitregister is

    signal wtmp : std_logic_vector (n-1 downto 0);

begin
    process(win, clock, regload, regclear)
    begin
        if regclear = '1' then
            wtmp <= (wtmp'range => '0');
        elsif (clock = '1' and clock'event) then
            if regload = '1' then
                wtmp <= win;
            end if;
        end if;
    end process;

    wout <= wtmp;
end Behavioral;
-- 

```

mux4.vhd

```

-- 
----- 
-- Company:      comp. engr. KKU.
-- Engineer:     TK
-- 
-- Create Date:   11:58:12 09/02/2011
-- Design Name:
-- Module Name:   mux - Behavioral
-- 
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
-- "The idea of wilderness needs no defense. It only needs more defenders."
-- - Edward Abbey
-- 

-----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
--use IEEE.NUMERIC_STD.ALL;

entity mux4 is
port(
    sel:          in std_logic_vector(1 downto 0);
    ch1:          in std_logic_vector(31 downto 0);

```

```

        ch2:      in std_logic_vector(31 downto 0);
        ch3:      in std_logic_vector(31 downto 0);
        ch4:      in std_logic_vector(31 downto 0);
        muxout: out std_logic_vector (31 downto 0)
    );
end mux4;

architecture Behavioral of mux4 is

begin
    SEL_PROCESS: process (sel,ch1,ch2,ch3,ch4)
    begin
        case sel is
            when "00"  => muxout <= ch1;
            when "01"  => muxout <= ch2;
                when "10"  => muxout <= ch3;
                when "11"  => muxout <= ch4;
            when others => muxout <= (muxout'range => 'Z');
        end case;
    end process SEL_PROCESS;
end Behavioral;
--
```

mux2.vhd

```

--
-----
-- Company:          comp. engr. KKU.
-- Engineer:         TK
--
-- Create Date:     15:50:12 09/01/2011
-- Design Name:    mux - Behavioral
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
--use IEEE.NUMERIC_STD.ALL;

entity mux2 is
port(
    sel:      in std_logic;
    ch1:      in std_logic_vector(31 downto 0);
    ch2:      in std_logic_vector(31 downto 0);
    muxout: out std_logic_vector (31 downto 0)
);
end mux2;

architecture Behavioral of mux2 is

begin
    SEL_PROCESS: process (sel,ch1,ch2)
    begin
        case sel is
            when '0'  => muxout <= ch1;
            when '1'  => muxout <= ch2;
            when others => muxout <= (muxout'range => 'Z');
        end case;
    end process SEL_PROCESS;
end Behavioral;
--
```

signextend.vhd

```

-- 
-- Company:
-- Engineer:
--
-- Create Date: 00:19:34 09/05/2011
-- Design Name:
-- Module Name: signextend - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity signextend is
    Port ( halfword : in STD_LOGIC_VECTOR (15 downto 0);
           fullword : out STD_LOGIC_VECTOR (31 downto 0));
end signextend;

architecture Behavioral of signextend is

signal upperhalf : STD_LOGIC_VECTOR (15 downto 0);

begin

    fullword <= upperhalf & halfword;
    upperhalf <= (upperhalf'range => halfword(15));

end Behavioral;
-- 
```

ALUControl.vhd

```

-- 
-- Company:          comp. eng. KKU.
-- Engineer:         TK
--
-- Create Date: 08:48:11 09/06/2011
-- Design Name:
-- Module Name: ALUControl - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
--
-- Dependencies:
-- 
```

```

-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--

-----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity ALUControl is

    port(
        ALUOp      : in std_logic_vector(1 downto 0);
        funct      : in std_logic_vector(5 downto 0); -- I Rout(5 downto 0)
        Binvert    : out std_logic;
        Operation  : out std_logic_vector(1 downto 0) );
end ALUControl;

architecture Behavioral of ALUControl is

begin

    ALUControl: process(ALUOp, funct)
    begin

        case ALUop is
        when "00" =>
            -- lw/sw: add --
            Binvert <= '0';
            Operation <= "10";
        when "01" =>
            -- beq: sub --
            Binvert <= '1';
            Operation <= "10";
        when "10" =>
            -- R-type --
            case funct is
            when "100000" =>
                -- add --
                Binvert <= '0';
                Operation <= "10";

            when "100010" =>
                -- sub --
                Binvert <= '1';
                Operation <= "10";

            when "100100" =>
                -- and --
                Binvert <= '0';
                Operation <= "00";

            when "100101" =>
                -- or --
                Binvert <= '0';
                Operation <= "01";

            when "101010" =>
                -- slt --
                Binvert <= '1';

```

```

        Operation <= "11";

        when others => Binvert <= '0'; Operation <= "00";
        end case;
    when others =>
        -- default case --
        Binvert <= '0';
        Operation <= "00";
    end case;

end process;

end Behavioral;

```

maincontrol.vhd

```

--
-----
-- Company:          comp. engr. KKU.
-- Engineer:         TK
--
-- Create Date:     07:41:53 09/06/2011
-- Design Name:
-- Module Name:     maincontrol - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--     "Truth will set you free." - James A. Garfield
-----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity maincontrol is

    port(
        PCWriteCond : out std_logic;
        PCWrite      : out std_logic;
        PCSource     : out std_logic_vector(1 downto 0);
        MemRead      : out std_logic;
        MemWrite     : out std_logic;
        IorD         : out std_logic;
        IRWrite      : out std_logic;
        ALUop        : out std_logic_vector(1 downto 0);
        ALUSrcB     : out std_logic_vector(1 downto 0);
        ALUSrcA     : out std_logic;
        RegWrite     : out std_logic;
        RegDst       : out std_logic;
        MemtoReg     : out std_logic;
        stagein      : in  std_logic_vector(2 downto 0);

```

```

        opcode      : in  std_logic_vector(5 downto 0); -- I Rout(31 downto 26)
        stageout    : out std_logic_vector(2 downto 0)      );
end maincontrol;

architecture Behavioral of maincontrol is
begin
    MainControl: process(stagein)
    begin
        case stagein is
            when "000" =>
                -- boot up --
                PCWrite <= '1'; PCSource <= "11";
                MemRead <= '0'; MemWrite <= '0'; IRWrite <= '0'; RegWrite <= '0';
                stageout <= "001";

            when "001" =>
                -- Instruction Fetch --
                PCWriteCond <= '0';      PCWrite <= '1'; IorD <= '0';
                MemRead <= '1';         MemWrite <= '0'; MemtoReg <= '0';
                IRWrite <= '1';         PCSource <= "00";
                ALUop <= "00";          ALUSrcB <= "01";           ALUSrcA <= '0';
                RegWrite <= '0';         RegDst <= '0';

                stageout <= "010";

            when "010" =>
                -- Instruction Decode & Branch Address Calculation --
                PCWriteCond <= '0';      PCWrite <= '0'; IorD <= '0';
                MemRead <= '0';         MemWrite <= '0'; MemtoReg <= '0';
                IRWrite <= '0';         PCSource <= "00";
                ALUop <= "00";          ALUSrcB <= "11";           ALUSrcA <= '0';
                RegWrite <= '0';         RegDst <= '0';

                stageout <= "011";

            when "011" =>
                case opcode is
                    when "000000" =>
                        -- r-type --
                        PCWriteCond <= '0';      PCWrite <= '0'; IorD <= '0';
                        MemRead <= '0';         MemWrite <= '0'; MemtoReg <= '0';
                        IRWrite <= '0';         PCSource <= "00";
                        ALUop <= "10";          ALUSrcB <= "00";           ALUSrcA <= '1';
                        RegWrite <= '0';         RegDst <= '0';

                        stageout <= "100";

                    when "100011" =>
                        -- lw --
                        PCWriteCond <= '0';      PCWrite <= '0'; IorD <= '0';
                        MemRead <= '0';         MemWrite <= '0'; MemtoReg <= '0';
                        IRWrite <= '0';         PCSource <= "00";
                        ALUop <= "00";          ALUSrcB <= "10";           ALUSrcA <= '1';
                        RegWrite <= '0';         RegDst <= '0';

                        stageout <= "100";

                    when "101011" =>
                        -- sw --
                        PCWriteCond <= '0';      PCWrite <= '0'; IorD <= '0';
                        MemRead <= '0';         MemWrite <= '0'; MemtoReg <= '0';
                        IRWrite <= '0';         PCSource <= "00";
                        ALUop <= "00";          ALUSrcB <= "10";           ALUSrcA <= '1';
                        RegWrite <= '0';         RegDst <= '0';
                end case;
        end when;
    end process;
end Behavioral;

```

```

        stageout <= "100";

when "000100" =>
    -- beq --
    PCWriteCond <= '1';
    MemRead <= '0';
    IRWrite <= '0';
    ALUop <= "01";
    RegWrite <= '0';
    PCWrite <= '0'; IorD <= '0';
    MemWrite <= '0'; MemtoReg <= '0';
    PCSource <= "01";
    ALUSrcB <= "00";           ALUSrcA <= '1';
    RegDst <= '0';

        stageout <= "001";

when "000010" =>
    -- j --
    PCWriteCond <= '0';
    MemRead <= '0';
    IRWrite <= '0';
    ALUop <= "00";
    RegWrite <= '0';
    PCWrite <= '1'; IorD <= '0';
    MemWrite <= '0'; MemtoReg <= '0';
    PCSource <= "10";
    ALUSrcB <= "00";           ALUSrcA <= '0';
    RegDst <= '0';

        stageout <= "001";

when others =>
    -- unknown operation --
    stageout <= "000";
end case;
when "100" =>
    case opcode is
        when "000000" =>
            -- r-type --
            PCWriteCond <= '0';
            MemRead <= '0';
            IRWrite <= '0';
            ALUop <= "00";
            RegWrite <= '1';
            PCWrite <= '0'; IorD <= '0';
            MemWrite <= '0'; MemtoReg <= '0';
            PCSource <= "00";
            ALUSrcB <= "00";           ALUSrcA <= '0';
            RegDst <= '1';

            stageout <= "001";

        when "100011" =>
            -- lw --
            PCWriteCond <= '0';
            MemRead <= '1';
            IRWrite <= '0';
            ALUop <= "00";
            RegWrite <= '0';
            PCWrite <= '0'; IorD <= '1';
            MemWrite <= '0'; MemtoReg <= '0';
            PCSource <= "00";
            ALUSrcB <= "00";           ALUSrcA <= '0';
            RegDst <= '0';

            stageout <= "101";

        when "101011" =>
            -- sw --
            PCWriteCond <= '0';
            MemRead <= '0';
            IRWrite <= '0';
            ALUop <= "00";
            RegWrite <= '0';
            PCWrite <= '0'; IorD <= '1';
            MemWrite <= '1'; MemtoReg <= '0';
            PCSource <= "00";
            ALUSrcB <= "00";           ALUSrcA <= '0';
            RegDst <= '0';

            stageout <= "001";

        when others =>
            -- unknown operation --
            stageout <= "000";
    end case;
when "101" =>

    if opcode = "100011" then
        -- lw --
        PCWriteCond <= '0';
        MemRead <= '0';
        PCWrite <= '0'; IorD <= '0';
        MemWrite <= '0'; MemtoReg <= '1';

```

```

        IRWrite <= '0';          PCSource <= "00";
        ALUop <= "00";          ALUSrcB <= "00";      ALUSrcA <= '0';
        RegWrite <= '1';         RegDst <= '0';

    end if;

    stageout <= "001";
when others =>
    -- default --
    stageout <= "000";
end case;

end process;

end Behavioral;
--
```

ch5mem.vhd

```

-- Company:
-- Engineer:
--
-- Create Date: 19:18:21 09/04/2011
-- Design Name:
-- Module Name: ch5mem - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description: to provide interface of 32-bit address/data
--                                         It allows only addresses:
--                                         1000 0000 to 1000 00FF for the data segment
--                                         and 0040 0000 to 0040 00FF for the program segment (full range:
0040 0000-0FFF FFFF)
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
--use IEEE.STD_LOGIC_ARITH.ALL;

entity ch5mem is
    port
    (
        clock           : in std_logic;
        datain          : in std_logic_vector(31 downto 0);
        memaddress     : in std_logic_vector(31 downto 0);
        memwrite        : in std_logic;
        memread         : in std_logic;
        dataout         : out std_logic_vector(31 downto 0);
        enable          : in std_logic;
        startup         : in std_logic -- to load pre-written data
    );
end ch5mem;

architecture Behavioral of ch5mem is
    type RAMROM is array(0 TO 2 ** 8 - 1) of std_logic_vector(31 downto 0);
    signal data_block : RAMROM;
    signal program_block: RAMROM;
```

```

begin

    process(enable, clock, memread, memwrite, memaddress, startup)
        variable index: integer range 0 to 7;
        begin

            if startup = '1' then
                -- initialize the ROM contents
                program_block(0) <= x"8e080000"; -- [00400000] lw $t0,
0($s0)
                program_block(1) <= x"8e090004"; -- [00400004] lw $t1,
4($s0)
                program_block(2) <= x"0109502a"; -- [00400008] slt $t2,
$t0, $t1
                program_block(3) <= x"11400003"; -- [0040000C] beq $t2,
$zero, LAB_t1ELTt0
                program_block(4) <= x"01285822"; -- [00400010] sub $t3,
$t1, $t0
                program_block(5) <= x"08100007"; -- [00400014] j
LAB_SAVE
                program_block(6) <= x"01095822"; -- [00400018] LAB_t1ELTt0: sub $t3, $t0, $t1
                program_block(7) <= x"ae0b0008"; -- [0040001C] LAB_SAVE: sw $t3, 8($s0)
                program_block(8) <= x"8e080008"; -- [00400020] lw $t0,
8($s0) # to check if it is well-saved in memory

                -- initialize the data content
                -- This may not sound practical, but since we don't have any instruction dealing with a
constant yet.
                -- So, it is for simplicity sake of homework.
                data_block(0) <= x"00000019"; -- [10000000]
                data_block(1) <= x"00000037"; -- [10000004]

-- [10000008]

-- after run, it should has a value, abs( data_block(0) - data_block(1) ) = x"0000001E"

        end if;

        -- 0x10000XX [0001 0000 0000 0000 00xx xxxx xx--] => data segment;
        -- 0x00400XX [0000 0000 0100 0000 0000 00xx xxxx xx--] => program segment

        index := to_integer(unsigned( memaddress(9 downto 2) ));

        if (enable = '1' and memread = '1') then

            if memaddress(31 downto 10)      = "000100000000000000000000" then
                dataout <= data_block(index);
            elsif memaddress(31 downto 10) = "00000000100000000000" then
                dataout <= program_block(index);
            else
                dataout <= (dataout'range => 'Z');
            end if;

        elsif (enable = '1' and memwrite = '1' and clock'event and clock = '0') then

            if memaddress(31 downto 10)      = "000100000000000000000000" then
                data_block(index) <= datain;
            elsif memaddress(31 downto 10) = "00000000100000000000" then
                program_block(index) <= datain;
            end if;

            dataout <= (dataout'range => 'Z');

        else
            dataout <= (dataout'range => 'Z');
        end if;

    end process;

```

```
end Behavioral;  
--
```