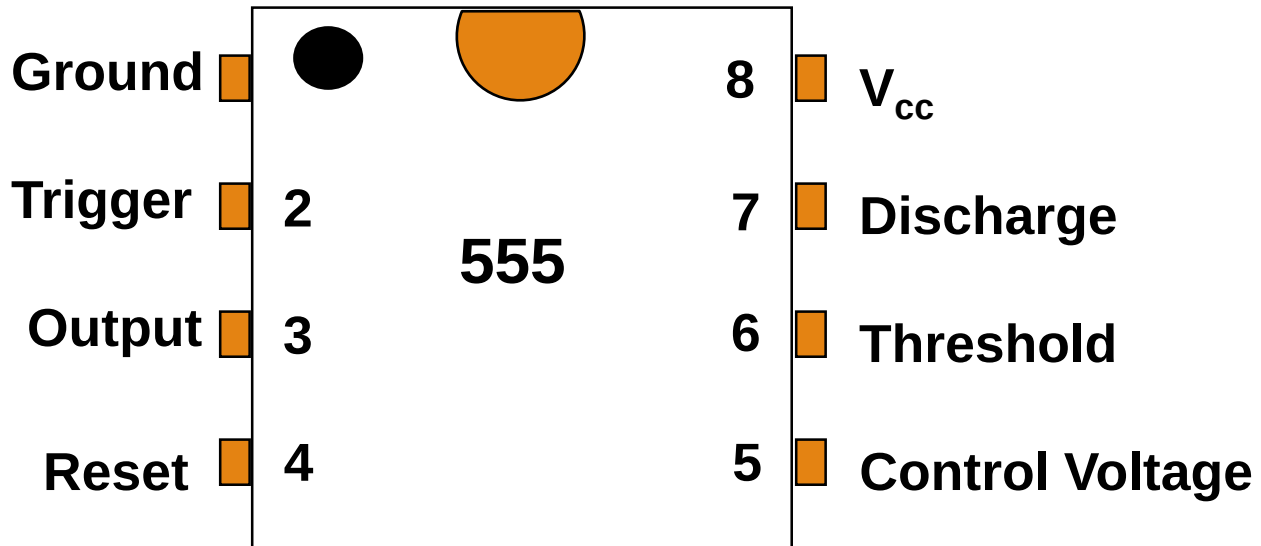


EE2-07: 555 IC Timer

Objectives

- To get familiarized with the LM 555 Timer IC and its usage.
- To design a monostable multivibrator circuit (“one-shot”).
- To design an astable multivibrator circuit (free-running oscillator).

555 Timer pin layout




The **trigger** and **reset** inputs are active LOW inputs.

Output goes HIGH when triggered.

555 Timer specifications


- Supply voltage: 4.5 V to 18 V
- Power dissipation: 600 mW
- Threshold current: 0.1 mA
- Trigger current: 0.5 mA
- Maximum output source/sink current: 200 mA

555 Timer functional block diagram

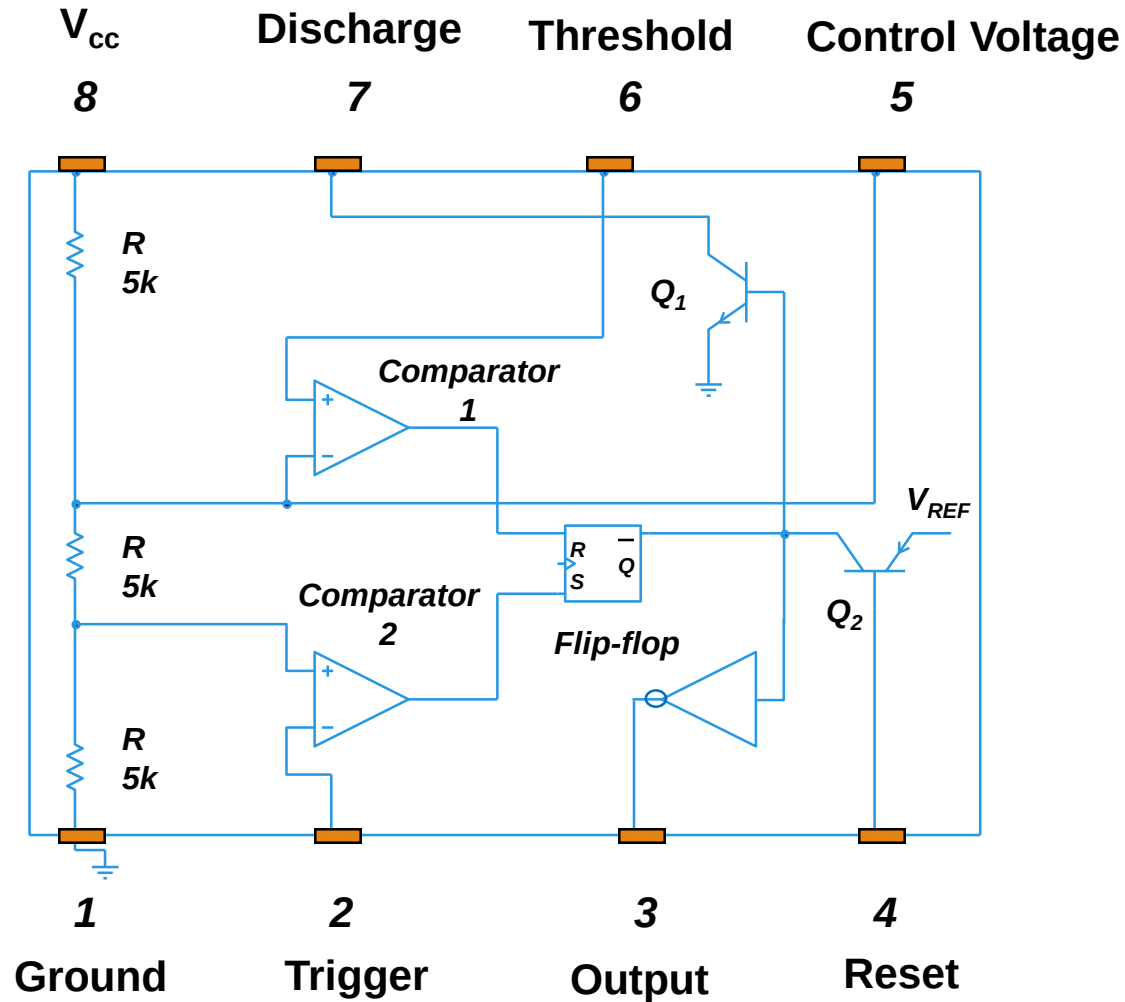



The output of a 555 timer is either HIGH (close to $+V_{CC}$) or LOW (close to GND).

1. Monostable multivibrator

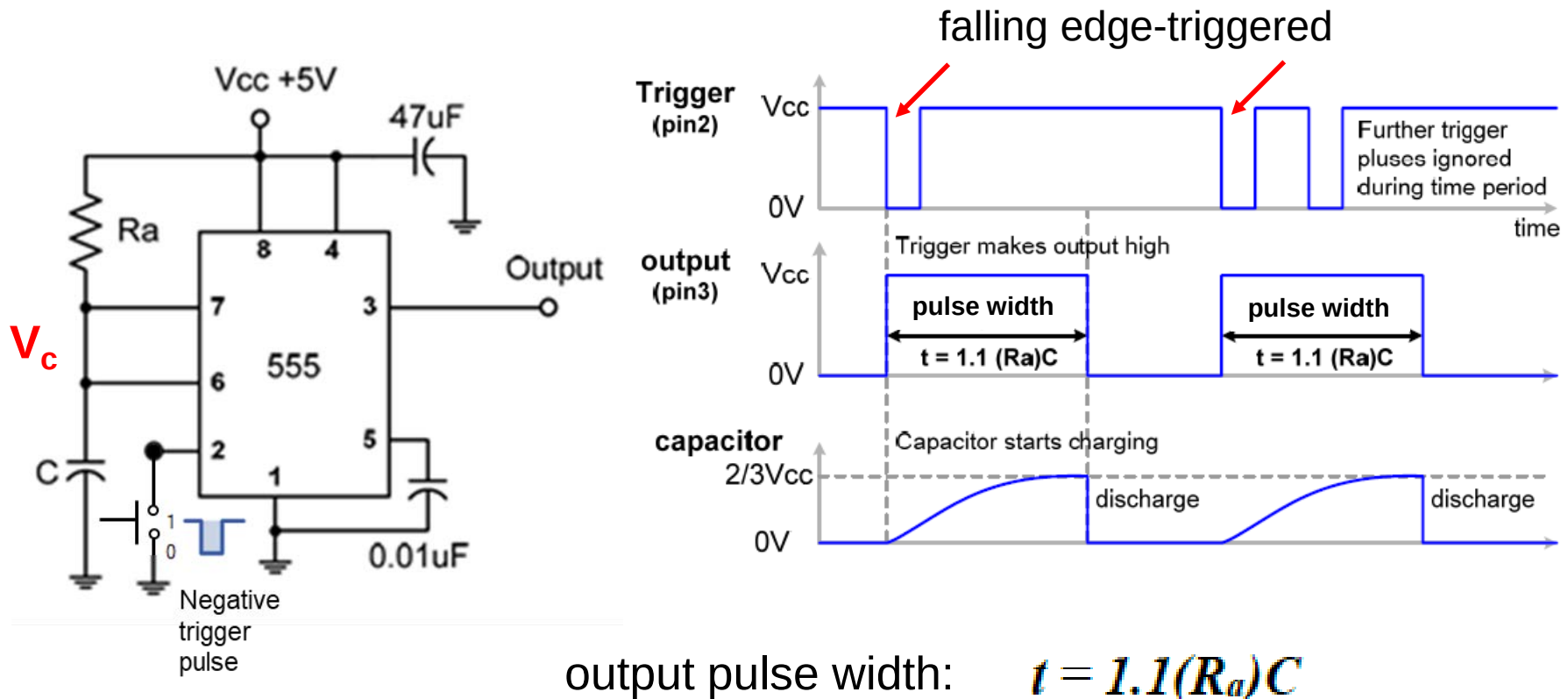

Each time the 555 timer is triggered, the output will go HIGH for a specified amount of time, then it will return to LOW and await another trigger signal.

2. Astable multivibrator

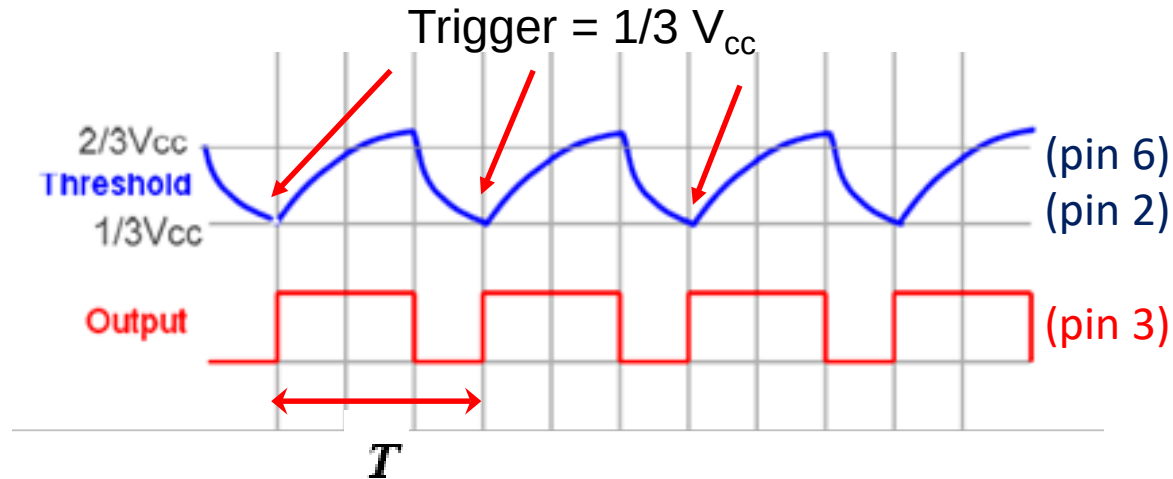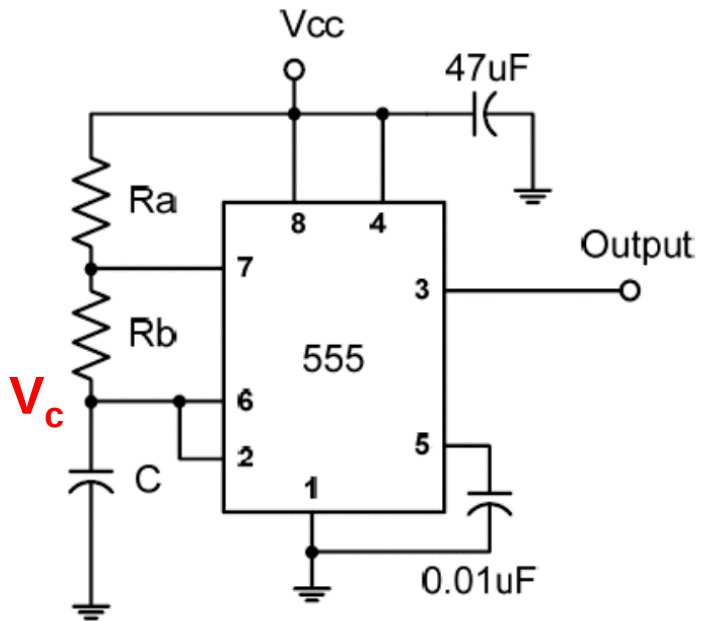

$$t_{high} = 0.693 (R_a + R_b) C$$

$$t_{low} = 0.693 (R_b) C$$



$$T = t_{high} + t_{low}$$

$$f = 1/T = 1.44 / (R_a + 2R_b) C$$

$$D = t_{high} / T = (R_a + R_b) / (R_a + 2R_b)$$

- The timer triggers itself periodically and becomes an oscillator, sending out a train of pulses.
- The duty cycle is always greater than 50%.

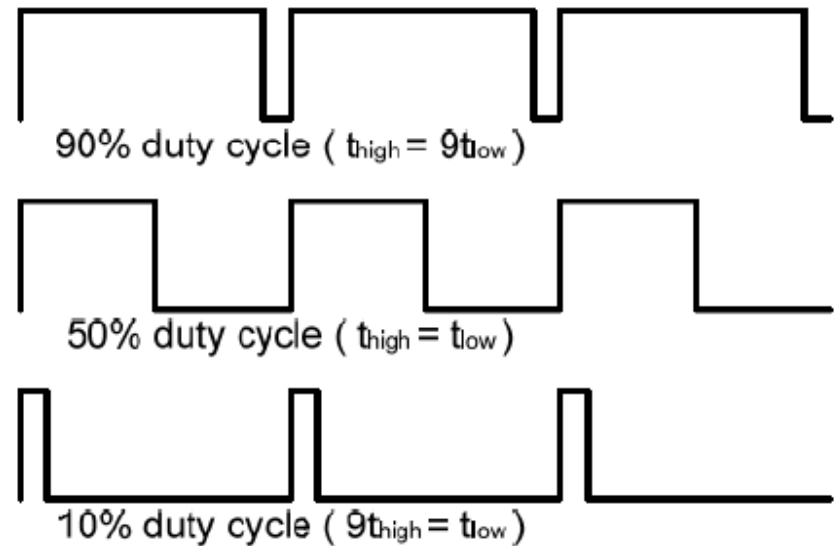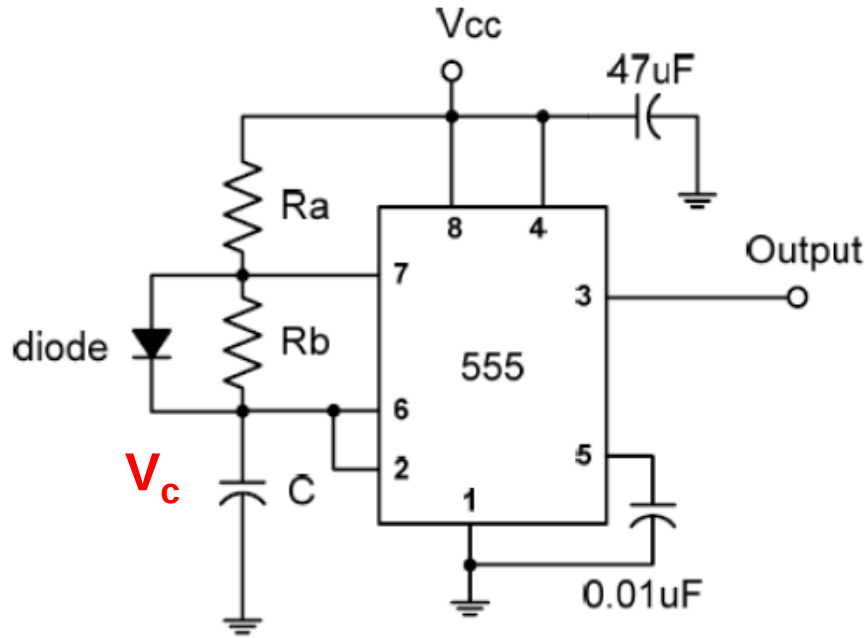3. Astable multivibrator with a diode across R_b




$$t_{high} = 0.693 \times R_a \times C$$

$$t_{low} = 0.693 \times R_b \times C$$

$$D = t_{high}/T = R_a/(R_a + R_b).$$


To achieve a duty cycle of less than 50% or any value, a signal diode can be added in parallel with R_b . This will bypass R_b during the charging period (HIGH) of the cycle.

The voltage divider

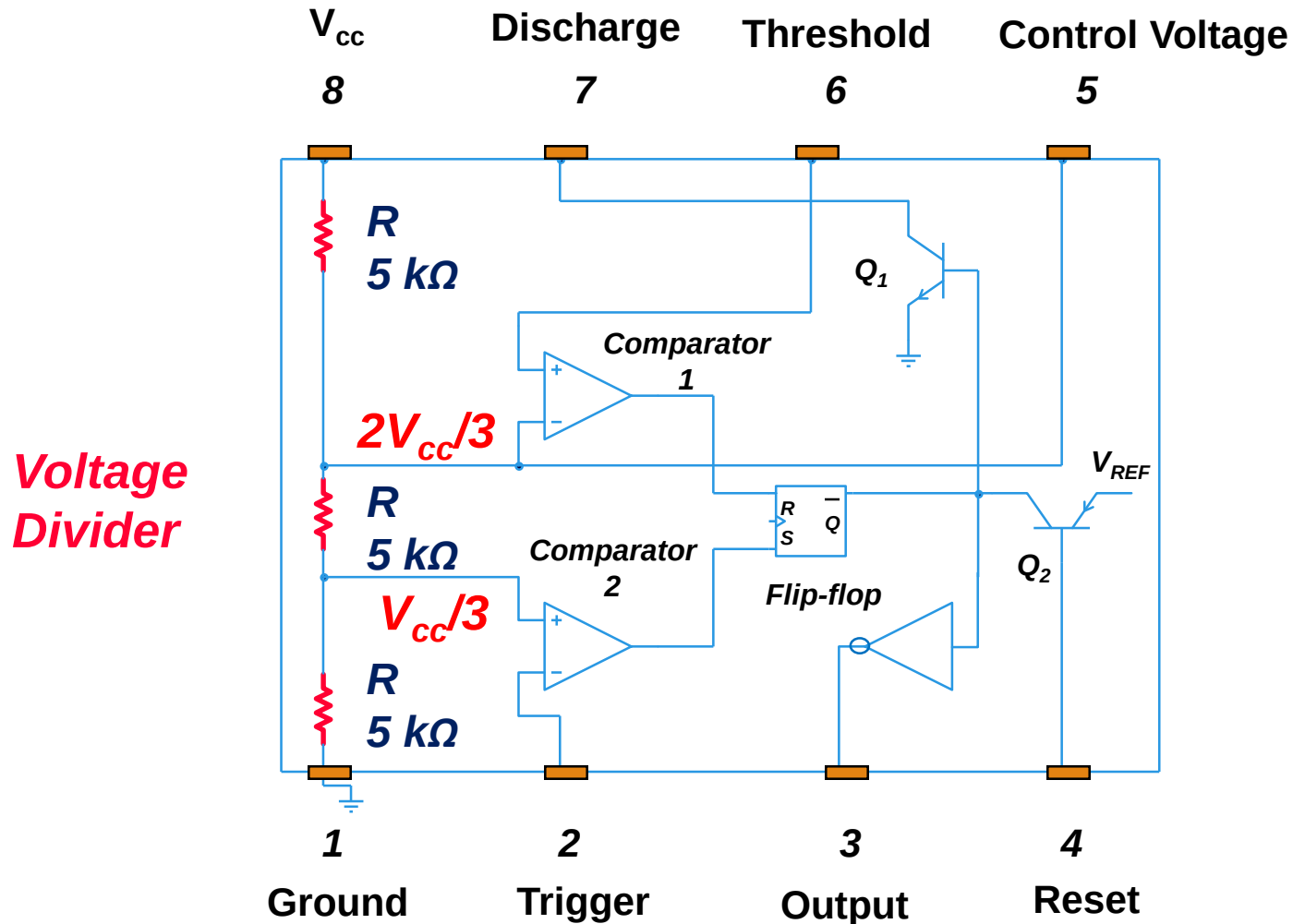


Inside the 555 timer, there is a voltage divider that divides V_{CC} into thirds.

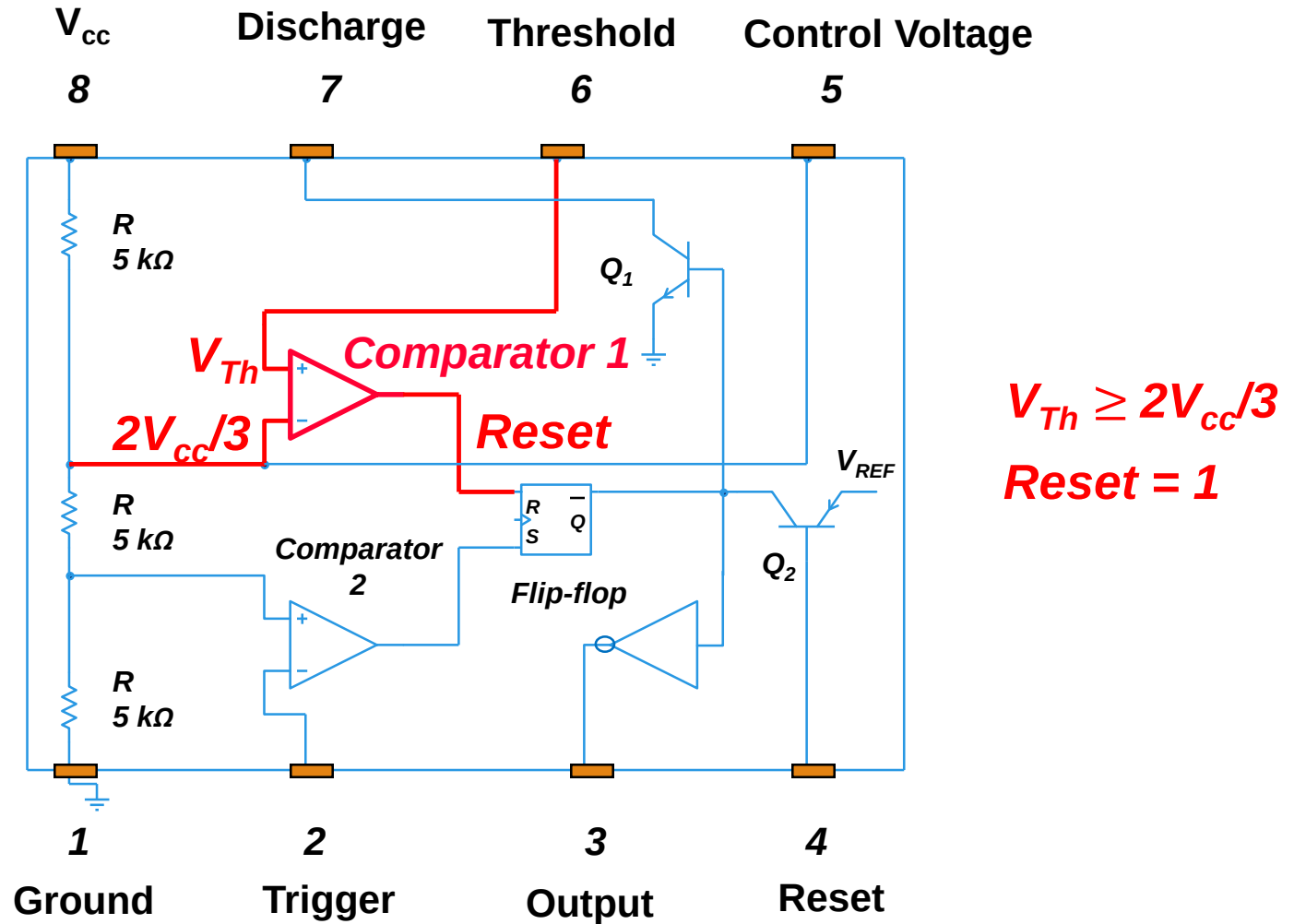Voltage comparator 1 (Threshold vs. $2V_{CC}/3$)




The voltage comparator 1 compares the threshold (pin 6) with $2/3 V_{CC}$.

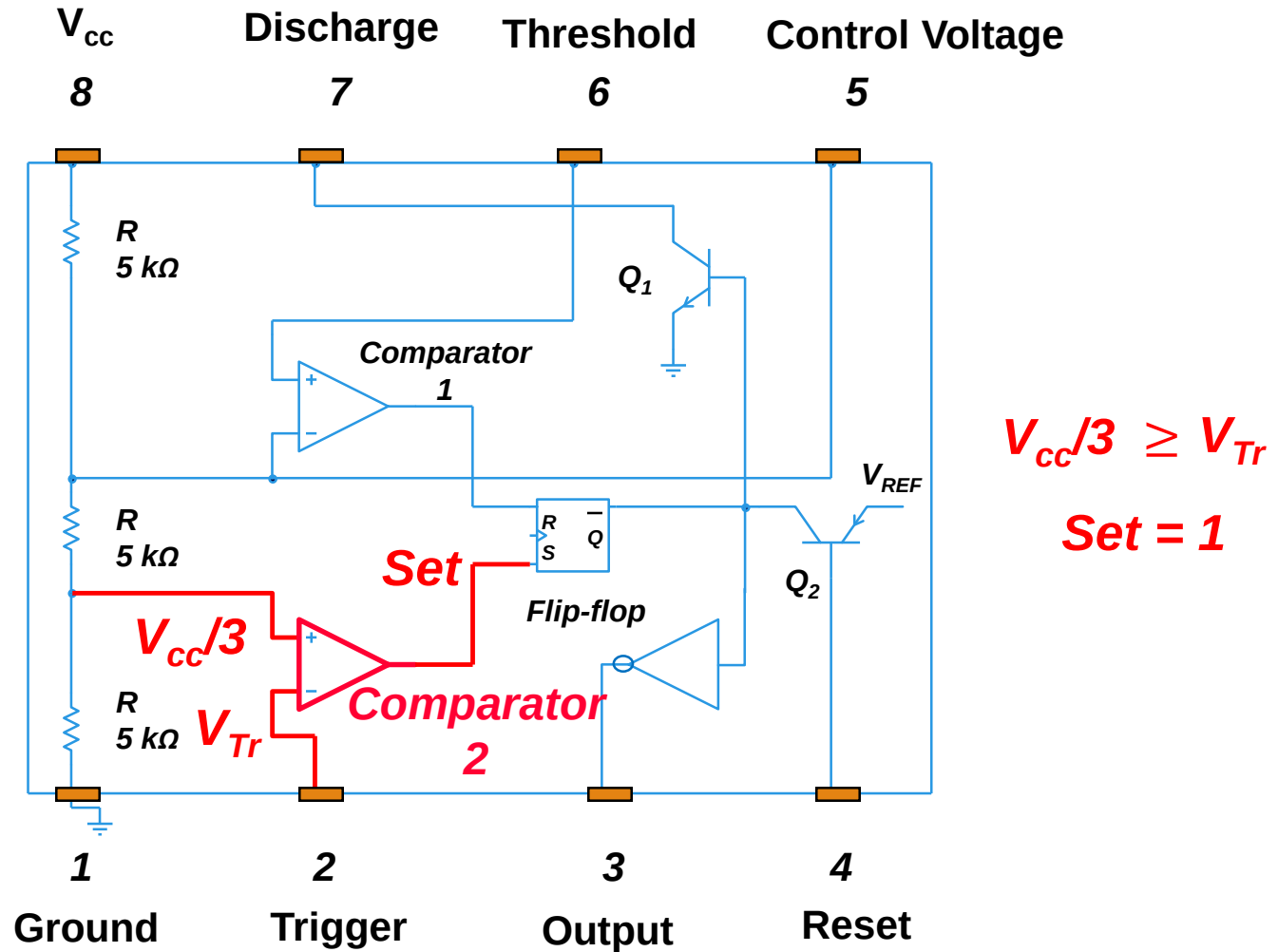Voltage comparator 2 (Trigger vs. $V_{cc}/3$)




The voltage comparator 2 compares $1/3 V_{cc}$ with the trigger input (pin 2).

RS flip-flop

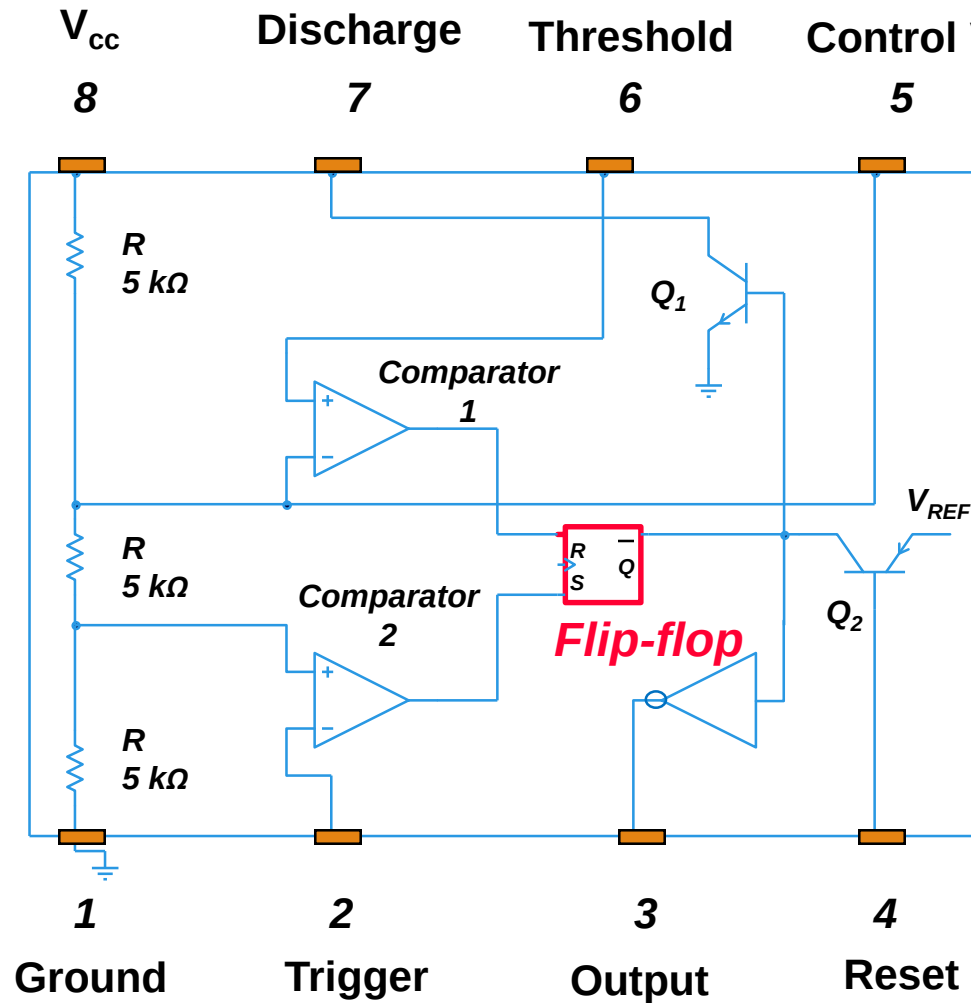


R	S	Q
0	0	No Change
0	1	1 (Set)
1	0	0 (Reset)
1	1	Not Allowed

Inverted-output buffer

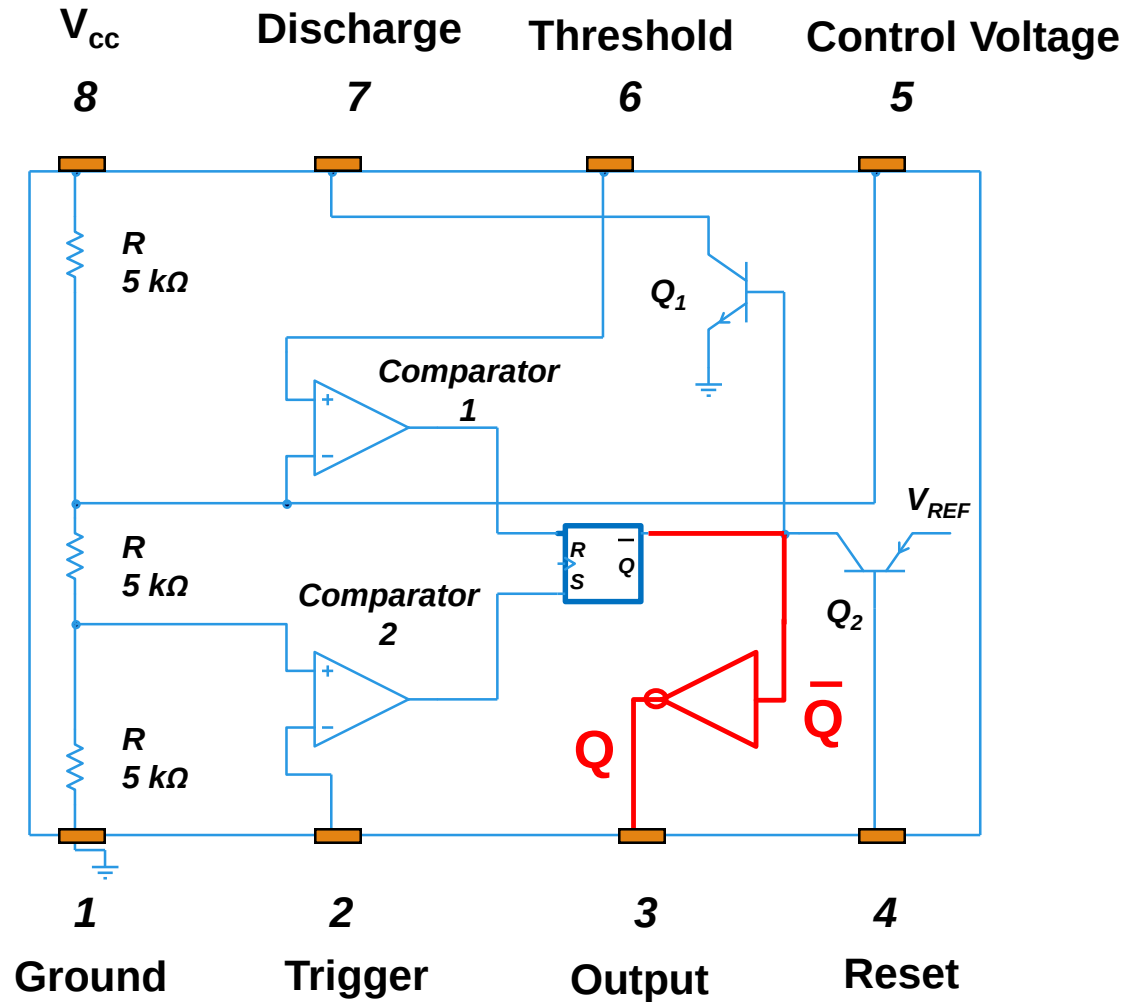


Discharge transistor (Q_1)

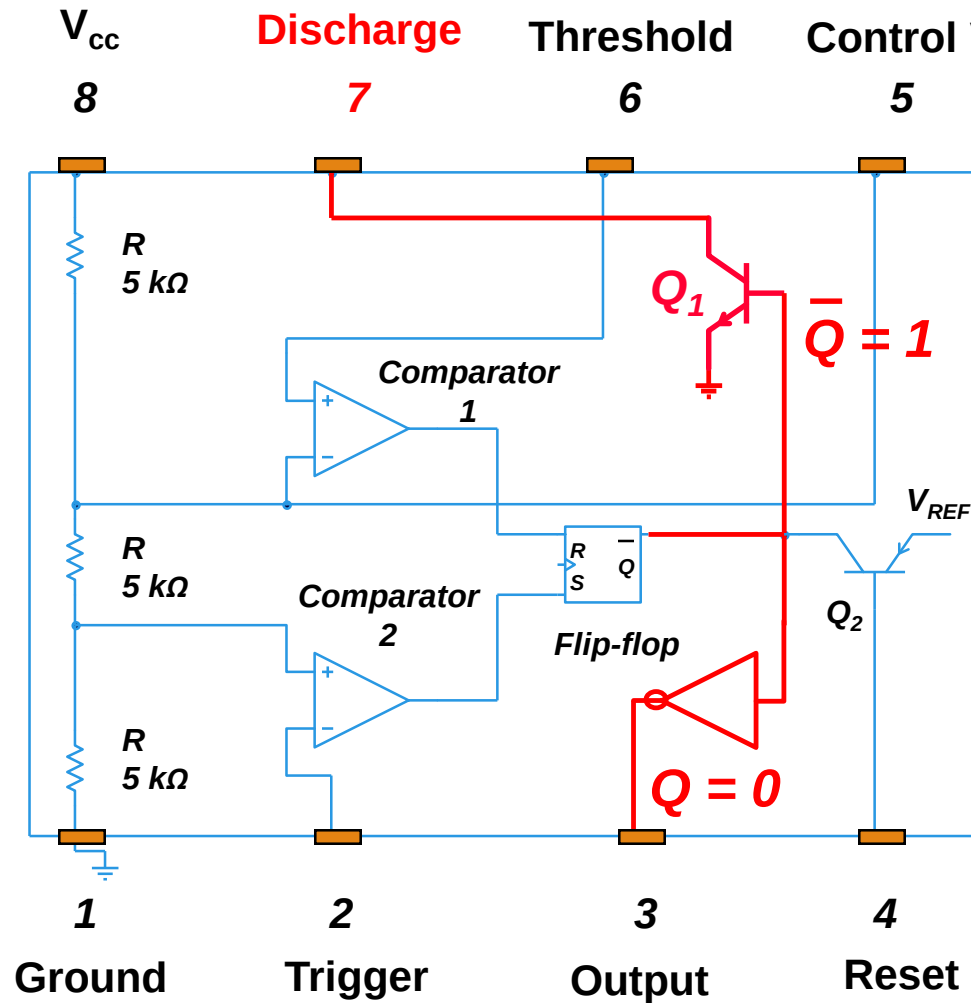


ON when $\bar{Q}$ is HIGH (V_{CC})
➔ Discharge (Output = 0)

OFF when $\bar{Q}$ is LOW (0 V)

Reset Transistor (Q_2)

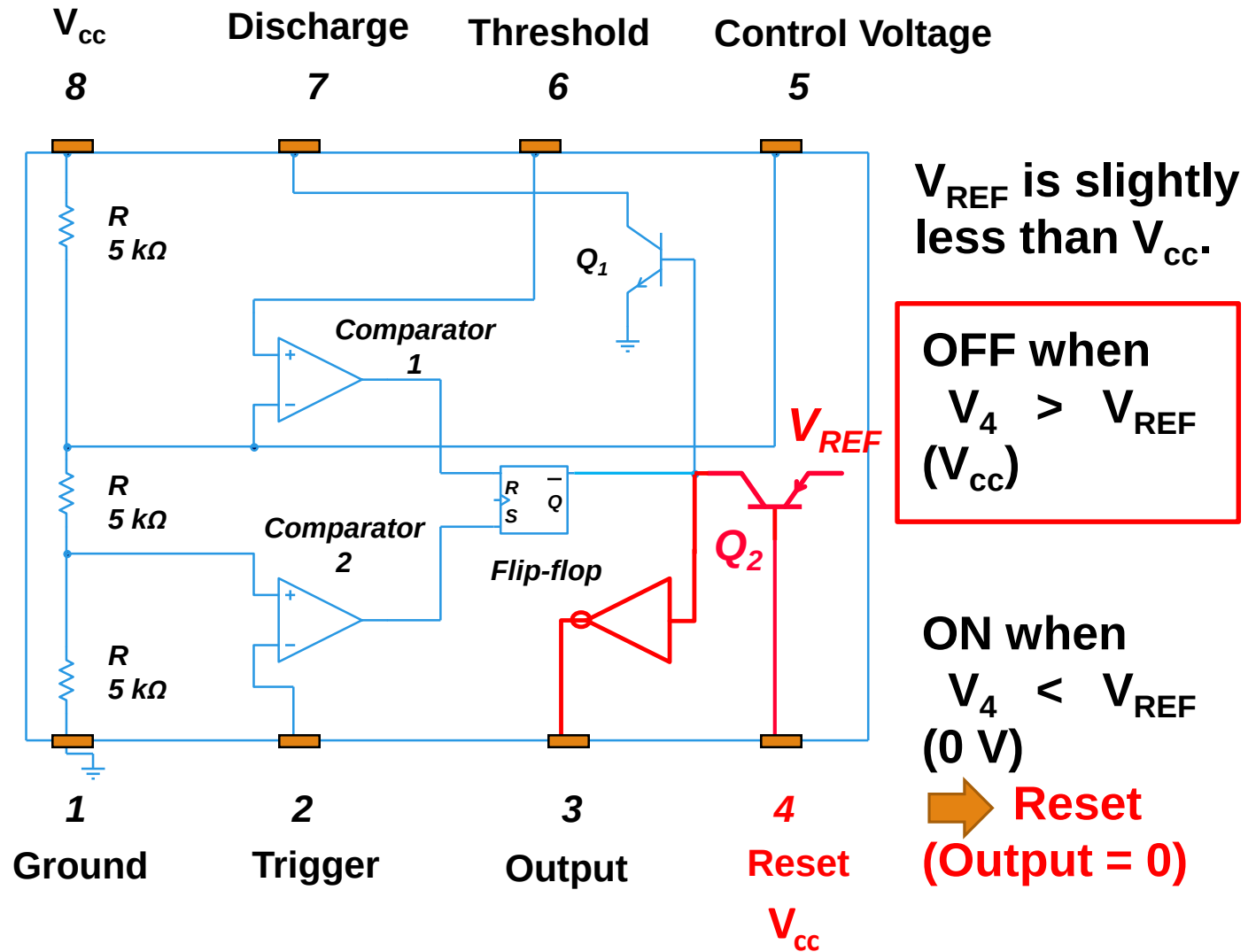



Control voltage

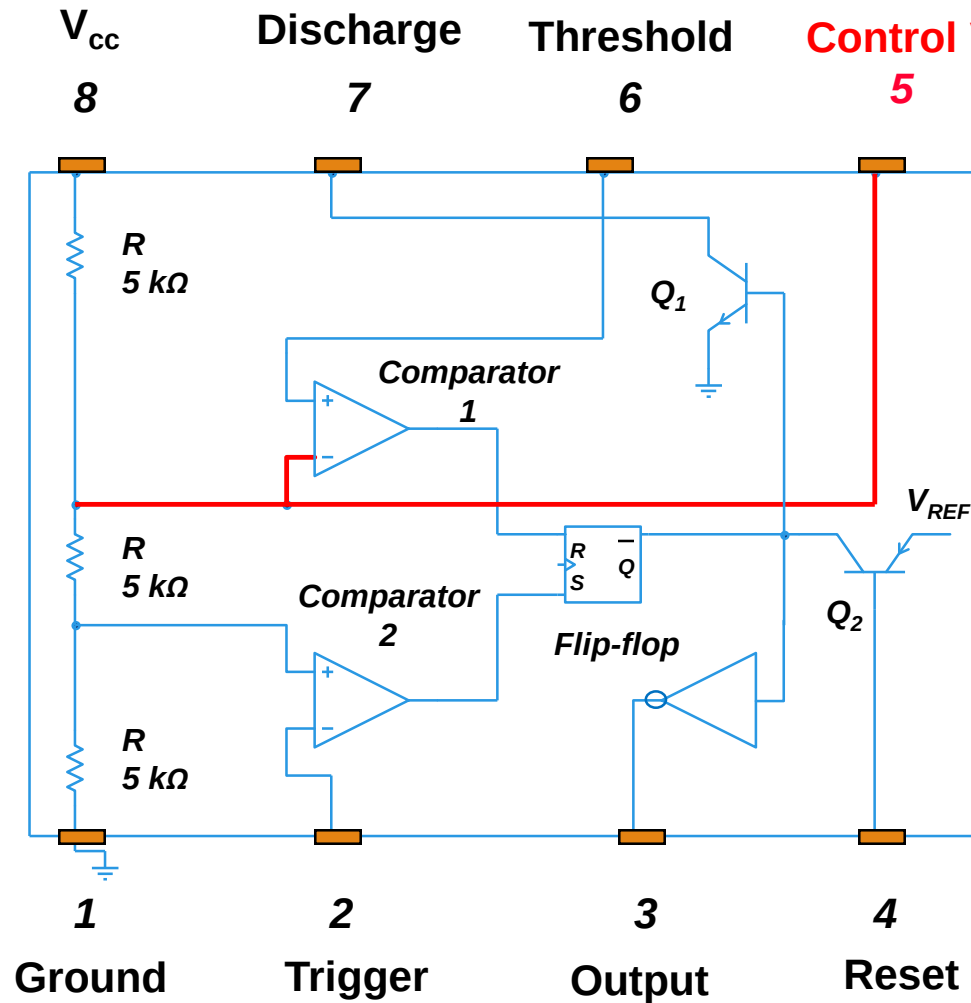

**Control Voltage
is connected to
ground through
a capacitor
if not use.**

**The capacitance of
0.01 μ F is
recommended.**

P1 Monostable multivibrator

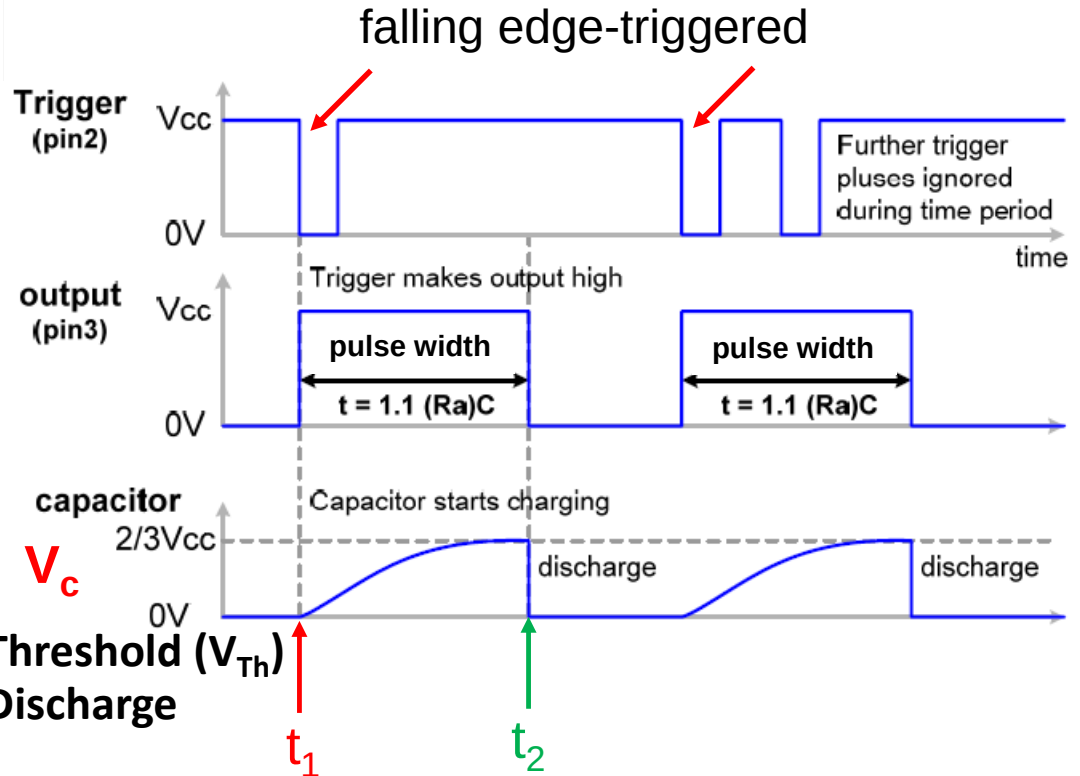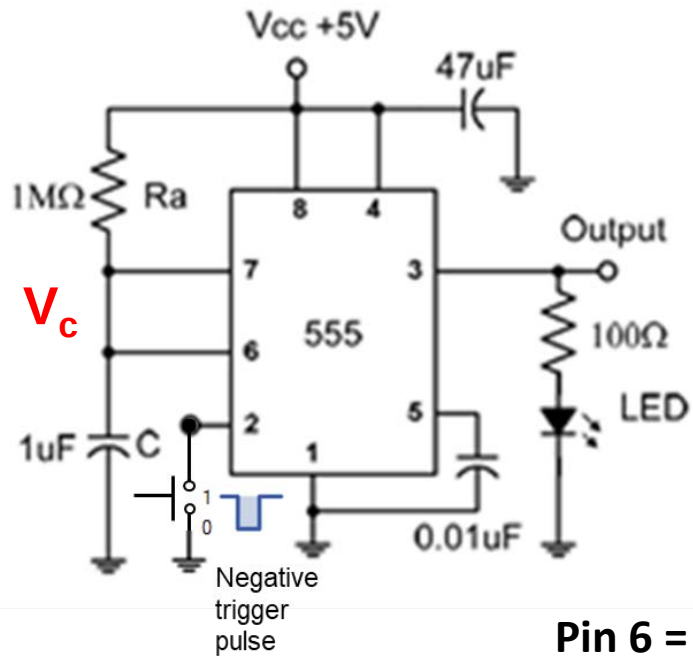

Pin 6 = Threshold (V_{Th})
Pin 7 = Discharge

$$t = t_1:$$

$$V_{Th} < 2V_{cc}/3$$

$$V_{cc}/3 > V_{Tr} (0V)$$

$R = 0, S = 1, Q = 1, \text{Output} = V_{cc}$
 Q_1 is OFF (capacitor charging)

$$t_1 < t < t_2:$$

$$V_{Th} < 2V_{cc}/3$$

$$V_{cc}/3 < V_{Tr} (V_{cc})$$

$R = 0, S = 0, \text{no change}$



$$t = t_2:$$

$$V_{Th} = 2V_{cc}/3$$

$$V_{cc}/3 < V_{Tr} (V_{cc})$$

$R = 1, S = 0, Q = 0, \text{Output} = 0$
 Q_1 is ON (capacitor discharging)

P1 Monostable multivibrator

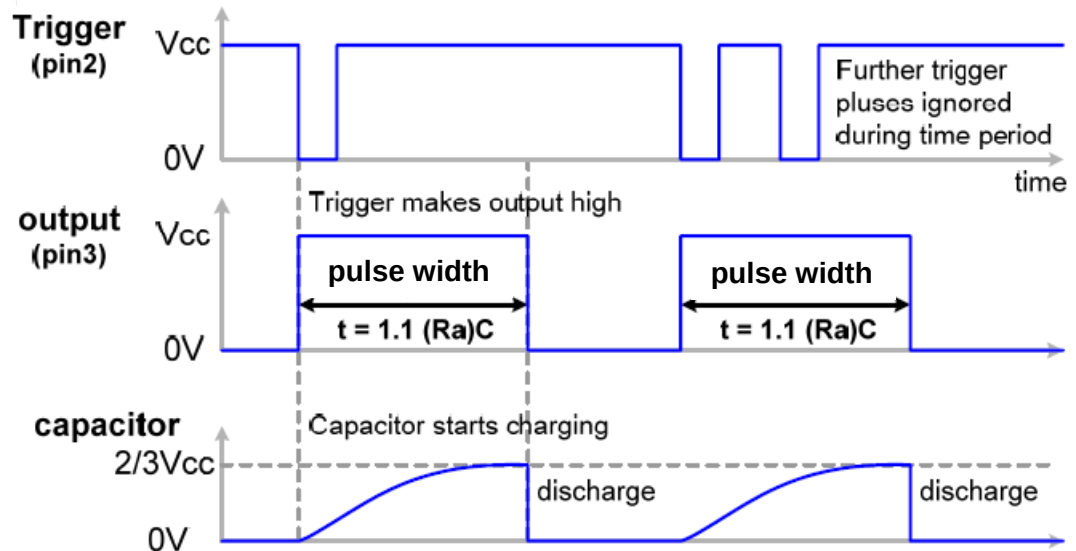
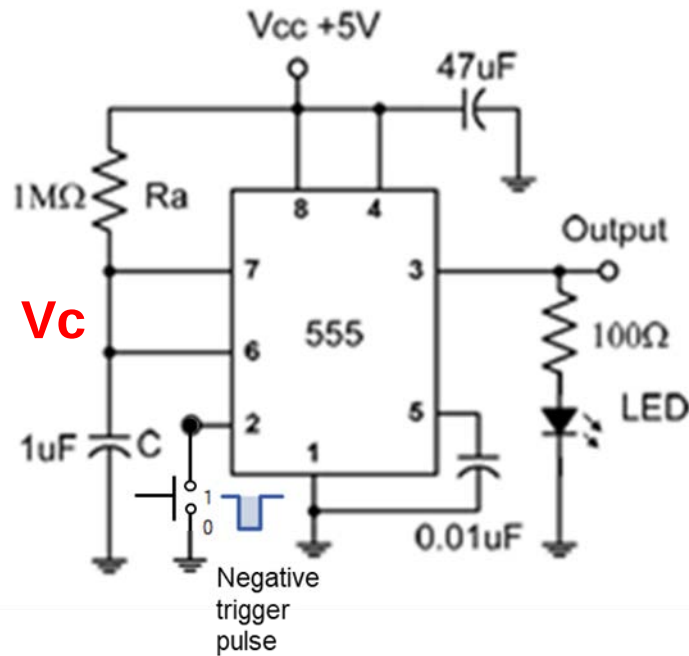


output pulse width: $t = 1.1(R_a)C$

R1 (10 points)

- Sketch the trigger signal, the voltage signal across the capacitor (V_C), and the output signal.
- Measure the output pulse width and compare the result with the theoretical value.
- Observe and describe the LED on/off behavior.

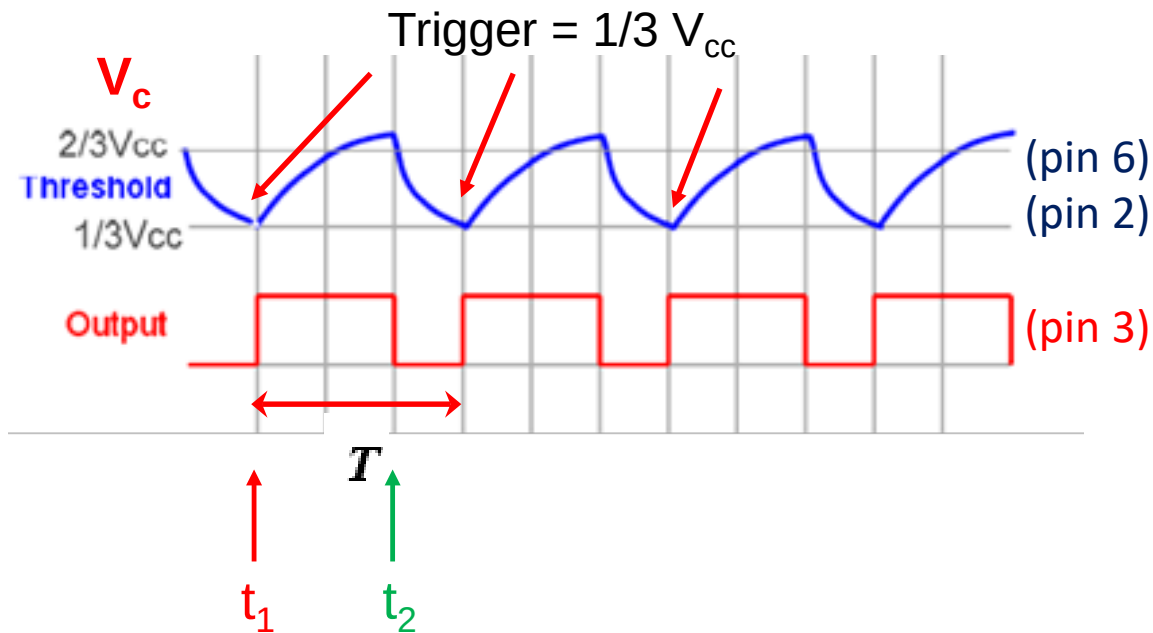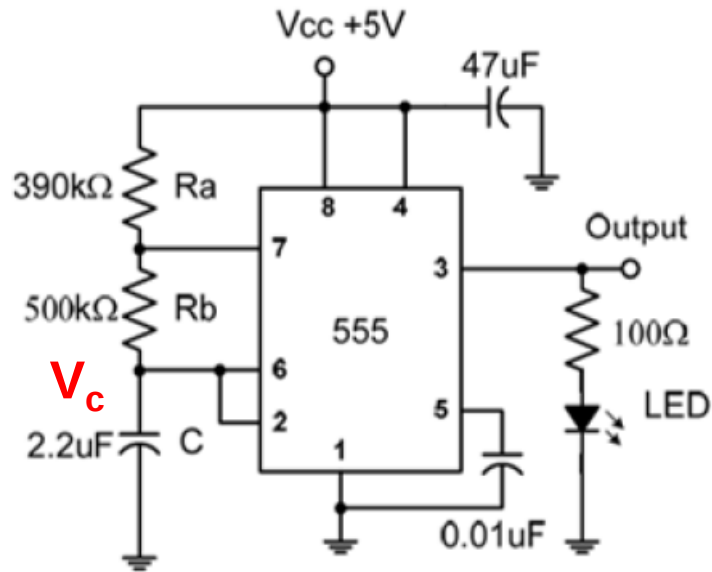P2 Astable multivibrator ($C = 2.2 \mu\text{F}$)



$$t = t_1:$$

$$V_{Th} = V_{Tr} = V_{cc}/3$$

$R = 0, S = 1, Q = 1, \text{Output} = V_{cc}$
 Q_1 is OFF (capacitor charging)

$$t_1 < t < t_2:$$

$$V_{Th} < 2V_{cc}/3$$

$R = 0, S = 0, \text{no change}$



$$V_{cc}/3 < V_{Tr}$$

$$t = t_2:$$

$$V_{Th} = V_{Tr} = 2V_{cc}/3$$

$R = 1, S = 0, Q = 0, \text{Output} = 0$
 Q_1 is ON (capacitor discharging)

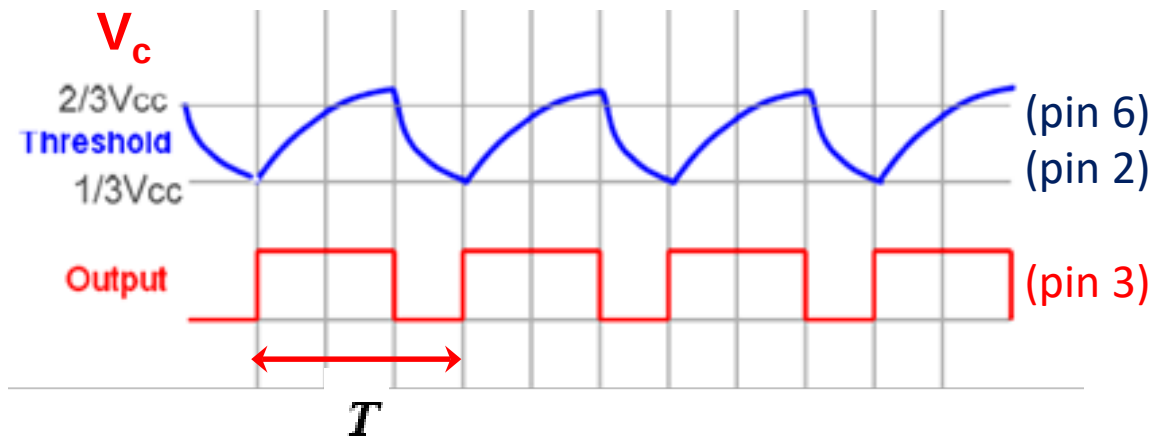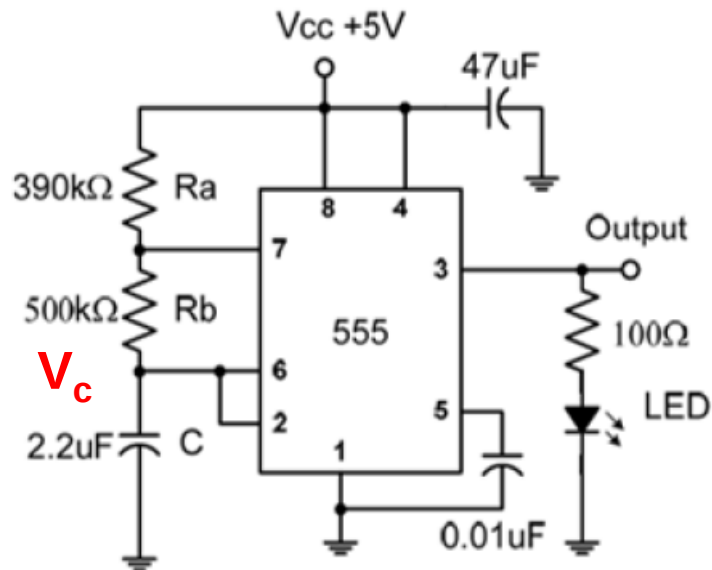P2 Astable multivibrator ($C = 2.2 \mu\text{F}$)



$$t_{high} = 0.693 (R_a + R_b) C$$

$$t_{low} = 0.693 (R_b) C$$

$$T = t_{high} + t_{low}$$



$$f = 1/T = 1.44 / (R_a + 2R_b) C$$

$$D = t_{high}/T = (R_a + R_b) / (R_a + 2R_b)$$

R2 (10 points)

- Sketch the voltage signal across the capacitor (V_c) and the output signal.
- Measure the time intervals for a HIGH output (t_{high}) and a LOW output (t_{low}).
- Determine the duty cycle, the period, and the frequency and compare the results with the theoretical values.
- Observe and describe the LED on/off behavior.

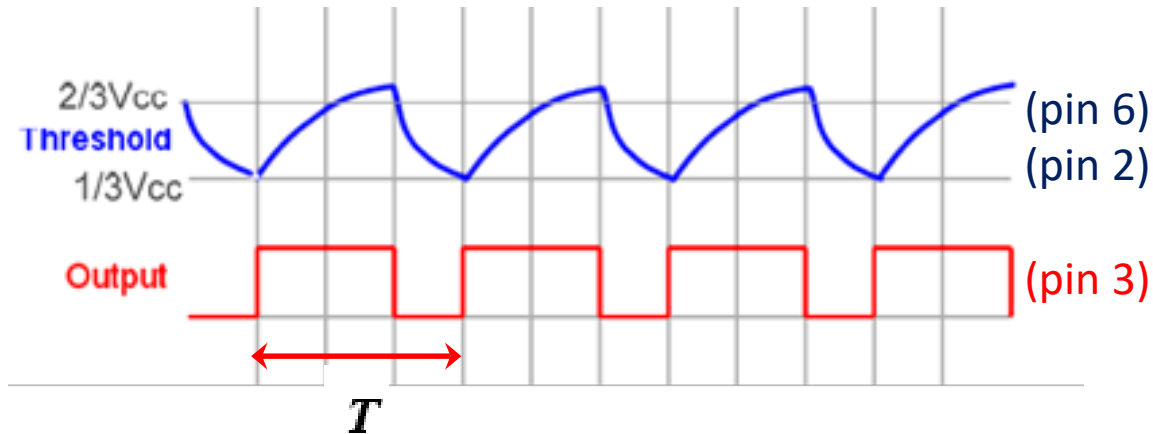
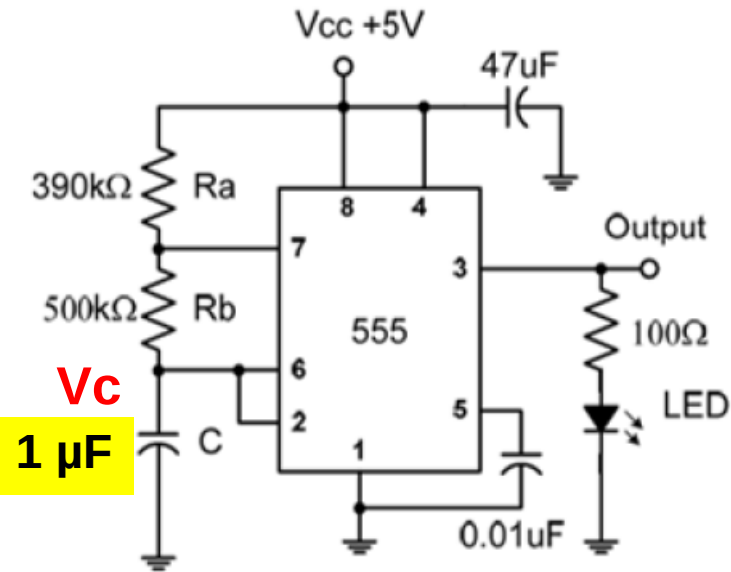
P3 Astable multivibrator ($C = 1 \mu\text{F}$)



R3 (10 points)

- Sketch the voltage signal across the capacitor (V_C) and the output signal.
- Measure the time intervals for a HIGH output (t_{high}) and a LOW output (t_{low}).
- Determine the duty cycle, the period, and the frequency and compare the results with the theoretical values.
- Observe and describe the LED on/off behavior.
- Discuss the experimental results obtained from R2 and R3.

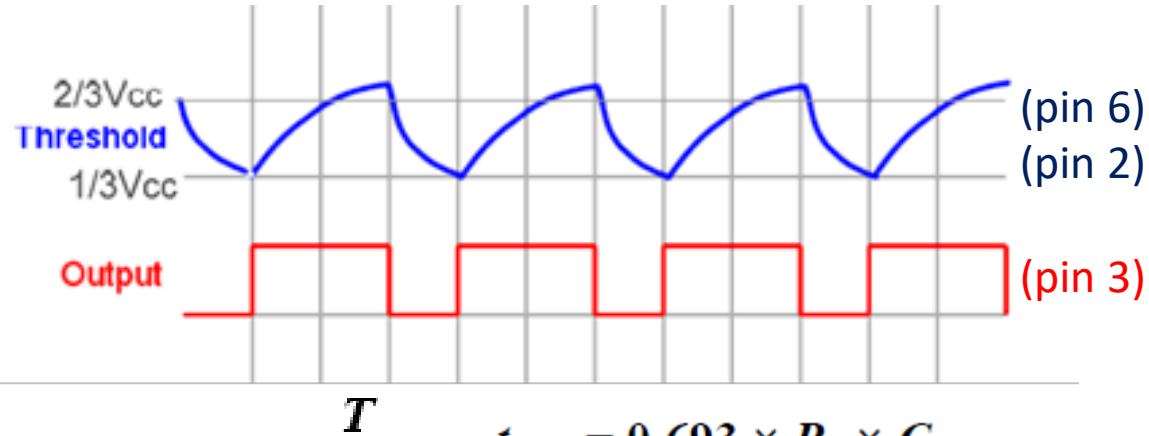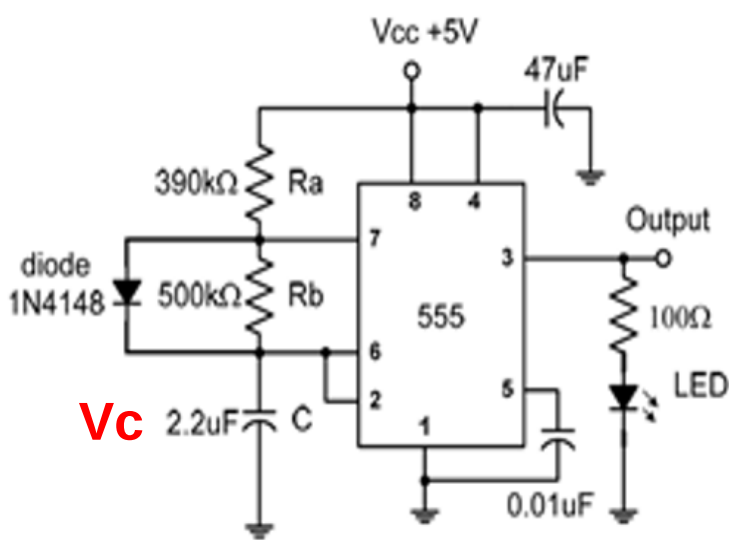P4 Astable multivibrator with a diode across R_b



$$t_{high} = 0.693 \times R_a \times C$$

$$t_{low} = 0.693 \times R_b \times C$$

$$D = t_{high}/T = R_a/(R_a + R_b).$$

R4 (10 points)

- Sketch the voltage signal across the capacitor (V_c) and the output signal.
- Measure the time intervals for a HIGH output (t_{high}) and a LOW output (t_{low}).
- Determine the duty cycle, the period, and the frequency and compare the results with the theoretical values.
- Observe and describe the LED on/off behavior.

Note:

- Use a **10x probe** to measure the voltage across the capacitor C (V_c).
- Make sure that electrolytic capacitors have a correct polarity.

FINAL REPORT

Write a report on how this experiment is performed which should include the followings:

- 1. Describe the operation of each circuit.**
- 2. Discuss the waveforms obtained at each section.**
- 3. Discuss about the results obtained from R2 and R3.**
- 4. Discuss about the results obtained from R2 and R4.**

QUESTIONS

Q1 Describe the difference(s) between a square wave and a rectangular wave.

Q2 Consider the circuit in Figure 11, if we want the LED to be ON for 2 s and OFF for 2 s, what would be the values of the resistors R_a and R_b ?