



EE2-10: T FLIP-FLOP AND A COUNTER CIRCUIT

Kittipitch Meesawat




Four Bits Binary Ripple Counter

(P1) Set the clock signal which is a square wave with 5 Vp-p, 1 Hz.

- ★ Min volt is "0 V", Max volt is "5 V." This can be done using TTL output of the generator, or using offset of the main output.

(P2) Construct a 4-bits ripple counter using JK Flip-flops.

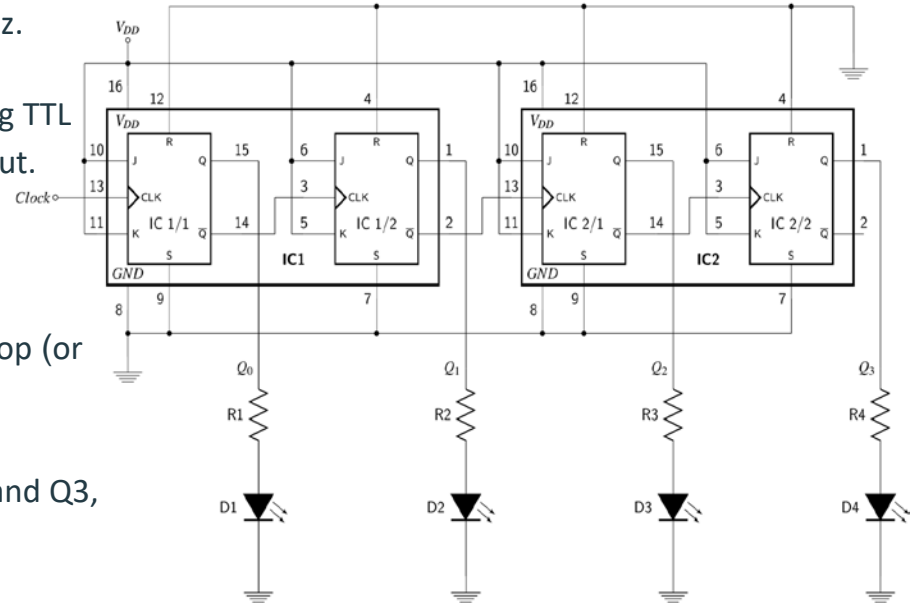
- Make it simple by constructing one flip-flop by one flip-flop (or two by two).
- Test it at each step.
- Drive LEDs with their active output, namely Q0, Q1, Q2, and Q3, through current limit resistors.
- Be careful about the LED polarity, and the resistor value.



Mod-10 Ripple Counter



(P3) Modify the circuit to reset its count whenever the count reaches “10” or $(1010)_2$.

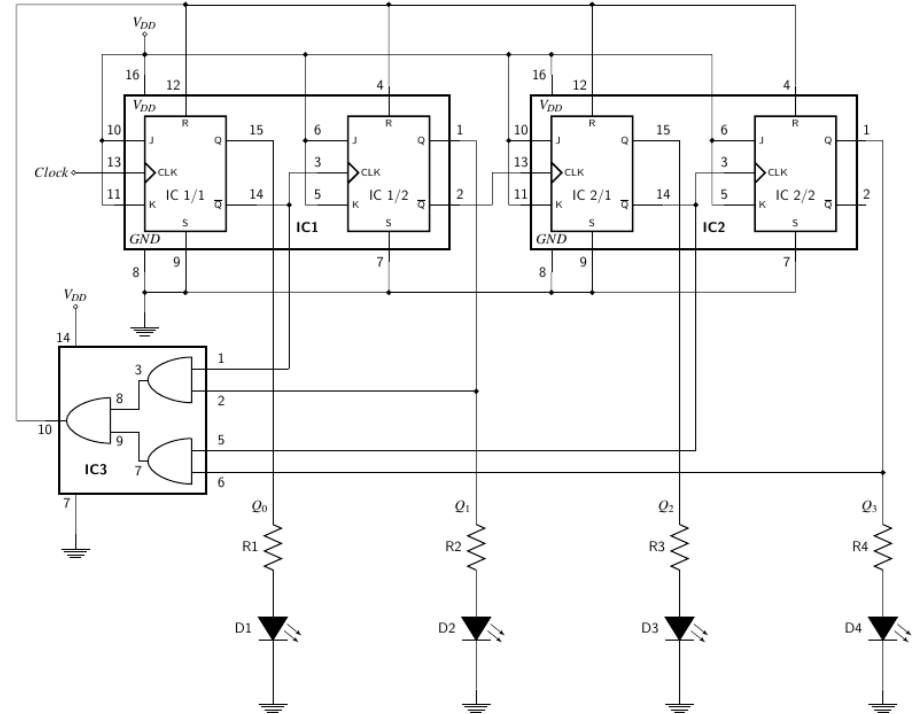- Just add 3 AND gates.
- All AND gates are packed in one IC.
- All connections are not changed except the *Reset* pins of every flip-flop.
- Good planing make this step really fast.




Display counter result with 7-segments LEDs

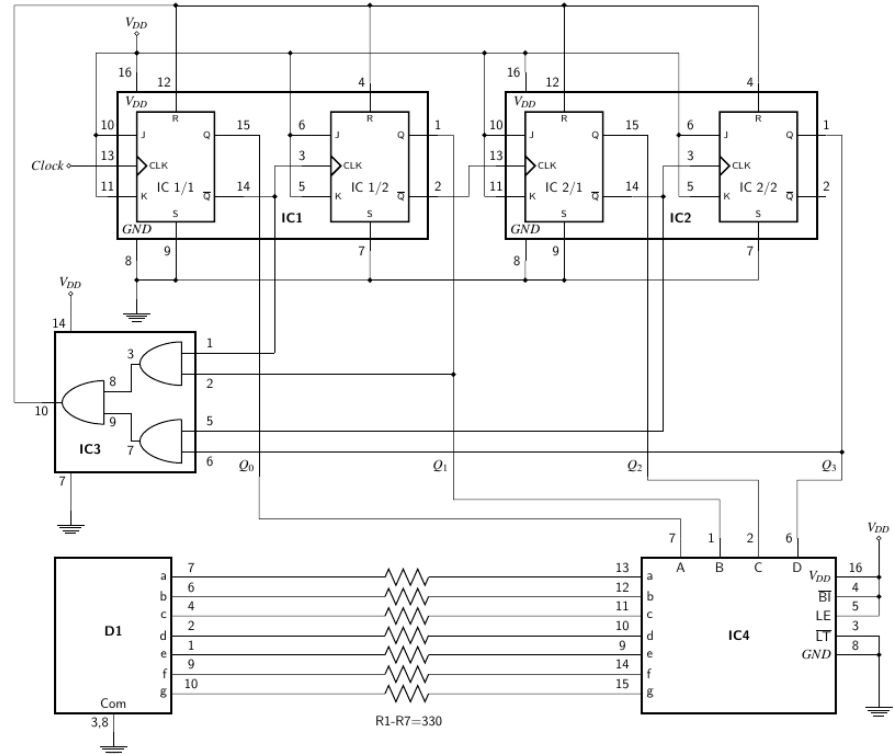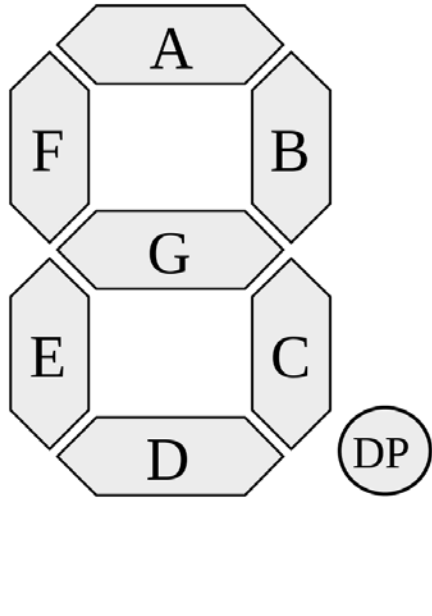(P4) Add the display module to the circuit.
IC4 is a CD4511 and D1 is the 7-segment LEDs.
R1 – R7 are 330-Ω resistors.



Display counter result with 7-segment LEDs

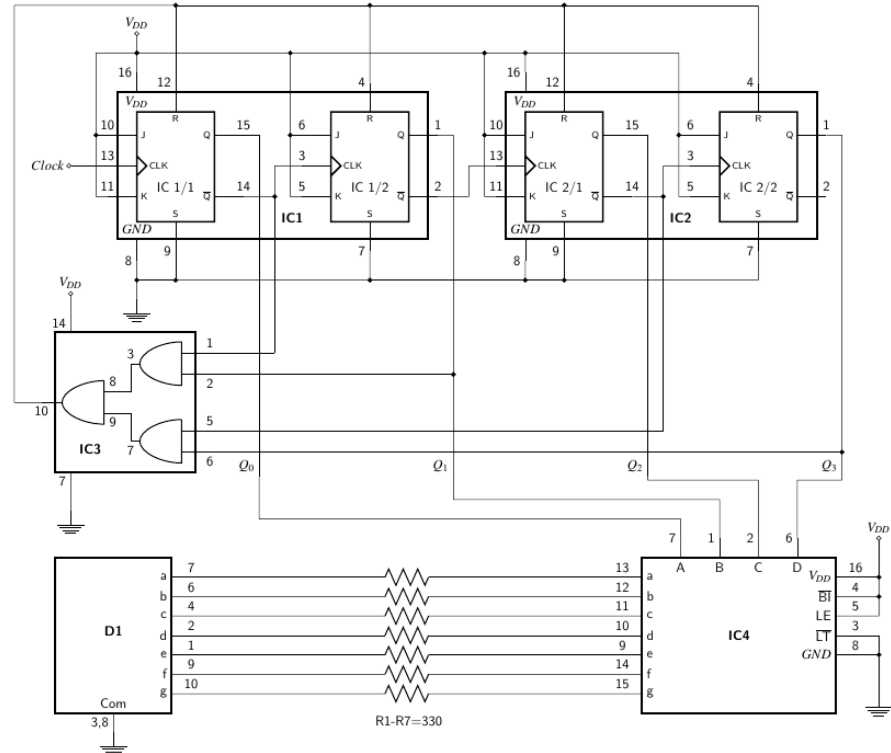
- You can keep your existing 4 LEDs if you like. It could help debugging you circuit, just in case.
- Conceptually, this consists of 2 circuits:
 - The counter
 - The decoder and display
- You can debug these 2 circuits separately.
- You can even construct these two circuits separately.
- Output of the counter is the input of the decoder.



A word from instructor

- Circuits can be considered as a composition of many smaller circuits.
- Build things from small to large.
- Solve problems from easy to difficult.
- Make them modular so debugging will be a lot easier.

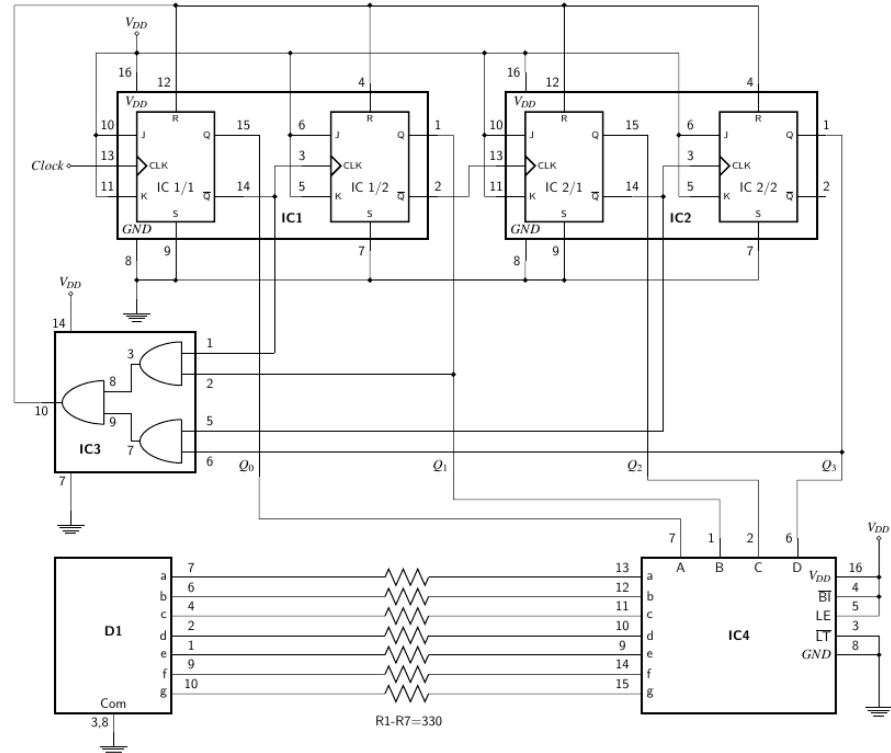The circuit itself is an old fashion. You may not encounter such a circuit in your working life ever. But it is an exercise for modular system which will never be outdated in the engineering world.





Q&A