

A06: รวมเข้าด้วยกัน.

"Whether you think you can, or you think you can't--you're right." — [Henry Ford](#)

เราทำมากันเยอะแล้ว--- สร้าง ALU ไปแล้ว. ตอนนี้, มาสร้างโปรเซสเซอร์ (เวอร์ชันนักเรียน) กันเถอะ.

งานมอบหมายนี้ มีพื้นฐานจากเนื้อหาบท Datapath and Control ของ ตำรา P&H 2nd edition.

จากสถาปัตยกรรม (ชุดคำสั่ง) ที่ให้ตามตารางที่ 1, ส่วนประกอบต่างๆและเส้นทางข้อมูล (datapath) ที่เชื่อมต่อกัน แสดงดังรูปที่ 1. สรุปแต่ละขั้นตอนที่ใช้ในการทำคำสั่งแสดงในตารางที่ 2.

MIPS core instruction	Format	Bits =	m/c code					
			6	5	5	5	5	6
add	add rd, rs, rt		0	rs	rt	rd	0	0x20
subtract	sub rd, rs, rt		0	rs	rt	rd	0	0x22
and	and rd, rs, rt		0	rs	rt	rd	0	0x24
or	or rd, rs, rt		0	rs	rt	rd	0	0x25
set on less than	slt rd, rs, rt		0	rs	rt	rd	0	0x2A
load word	lw rt, addr		0x23	rs	rt	offset		
store word	sw rt, addr		0x2B	rs	rt	offset		
branch on equal	beq rs, rt, label		4	rs	rt	offset		
jump	j target		2	target				

Table 1: an instruction set that we are going to implement a hardware for. Woohoo! sounds fun.

หน้าที่:

1. ศึกษาเนื้อหา Section 5.4 A Multiple-cycle Implementation (P&H 2e).

2. ศึกษาพฤติกรรมการทำงานของแต่ละชิ้นส่วน.

ศึกษาพฤติกรรมการทำงานของแต่ละชิ้นส่วน. สังเกตความสัมพันธ์ระหว่าง เอาต์พุต และ อินพุตของมัน. ศึกษาการทำงานของ state component, เช่น memory.

a) The word ALU.

ลองรัน WordALU_tb และตรวจสอบว่าแต่ละชิ้นส่วนทำงานได้ถูกต้อง.

นักเรียนควรจะได้ waveform ดังแสดงในรูปที่ 2.

ควรฝึกให้เป็นนิสัยในการตรวจสอบผลด้วยมือ เช่น ตรวจสอบว่าการคำนวณทำงานถูกต้องหรือไม่ **ผลลัพธ์**, สัญญาณ **overflow**, และ สัญญาณ **Zero** เป็นไปตามที่คาดไว้หรือไม่.

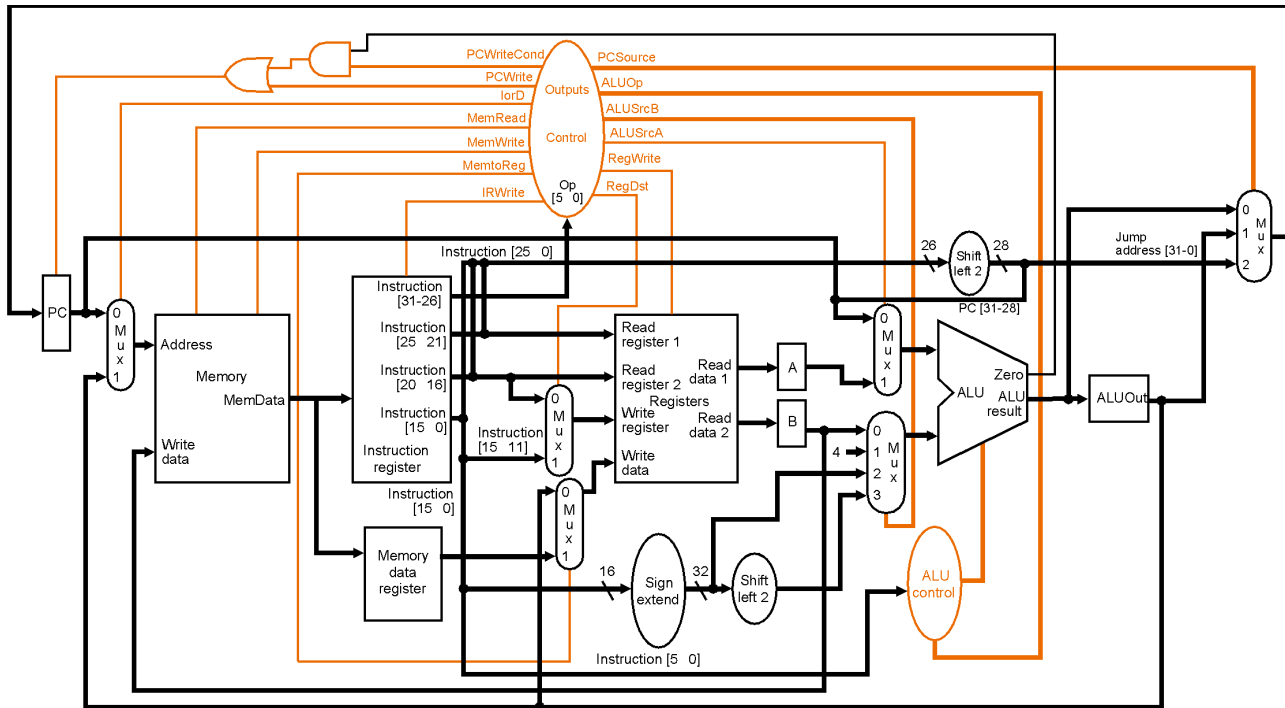


Figure 1: Fig. 5.33 (P&H 2e) The complete datapath for the multicycle implementation of the instruction set shown in Table 1.

Step	Action for R-type instructions	Action for memory-reference instructions	Action for branches	Action for jumps
1	IR <= Memory[PC] PC <= PC + 4 IorD = 0, MemRead, IRWrite ALUSrcA = 0, ALUSrcB = 01, ALUOp = 00, PCSource = 00, PCWrite			
2	A <= Reg[IR[25:21]] B <= Reg[IR[20:16]] ALUOut <= PC + (sign-extend (IR[15:0]) << 2) ALUSrcA = 0, ALUSrcB = 11, ALUOp = 00			
3	ALUOut <= A op B ALUSrcA = 1, ALUSrcB = 00, ALUOp = 10	ALUOut <= A + sign-extend (IR[15:0]) ALUSrcA = 1, ALUSrcB = 10, ALUOp = 00	if (A == B) PC <= ALUOut ALUSrcA = 1, ALUSrcB = 00, ALUOp = 01, PCSource = 01, PCWriteCond	PC <= {PC[31:28],(IR[25:0]),2'b00} PCSource = 10, PCWrite
4	Reg[IR[15:11]] <= ALUOut RegDst = 1, MemtoReg = 0, RegWrite	Load: MDR <= Memory[ALUOut] IorD = 1 MemRead	Store: Memory[ALUOut] <= B IorD = 1 MemWrite	
5		Load:		

		Reg[IR[20:16]] <= MDR RegDst = 0, MemtoReg = 1, RegWrite		
--	--	---	--	--

Table 2: Summary of the steps taken to execute any instruction class with corresponding control signals.

 


Figure 2: Waveform obtained from WordALU_tb.

(b) The register file.

ลองรัน regfile_tb และตรวจสอบการทำงานว่าถูกต้องหรือไม่.

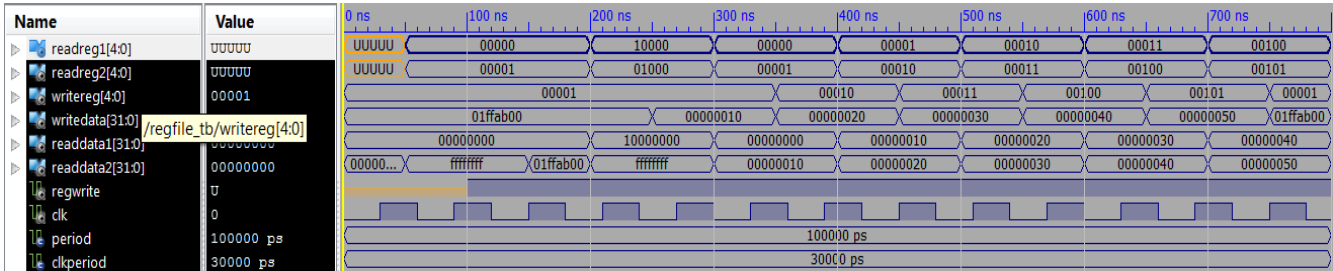


Figure 3: Waveform obtained from regfile_tb.

สังเกตว่า สัญญาณเอาต์พุต **readdata1** และ **readdata2** ตอบสนองทันทีที่สัญญาณ **readreg1** หรือ **readreg 2** มีการเปลี่ยนแปลง. รูปที่ 4 ขยายรูปที่ 3 ออกมาพร้อมทั้งแสดงข้อความอธิบาย

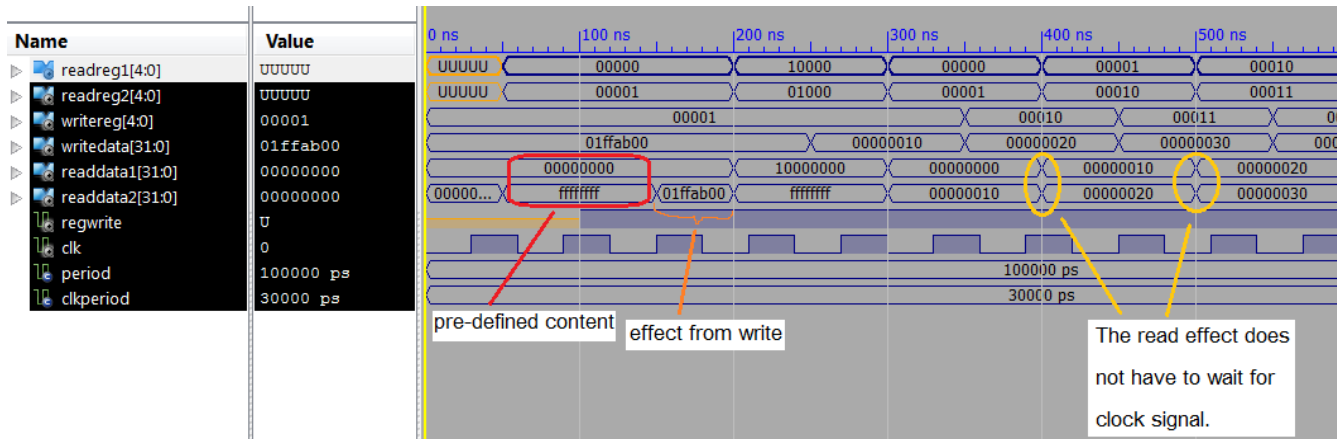


Figure 4: Enlarged version of Figure 3

(c) The one-word registers.

ลองรัน nbitregister_tb และตรวจสอบดูว่ามันทำงานถูกต้อง.

การที่ใส่สัญญาณ **regload** เข้าไป (กรณีนี้ **regload** เป็น '1') จะทำให้ register รับค่าอินพุตเข้าไปและเก็บไว้ จนกระทั่งเกิดการเปลี่ยนแปลงใหม่ (จาก สัญญาณ **regload** หรือ **regclear**).

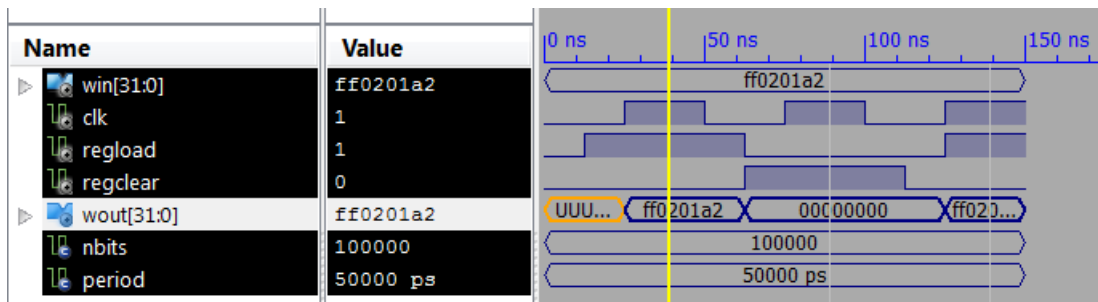


Figure 5: Waveform obtained from nbitregister_tb.

(d) The multiplexors.

(d1) The 2-to-1 multiplexor.

ลองรัน mux2_tb และตรวจสอบการทำงานของ multiplexor (แบบสองเลือกหนึ่ง) ว่าทำงานได้อย่างถูกต้อง.

(ถ้าทำงานถูกต้อง) เอาต์พุตของ multiplexor จะเหมือนกับอินพุต ที่เลือก

 


Figure 6: Waveform obtained from mux2_tb.

(d2) The 4-to-1 multiplexor.

ลองรัน mux4_tb และตรวจสอบการทำงานของ multiplexor (แบบสี่เลือกหนึ่ง) ว่าทำงานได้ถูกต้อง.

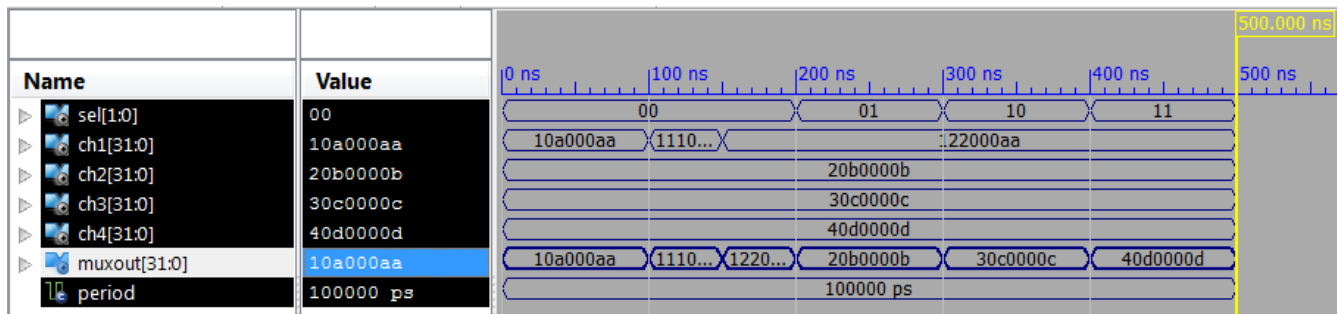


Figure 7: Waveform obtained from mux4_tb.

(e) The sign extension unit.

ลองรัน signextend_tb และตรวจสอบดูว่าทำงานถูกต้องหรือไม่.

 


Figure 8: Waveform obtained from signextend_tb.

(f) The memory unit.

ลองรัน ch5mem_tb และตรวจสอบดูว่ามันทำงานถูกต้อง.

ตัว program segment จะมีการโหลดคำสั่งเข้าไปเมื่อ สัญญาณ startup เป็น '1'. ที่แอดเดรส 0x10000000 และ 0x10000004, หน่วยความจำ (memory) จะมีข้อมูลอยู่ (ถูกโหลดเข้าไปตอนสัญญาณ startup เป็น '1'). ข้อมูลในหน่วยความจำสามารถจะถูกเขียนใหม่หรือแก้ไขได้โดยใส่ ค่าใหม่ไปที่พอร์ต data, ดังแสดงในรูปที่ 9 ระหว่างช่วงเวลา 120 ถึง 160 ns. ผลของการเขียนข้อมูลเข้าไปใหม่จะเห็นตอนที่อ่านข้อมูลออกมา, ดังแสดง ที่ค่า q ในรูป ระหว่างเวลา 170 to 210 ns. สังเกตว่าแอดเดรสของหน่วยความจำที่แอดเดรส 00400000, 00400004, 00400008

และ 0040000C จะเก็บไปบนารีที่แปลเป็น machine codes ของคำสั่ง lw \$t0, 0(\$s0), lw \$t1, 4(\$s0), slt \$t2, \$t0, \$t1, และ beq \$t2, 3 ตามลำดับ.

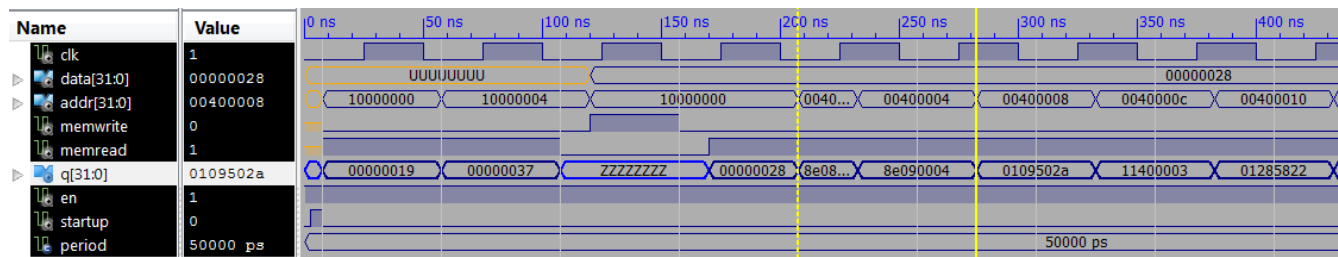


Figure 9: Waveform obtained from ch5mem_tb.

คำถาม:

* f1. ใน write mode, หน่วยความจำนี้ทำงานที่ rising หรือ falling clock edge?

* f2. คุณจะออกแบบการทดลองอย่างไรเพื่อยืนยันว่า คำตอบของคุณในข้อ f1 ถูกต้อง?

* f3. เขียนโค้ด VHDL สร้าง test bench เพื่อทำซิมูเลชัน และสร้าง waveform สนับสนุนคำตอบของคุณ.

(g) ALU control unit.

ตัว ALU control unit ทำหน้าที่ สร้างสัญญาณ operations, Binvert และ CarryIn สำหรับ ALU ตามสัญญาณ ALUop และ instruction bits จาก funct field (ดูตารางที่ 3). แนวคิดคือ แทนที่จะให้ ตัว main control ทำทุกอย่าง, เราจะมอบ หน้าที่การสร้างสัญญาณควบคุม ALU ไปให้กับ ALU control unit. วิธีนี้จะทำให้วงจร main control ซับซ้อนน้อยลง และ ทำให้การทำงานของ main control มีประสิทธิภาพมากขึ้น (สุดท้ายจะทำให้ CPU มีประสิทธิภาพมากขึ้น).

Instruction	m/c code						binary				
	6	5	5	5	5	6	ALUop	funct field	Desired ALU action	ALU control input (Binvert, ALU operation)	CarryIn of LSB
lw rt, addr	0x23	rs	rt	offset			00	xx xxxx	add	010	0
sw rt, addr	0x2B	rs	rt	offset			00	xx xxxx	add	010	0
beq rs, rt, label	4	rs	rt	offset			01	xx xxxx	subtract	110	1
add rd, rs, rt	0	rs	rt	rd	0	0x20	10	10 0000	add	010	0
sub rd, rs, rt	0	rs	rt	rd	0	0x22	10	10 0010	subtract	110	1
and rd, rs, rt	0	rs	rt	rd	0	0x24	10	10 0100	and	000	0
or rd, rs, rt	0	rs	rt	rd	0	0x25	10	10 0101	or	001	0

slt rd, rs, rt	0	rs	rt	rd	0	0x2A	10	10 1010	set on less than	111	1
----------------	---	----	----	----	---	------	----	---------	------------------	-----	---

Table 3 (Adapted from Fig 5.14 of P&H 2e): How the ALU control bits are set depends on the ALUop control bits and the different function codes for the R-type instruction. A value of "xxxxxx" means that we "don't care" about the value of the function code.

คำถาม:

g1. สัญญาณอะไรบ้างเป็นอินพุตของ ALU control unit?

g2. สัญญาณอะไรบ้างเป็นเอาต์พุตของ ALU control unit?

g3. สมมติว่า คำสั่ง เป็น r-type (ALUop = "10"), เติมตารางข้างล่างนี้ให้สมบูรณ์.

ALUop		Funcnt field						specific instr.	Binvert	ALU operation (2 bits)	CarryIn of LSB
ALUop1	ALUop2	F5	F4	F3	F2	F1	F0				
1	0	1	0	0	0	0	0	add	0	10	0
1	0	1	0	0	0	1	0	subtract	1	10	1
1	0	1	0	0	1	0	0				
1	0	1	0	0	1	0	1				
1	0	1	0	1	0	1	0				

Since the ALUop does not use the encoding 11, either value x1 or 1x would not be ambiguous.

g4. เขียน boolean expressions สำหรับตัวแปรเหล่านี้:

Binvert = _____
 ALU operation(1) = _____
 ALU operation(0) = _____
 CarryIn_LSB = _____

g5. ลองรัน ALUControl_tb และตรวจสอบดูว่า ALU Control Unit ทำงานถูกต้อง.

 


Figure 10: Waveform obtained from ALUControl_tb.

***Bonus* g6.** Propose the alternative architecture of the ALU control to the given architecture (ALUControl process in datapath.vhd).

[Yes, there are alternatives to the given code. For example, you can use the boolean expressions in g4 with a multiplexor to define structural architecture of the ALU.]

***Bonus* g7.** Write VHDL code to implement your proposal and make a test bench to verify its functionality.

***Bonus* g8.** Discuss pros and cons of your proposal comparing to the given architecture.

(h) The main control unit.

Questions:

h1. จาก datapath ในรูปที่ 1, สัญญาณอะไรบ้างที่เป็นอินพุตของ main control unit?

h2. จาก datapath ในรูปที่ 1, สัญญาณอะไรบ้างที่เป็นเอาต์พุตของ main control unit?

h3. จากสรุปของขั้นตอนการทำคำสั่ง ในตารางที่ 2, เติมตารางตรรกะของ main control ข้างล่างให้สมบูรณ์:

step	instr.	opcode	PCWrite Cond	PCWrite	lorD	Mem Read	Mem Write	Mem toReg	IRWrite	PCSource	ALU Op	ALU SrcB	ALU SrcA	Reg Write	RegDst	
1	all	'xxxxxx	0	1	0	1	0	x	1	'00	'00	'01	0	0	x	
2	all	'xxxxxx	0	0	x	0	0	x	0	'xx	'00	'11	0	0	x	
3	r-type	'000000	0	0	x	0	0	x	0	'xx	'10	'00	1	0	x	
3	lw/sw	'10x011														
3	beq	'000100														
3	j	'000010														
4	r-type	'000000														
4	lw	'100011														
4	sw	'101011														
5	lw	'100011														

'x' (don't care) represents the logic whose value does not affect the processor functionality. All asserting signals are assumed to be active on '1'.

***bonus* h4.** How do we implement keep track of the step shown in the table of question h3? (What component do we need? And, how many bits? Draw a diagram illustrating your idea.)

h5. Run maincontrol_tb and verify that the component works correctly.

Check all control signals.

What are signals stagein and stageout for?

 


Figure 11: Waveform obtained from `maincontrol_tb`. The waveform here should be conformed to summary of control signals shown in Table 2. Stage 000 is added to add starting-up capability such that the PC will be loaded with `0x00400000` for starting address. The PCSource multiplexor (in Fig. 5.33 P&H 2e) is implemented with a 4-to-1 multiplexor and the starting address `0x00400000` is mounted at "11" position.

***bonus* h6. Propose the alternative architecture of the main control to the given architecture (MainControl process in `maincontrol.vhd`).**

3. Examine how these components work together in each instruction class.

3.1) Examine simulation results of `Ch5path_tb.vhd`.

The signals shown in the waveform viewer reveal data flow and timing of control signals.

A memory preloaded program to calculate an absolute value of difference between two numbers is shown below.

The program is:

```

lw $t0, 0($s0)
lw $t1, 4($s0)
slt $t2, $t0, $t1
beq $t2, $zero, LAB_t1ELTt0
sub $t3, $t1, $t0
j LAB_SAVE
LAB_t1ELTt0:
sub $t3, $t0, $t1
LAB_SAVE:
sw $t3, 8($s0)
lw $t0, 8($s0) # to check if it is well-saved in memory

```

and it is hard-coded in `ch5mem.vhd` from address `0x00400000`, which is the MIPS starting address for instructions.

You are encourage to familiarize this program with SPIM. (I, myself, use QtSPIM in development of the program.) It should be noted that the different starting address of the program may lead to different machine code, especially the machine code for an instruction with absolute addressing mode, e.g. jump (j).

The data flow of execution of instructions (1) `lw $t0, 0($s0)`, (2) `slt $t2, $t0, $t1`, (3) `beq $t2, $zero, LAB_t1ELTt0`, (4) `j LAB_SAVE`, and (5) `sw $t3, 8($s0)` are shown in Fig. 10 to 14, respectively. These five instructions are picked from instructions coded for the absolute difference calculation program such that each represents different instruction class.

Questions based on Fig. 5.33 (P&H 2e) and Table 2.

3.1.1) Given the PC content is 0x00400000 at stage 1 of any execution, what is the value at the address port of the memory at stage 1?

3.1.2) According to 3.1.1, what content of the PC will be at the end of stage 2?

3.1.3) Suppose the memory contains data as shown in the table below, after fetch and decode an instruction of the address 0x00400000, what value does the Instruction Register (IR) contain?

Address	Data
0x00400000	0x00
0x00400001	0x00
0x00400002	0x08
0x00400003	0x8e
:	:

3.1.4) According to 3.1.3, if the content of the IR is a valid MIPS instruction, what instruction is it?

! recommended bonus ! 3.1.5) Suppose we are to change the functionality of lw/sw instruction so that the offset field refers to a word, not a byte. This will free us from a tedious task of multiplying an index by 4, every time we want to go by word. It sounds good, right? How will you do it?

To have it more fun, you are allowed to change only the datapath, but leave all control signals untouched. No new component is allowed.

(You are pretty much left with options of re-routing signal or signals.)

What would you do?

[Hint: the answer may be much simpler than you think. Now you are forced to think about datapath.]

 


Figure 12: Waveform obtained from Ch5path_tb.vhd showing signal dynamic of the lw instruction. The second signal from top is **stagein32** indicating which stage the execution is going on. The **pcout** indicates the current value of the PC. The **memdatain**, **memdataout**, and **memaddress** indicate data obtained from the memory, data candidate to put in the memory, and the memory address, respectively. The **irout** indicates the current value of the instruction register (IR). The **readreg1**, **readreg2**, **writereg**, **writedata**, **readdata1**, and **readdata2** are index and data ports of the register file. The **aout**, **bout**, and **aluoutput** indicate current values of registers A, B, and ALUOut respectively. The **mdrou** indicates the current content of register MDR. The **pload** is a signal enabling overwrite of PC content. [VHDL: pload <= PCWrite or (PCWriteCond and Zero).] The **regwrite**, **memwrite**, and **memread** are signals controlling writing a content of the register file, writing a content of the memory, and reading a content of the memory, respectively. It should be noted that there are more control signals that are not shown here.

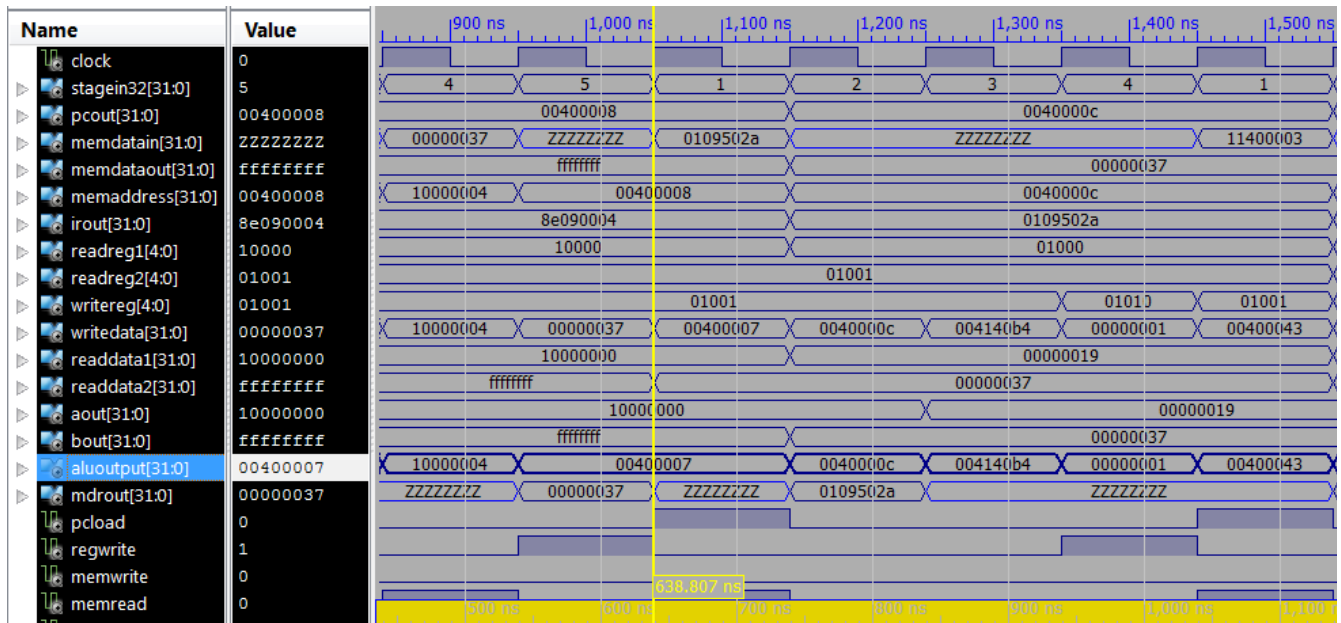


Figure 13: Data flow of the execution of `slt` instruction. The yellow line marks the beginning of the execution. In stage 1, instruction is fetched from the memory. The value is at `memdatain`. After stage 1, PC and IR values are updated. In stage 2, values of registers referred by decoded instruction are ready. See `readdata1` and `readdata2`. The contents of registers A and B (`aout` and `bout`) are ready for use in stage 3. The content of ALUOut (`aluoutput`) is ready for stage 4 and the `writedata` port of the register file is set to `0x00000001` in the stage 4 of the execution. An R-type instruction such as `slt` requires 4 stages to complete the execution.


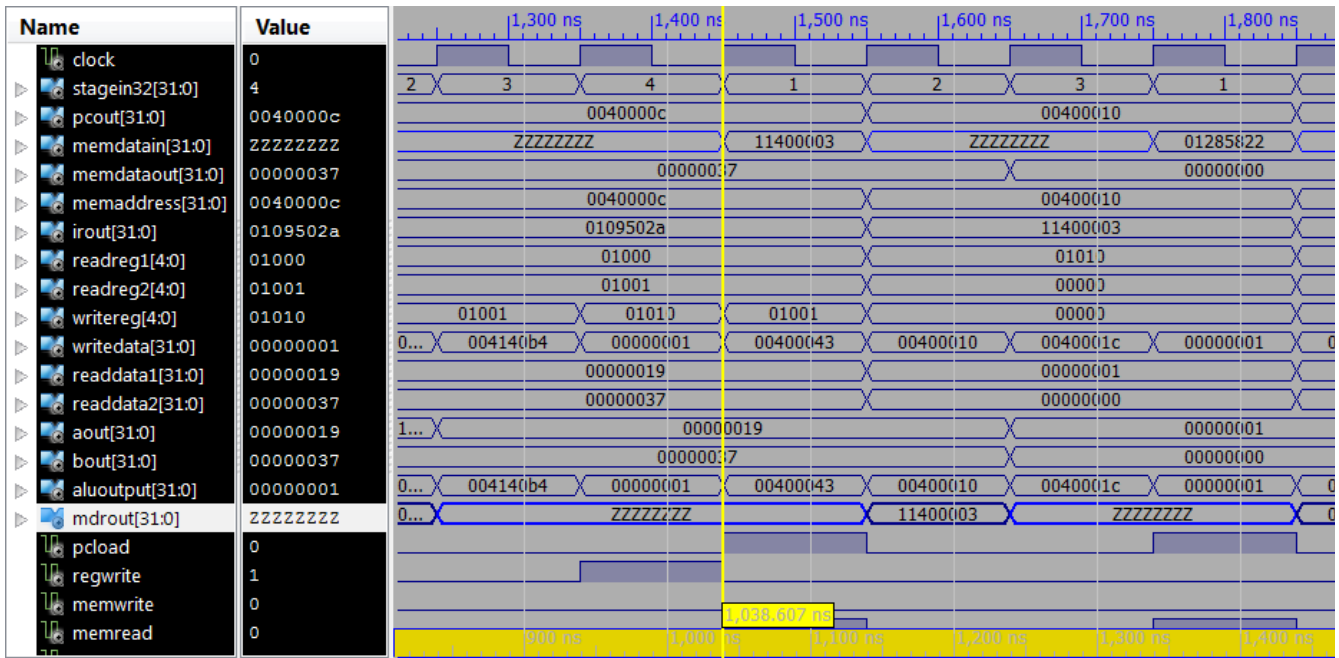


Figure 14: Data flow of the execution of beq instruction. The branch address calculated in stage 2 (0x0040001C) is ready in ALUOut for stage 3. The two values being compared, 0x00000001 and 0x00000000, are loaded into registers A and B whose contents are ready after stage 2. The compared values are not equal, so the branch is not taken and PC keeps its address.

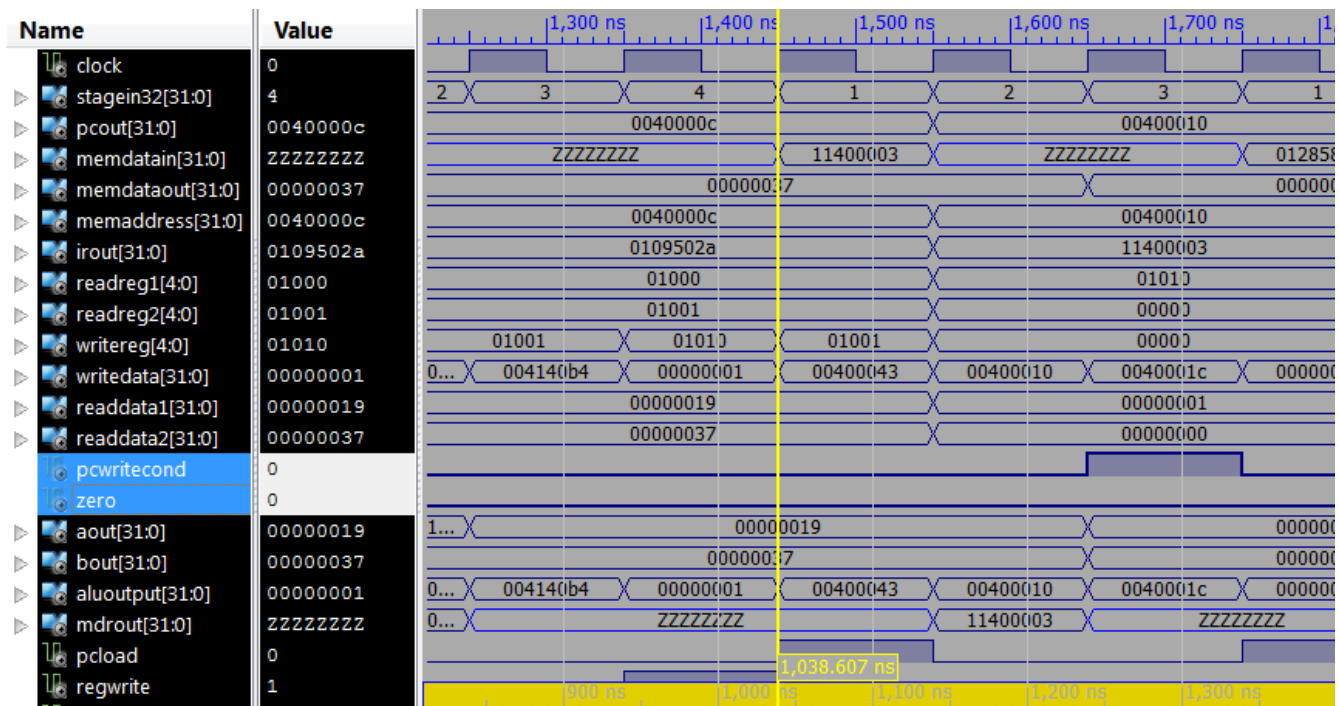

Supplement 1: Moving pcwritecond and zero signals upto the viewable area showing pcwritecond is asserted at stage 3 allowing change address of the PC if zero is '1'.

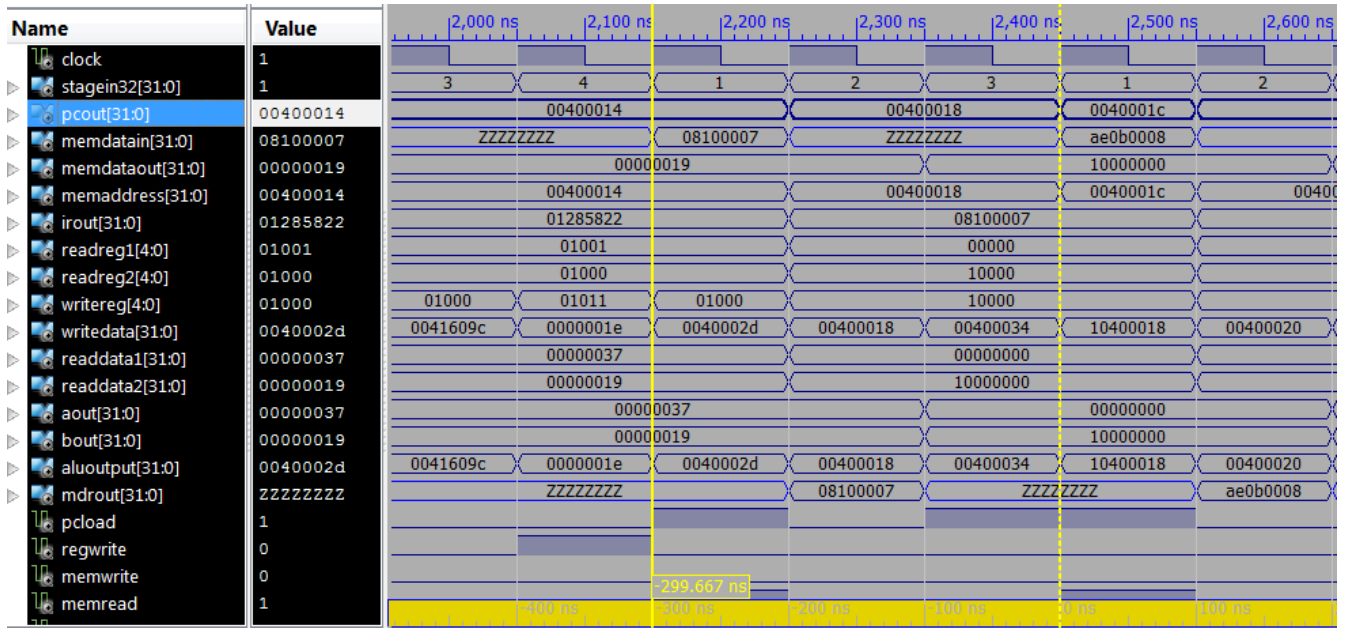


Figure 15: Data flow of the execution of *j* instruction. In stage 3, *pload* is '1', because *PCWrite*, not shown here, is '1'. The *PC* is updated after the end of stage 3 and having its new address ready for the next execution, as seen by that 0x0040001C is a content of *PC* at stage 1 of the following instruction.

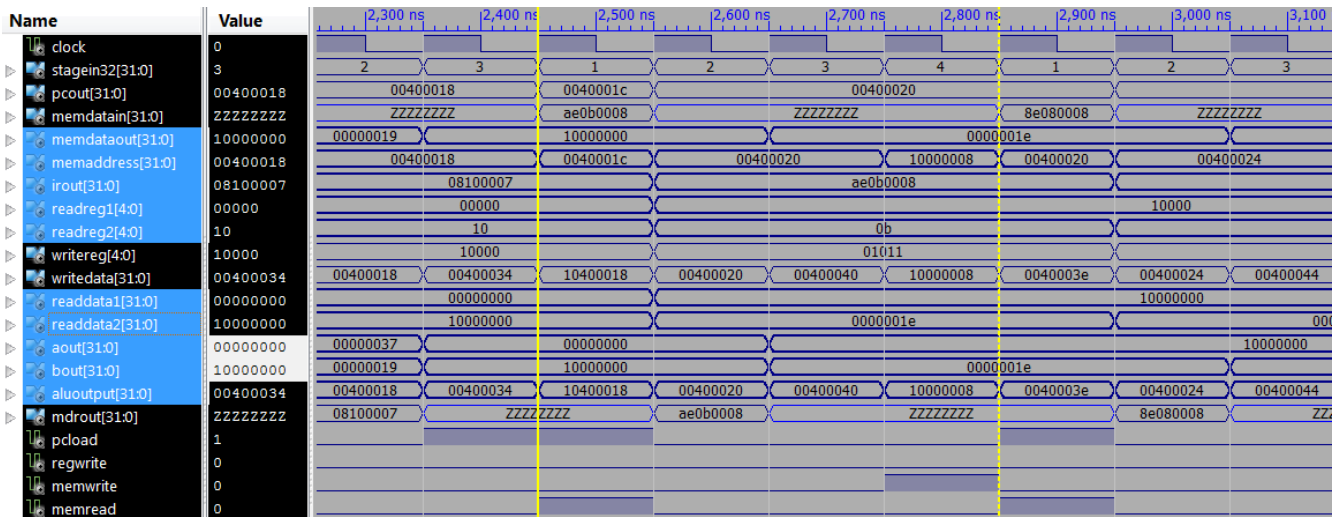


Figure 16: Data flow of the execution of *sw* instruction. After stage 2, values of registers *A* and *B*, indicated by *aout* and *bout* are 0x10000000 (the base address) and 0x0000001E (the value to be stored). The value of register *B* is connected to write data port of the memory (*memdataout*). After stage 3, *ALUOut* (*aluoutput*) is updated and its value is the target address. In stage 4, the address port of the memory is rerouted to the *ALUOut* and the *memwrite* signal is asserted to write the data into the memory.

3.2) Your task is to change contents of the memory at addresses 0x10000000 and 0x10000004 to be

0xFFFFFFFF19 and 0xFFFFFFFF37.

Questions

(3.2.1) What are the decimal values of 0xFFFFFFFF19 and 0xFFFFFFFF37, if they are in 2's complement format?

(3.2.2) With this change, will the branch be taken when we run the same program? Why? (or, if you think the branch will not be taken, why not?)

(3.2.3) With this data, what will be the value to be stored at the address 0x10000008?

(3.2.4) Run the simulation, report the result, and explain what is going on in each stage of the execution of the branch instruction.

(d1) How can you find the branch instruction in a long simulated waveform?

(d2) By looking at the waveform, how can you tell whether the branch is taken or not?

***Bonus* Extend what was given. It's your turn, Little engineer.**

B.1 What aspect of the given implementation do you want to improve? Why and how? Propose your idea. You don't need to do the VHDL code.

B.2 Now, choose your contribution you like to work on this processor project. Code it in VHDL and make a test bench and verify that it functions as expected.

Hint: there are many things you can do, such as adding capacity to handle other instructions. This does not have to be implementation of your answer to B.1.

B.3 The function of the memory data register.

(a) What is the function of the memory data register (MDR)?

(b) Instead of sticking to the datapath in Fig. 5.33 (P&H 2e) and the control signals as shown in Table 2, what would happen if we bypass the MDR?

This is to connect the MemData directly to the multiplexor controlled with MemtoReg signal.

What are the pros and cons of doing this?

(c) Design experiments to support your answer in 2.2b.

(d) Run your designed experiments, present results, and provide conclusions.

"It's not about what happened in the past, or what you think might happen in the future. It's about the ride, for Christ's sake. There is no point in going through all this crap, if you are not going to enjoy the ride. And you know what... when you least expect something great might come along. Something better than you even planned for." - Irving Feffer, from Along Came Polly (2004).

==== **Want more? Try these out.** ====

* <http://www.xilinx.com/itp/xilinx4/data/docs/xst/hdlcode.html>

Closing note

It is a good practice to test every newly created component, so that any flaw in design will be spotted earlier in the development cycle. It's also easier to pin point an error in a single component than trouble shooting unexpected results of an entire system.

Appendix: VHDL codes

ch5path_tb

```
-----
-- Company:      comp. engr. KKU.
-- Engineer:     TK
--
-- Create Date:  17:22:42 09/05/2011
--
-- Module Name:  ch5path_tb - Behavioral
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ch5path_tb is
end ch5path_tb;

architecture Behavioral of ch5path_tb is

-- output of datapath --
signal      clock           : std_logic;
signal      memdatain       : std_logic_vector(31 downto 0);
signal      memdataout      : std_logic_vector(31 downto 0);
signal      memaddress      : std_logic_vector(31 downto 0);
signal      memwrite        : std_logic;
signal      memread         : std_logic;
signal      startup         : std_logic;
load a start-up setting

-----

-- test bench component --

    component ch5mem is
    port
    (
        clock           : in std_logic;
        datain          : in std_logic_vector(31 downto 0);
        memaddress      : in std_logic_vector(31 downto 0);
        memwrite        : in std_logic;
        memread         : in std_logic;
        dataout         : out std_logic_vector(31 downto 0);
        enable          : in std_logic;
        startup         : in std_logic -- to load pre-written data
    );
    end component;

-- original components --

component WordALU is
    Port ( a, b : in std_logic_vector (31 downto 0);
          Binvert, CarryIn : in std_logic;
          Operation : in std_logic_vector (1 downto 0);
          Result : out std_logic_vector (31 downto 0);
          Overflow, Zero : out std_logic);
```



```

end component;

component mux2 is
port(
    sel:          in std_logic;
    ch1:          in std_logic_vector(31 downto 0);
    ch2:          in std_logic_vector(31 downto 0);
    muxout: out std_logic_vector (31 downto 0)
);
end component;

component mux4 is
port(
    sel:          in std_logic_vector(1 downto 0);
    ch1:          in std_logic_vector(31 downto 0);
    ch2:          in std_logic_vector(31 downto 0);
    ch3:          in std_logic_vector(31 downto 0);
    ch4:          in std_logic_vector(31 downto 0);
    muxout: out std_logic_vector (31 downto 0)
);
end component;

component nbitregister is
    generic (n : integer := 32);
    Port (
        win:          in std_logic_vector (31 downto 0);
        clock:        in std_logic;
        reload:        in std_logic;
        regclear:      in std_logic;
        wout:          out std_logic_vector (31 downto 0)
    );
end component;

component regfile is
port(
    readreg1:        in std_logic_vector (4 downto 0);        -- index referring to a specific
    register         register
    readreg2:        in std_logic_vector (4 downto 0);        -- index referring to a specific
    register         register
    writereg:        in std_logic_vector (4 downto 0);        -- index referring to a specific
    register         register
    writedata:       in std_logic_vector (31 downto 0);        -- data to put in the specified
    register's content
    readdata1:       out std_logic_vector (31 downto 0);        -- data contained in register indexed by
    readreg1
    readdata2:       out std_logic_vector (31 downto 0);        -- data contained in register indexed by
    readreg2
    RegWrite:        in std_logic;
    clock:           in std_logic
);
end component;

component signextend
    port(
        halfword : in  std_logic_vector(15 downto 0);
        fullword : out std_logic_vector(31 downto 0)
    );
end component;

COMPONENT maincontrol
PORT(
    PCWriteCond : OUT  std_logic;
    PCWrite      : OUT  std_logic;
    PCSource    : OUT  std_logic_vector(1 downto 0);
    MemRead     : OUT  std_logic;
    MemWrite    : OUT  std_logic;

```

```

IorD          : OUT std_logic;
IRWrite       : OUT std_logic;
ALUOp        : OUT std_logic_vector(1 downto 0);
ALUSrcB      : OUT std_logic_vector(1 downto 0);
ALUSrcA      : OUT std_logic;
RegWrite     : OUT std_logic;
RegDst       : OUT std_logic;
MemtoReg     : OUT std_logic;
stagein      : IN  std_logic_vector(2 downto 0);
opcode       : IN  std_logic_vector(5 downto 0);
stageout     : OUT std_logic_vector(2 downto 0)
);
END COMPONENT;

component ALUControl
port(
    ALUOp        : in  std_logic_vector(1 downto 0);
    funct       : in  std_logic_vector(5 downto 0);
    Binvert     : out std_logic;
    Operation   : out std_logic_vector(1 downto 0)
);
end component;

-----
-- signals --
-----

signal clk          : std_logic;

-- register file --
signal readreg1 : std_logic_vector (4 downto 0);
signal readreg2 : std_logic_vector (4 downto 0);
signal writereg : std_logic_vector (4 downto 0);           -- we use only 4 bits, but this would allow it for being
used with a 32-bit mux.
signal writedata: std_logic_vector (31 downto 0);
signal readdata1: std_logic_vector (31 downto 0);
signal readdata2: std_logic_vector (31 downto 0);

-- alu --
signal a, b          : std_logic_vector (31 downto 0);
signal Binvert, CarryIn : std_logic;
signal Operation     : std_logic_vector (1 downto 0);
signal Result        : std_logic_vector (31 downto 0);
signal Overflow, Zero : std_logic;

-- registers --
signal PCin          : std_logic_vector (31 downto 0);
signal PCload       : std_logic;
signal PCout, IRout, MDRout, Aout, Bout, ALUoutput          : std_logic_vector (31 downto 0);

-- main control signals --
signal RegWrite : std_logic;
signal IRWrite  : std_logic;
signal ALUSrcB : std_logic_vector (1 downto 0);
signal PCSource : std_logic_vector (1 downto 0);
signal IorD, RegDst, MemtoReg, ALUSrcA : std_logic;
signal ALUOp    : std_logic_vector (1 downto 0);
signal PCWrite, PCWriteCond : std_logic;

-- pathway signals --

signal SignEx          : std_logic_vector (31 downto 0);

signal adapterMX0      : std_logic_vector (31 downto 0);
signal adapterMX1      : std_logic_vector (31 downto 0);

```

```

signal adapterMXout      : std_logic_vector (31 downto 0);

signal jaddr             : std_logic_vector (31 downto 0);
signal beqoffset: std_logic_vector (31 downto 0);

signal PCSourceOut      : std_logic_vector (31 downto 0);

signal stagein32, stageout32 : std_logic_vector (31 downto 0);

-- simulation variables --

-- Clock period definitions
constant clock_period : time := 100 ns;

begin

    clk <= clock;

    regs: regfile
    port map (
        readreg1      => readreg1,
        readreg2      => readreg2,
        writereg       => writereg,
        writedata      => writedata,
        readdata1      => readdata1,
        readdata2      => readdata2,
        RegWrite       => RegWrite,
        clock           => clk);

    alu: WordALU
    port map (
        a => a,
        b => b,
        Binvert => Binvert,
        CarryIn => CarryIn,
        Operation => Operation,
        Result => Result,
        Overflow => Overflow,
        Zero => Zero);

    PC: nbitregister
    port map (
        win => PCin,
        clock => clk,
        regload => PCload,
        regclear => '0',
        wout => PCout);

    IR: nbitregister
    port map (
        win => memdatain,
        clock => clk,
        regload => IRWrite,
        regclear => startup,
        wout => IRout);

    MDR: nbitregister
    port map (
        win => memdatain,
        clock => clk,
        regload => '1',
        regclear => startup,
        wout => MDRout);

    Areg: nbitregister

```

```

port map (
    win => readdata1,
    clock => clk,
    regload => '1',
    regclear => startup,
    wout => Aout);

Breg: nbitregister
port map (
    win => readdata2,
    clock => clk,
    regload => '1',
    regclear => startup,
    wout => Bout);

ALUout: nbitregister
port map (
    win => Result,
    clock => clk,
    regload => '1',
    regclear => startup,
    wout => ALUoutput);

mxsrcB: mux4
port map (
    sel          => ALUSrcB,
    ch1          => Bout,
    ch2          => x"00000004",
    ch3          => SignEx,
    ch4          => beqoffset,
    muxout      => b);
-- R-type
-- PC increment
-- lw/sw
-- branch address

beqoffset <= SignEx(29 downto 0) & "00";

mxsrcPC: mux4
port map (
    sel          => PCSource,
    ch1          => Result,
    ch2          => ALUoutput,
    ch3          => jaddr,
    ch4          => x"00400000",
    muxout      => PCSourceOut);
-- PC <= PC + 4
-- beq
-- j
-- boot up address

jaddr <= PCOut(31 downto 28) & IRout(25 downto 0) & "00";

mxIorD: mux2
port map (
    sel          => IorD,
    ch1          => PCout,
    ch2          => ALUoutput,
    muxout      => memaddress);
-- instruction access
-- memory access (lw/sw)

mxRegDst: mux2
port map (
    sel          => RegDst,
    ch1          => adapterMX0,
    ch2          => adapterMX1,
    muxout      => adapterMXout);
-- lw
-- R-type

adapterMX0 <= "000000000000000000000000" & IRout(20 downto 16);
adapterMX1 <= "000000000000000000000000" & IRout(15 downto 11);
writereg <= adapterMXout(4 downto 0);

```

```

mxMementoReg: mux2
port map (
    sel          => MementoReg,
    ch1          => ALUOutput,  -- R-type
    ch2          => MDRout,      -- lw
    muxout       => writedata);

mxsrcA: mux2
port map (
    sel          => ALUSrcA,
    ch1          => PCout,      -- PC increment / branch address
    ch2          => Aout,       -- R-type, lw, sw
    muxout       => a);

PCin <= PCSourceOut;

SE: signextend
port map (
    halfword => IRout(15 downto 0),
    fullword => SignEx);

alucon: ALUControl
port map (
    ALUOp => ALUOp,
    funct => IRout(5 downto 0),
    Binvert => Binvert,
    Operation => Operation);

CarryIn <= Binvert;    -- Both Binvert and CarryIn indicate subtraction (of sub, slt, and comparing for
beq) when set.                                               -- Both are reset for other operations.

maincon: maincontrol
port map (
    PCWriteCond => PCWriteCond,
    PCWrite => PCWrite,
    PCSource => PCSource,
    MemRead => MemRead,
    MemWrite => MemWrite,
    Iord => Iord,
    IRWrite => IRWrite,
    ALUOp => ALUOp,
    ALUSrcB => ALUSrcB,
    ALUSrcA => ALUSrcA,
    RegWrite => RegWrite,
    RegDst => RegDst,
    MementoReg => MementoReg,
    stagein => stagein32(2 downto 0),
    opcode => IRout(31 downto 26),
    stageout => stageout32(2 downto 0));

stageout32(31 downto 3) <= "00000000000000000000000000000000";

statereg: nbitregister
port map (
    win => stageout32,
    clock => clk,
    regload => '1',
    regclear => startup,
    wout => stagein32);

-- nodes --
memdataout <= Bout;

```

```

    readreg1 <= IRout(25 downto 21);
    readreg2 <= IRout(20 downto 16);

    PCload <= PCWrite or (PCWriteCond and Zero);

-- Simulation part --

    mem: ch5mem
    port map (
        clock           => clock,
        datain          => memdataout,
        memaddress      => memaddress,
        memwrite        => memwrite,
        memread         => memread,
        dataout         => memdatain,
        enable          => '1',
        startup         => startup);

-- Clock process definitions
clock_process :process
begin
    clock <= '0';
    wait for clock_period/2;
    clock <= '1';
    wait for clock_period/2;
end process;

-- Stimulus process
stim_proc: process
begin

    startup <= '0';
    wait for clock_period/10;

    startup <= '1';
    wait for clock_period/10;

    startup <= '0';
    wait;
end process;

-- simulation time = 4000 ns
end Behavioral;

```

ALUControl_tb

```

-----
-- Company:
-- Engineer:
--
-- Create Date:   08:59:04 09/06/2011
-- Design Name:
-- Module Name:   C:/xilinx_tutorial/Ch05/ALUControl_tb.vhd
-- Project Name:  Ch05
-- Target Device:
-- Tool versions:
-- Description:
--
-- VHDL Test Bench Created by ISE for module: ALUControl
--
-- Dependencies:
--
-- Revision:

```

```

-- Revision 0.01 - File Created
-- Additional Comments:
--
-- Notes:
-- This testbench has been automatically generated using types std_logic and
-- std_logic_vector for the ports of the unit under test. Xilinx recommends
-- that these types always be used for the top-level I/O of a design in order
-- to guarantee that the testbench will bind correctly to the post-implementation
-- simulation model.
-----
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

ENTITY ALUControl_tb IS
END ALUControl_tb;

ARCHITECTURE behavior OF ALUControl_tb IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT ALUControl
    PORT(
        ALUOp : IN  std_logic_vector(1 downto 0);
        funct : IN  std_logic_vector(5 downto 0);
        Binvert : OUT std_logic;
        Operation : OUT std_logic_vector(1 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal ALUOp : std_logic_vector(1 downto 0) := (others => '0');
    signal funct : std_logic_vector(5 downto 0) := (others => '0');

    --Outputs
    signal Binvert : std_logic;
    signal Operation : std_logic_vector(1 downto 0);
    -- No clocks detected in port list. Replace <clock> below with
    -- appropriate port name

    constant period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: ALUControl PORT MAP (
        ALUOp => ALUOp,
        funct => funct,
        Binvert => Binvert,
        Operation => Operation
    );

    -- Stimulus process
    stim_proc: process
    begin
        -- hold reset state for 50 ns.
        wait for 50 ns;

        -- lw/sw: add --
        ALUOp <= "00";
        wait for period;
    end process;

```

```

        -- beq: sub --
        ALUOp <= "01";
        wait for period;

        -- R-type --
        ALUOp <= "10";          funct <= "100000";
        wait for period;

        ALUOp <= "10";          funct <= "100010";
        wait for period;

        ALUOp <= "10";          funct <= "100100";
        wait for period;

        ALUOp <= "10";          funct <= "100101";
        wait for period;

        ALUOp <= "10";          funct <= "101010";
        wait for period;

        wait;
    end process;

END;
```

maincontrol_tb

```

-----
-- Company:
-- Engineer:
--
-- Create Date:   08:08:24 09/06/2011
-- Design Name:
-- Module Name:   C:/xilinx_tutorial/Ch05/maincontrol_tb.vhd
-- Project Name:  Ch05
-- Target Device:
-- Tool versions:
-- Description:
--
-- VHDL Test Bench Created by ISE for module: maincontrol
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-- Notes:
-- This testbench has been automatically generated using types std_logic and
-- std_logic_vector for the ports of the unit under test.  Xilinx recommends
-- that these types always be used for the top-level I/O of a design in order
-- to guarantee that the testbench will bind correctly to the post-implementation
-- simulation model.
-----
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

ENTITY maincontrol_tb IS
END maincontrol_tb;
```


ARCHITECTURE behavior OF maincontrol_tb IS

-- Component Declaration for the Unit Under Test (UUT)

```
COMPONENT maincontrol
PORT(
  PCWriteCond : OUT std_logic;
  PCWrite : OUT std_logic;
  PCSource : OUT std_logic_vector(1 downto 0);
  MemRead : OUT std_logic;
  MemWrite : OUT std_logic;
  IorD : OUT std_logic;
  IRWrite : OUT std_logic;
  ALUOp : OUT std_logic_vector(1 downto 0);
  ALUSrcB : OUT std_logic_vector(1 downto 0);
  ALUSrcA : OUT std_logic;
  RegWrite : OUT std_logic;
  RegDst : OUT std_logic;
  MemtoReg : OUT std_logic;
  stagein : IN std_logic_vector(2 downto 0);
  opcode : IN std_logic_vector(5 downto 0);
  stageout : OUT std_logic_vector(2 downto 0)
);
END COMPONENT;
```

--Inputs

```
signal stagein : std_logic_vector(2 downto 0) := (others => '0');
signal opcode : std_logic_vector(5 downto 0) := (others => '0');
```

--Outputs

```
signal PCWriteCond : std_logic;
signal PCWrite : std_logic;
signal PCSource : std_logic_vector(1 downto 0);
signal MemRead : std_logic;
signal MemWrite : std_logic;
signal IorD : std_logic;
signal IRWrite : std_logic;
signal ALUOp : std_logic_vector(1 downto 0);
signal ALUSrcB : std_logic_vector(1 downto 0);
signal ALUSrcA : std_logic;
signal RegWrite : std_logic;
signal RegDst : std_logic;
signal MemtoReg : std_logic;
signal stageout : std_logic_vector(2 downto 0);
-- No clocks detected in port list. Replace <clock> below with
-- appropriate port name
```

```
constant period : time := 10 ns;
```

BEGIN

-- Instantiate the Unit Under Test (UUT)

```
uut: maincontrol PORT MAP (
  PCWriteCond => PCWriteCond,
  PCWrite => PCWrite,
  PCSource => PCSource,
  MemRead => MemRead,
  MemWrite => MemWrite,
  IorD => IorD,
  IRWrite => IRWrite,
  ALUOp => ALUOp,
  ALUSrcB => ALUSrcB,
  ALUSrcA => ALUSrcA,
  RegWrite => RegWrite,
  RegDst => RegDst,
```

```

        MemtoReg => MemtoReg,
        stagein => stagein,
        opcode => opcode,
        stageout => stageout
    );

-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 20 ns;

        stagein <= "000";
    wait for period;

        -- r-type --
    opcode <= "000000";

        stagein <= "001";
    wait for period;

        stagein <= "010";
    wait for period;

        stagein <= "011";
    wait for period;

        stagein <= "100";
    wait for period;

        -- lw --
    opcode <= "100011";

        stagein <= "001";
    wait for period;

        stagein <= "010";
    wait for period;

        stagein <= "011";
    wait for period;

        stagein <= "100";
    wait for period;

        stagein <= "101";
    wait for period;

        -- sw --
    opcode <= "101011";

        stagein <= "001";
    wait for period;

        stagein <= "010";
    wait for period;

        stagein <= "011";
    wait for period;

        stagein <= "100";
    wait for period;

        -- beq --
    opcode <= "000100";

```

```

        stagein <= "001";
wait for period;

        stagein <= "010";
wait for period;

        stagein <= "011";
wait for period;

        -- j --
opcode <= "000010";

        stagein <= "001";
wait for period;

        stagein <= "010";
wait for period;

        stagein <= "011";
wait for period;

        -- simulation time = 300 ns --
wait;
end process;

```

END;

WordALU_tb

```

-----
-- Company:          comp. engr. KKU.
-- Engineer:         TK
--
-- Create Date:     09:55:02 08/22/2011
-- Design Name:
-- Module Name:     WordALU_tb - Behavioral
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
-- "If you think you can do a thing or think you can't do a thing, you're right."
-- - Henry Ford

```

```

-----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity WordALU_tb is
end WordALU_tb;

architecture Behavioral of WordALU_tb is

component WordALU is
    Port ( a, b : in  STD_LOGIC_VECTOR (31 downto 0);

```

```

    Binvert, CarryIn : in STD_LOGIC;
    Operation : in STD_LOGIC_VECTOR (1 downto 0);
    Result : out STD_LOGIC_VECTOR (31 downto 0);
    Overflow, Zero : out STD_LOGIC;
end component;

    signal a, b : STD_LOGIC_VECTOR (31 downto 0);
    signal Binvert, CarryIn : STD_LOGIC;
    signal Operation : STD_LOGIC_VECTOR (1 downto 0);
    signal Result : STD_LOGIC_VECTOR (31 downto 0);
    signal Overflow, Zero : STD_LOGIC;

    constant PERIOD : time := 100 ns;

begin

    walu: WordALU
    port map (
        a => a,
        b => b,
        Binvert => Binvert,
        CarryIn => CarryIn,
        Operation => Operation,
        Result => Result,
        Overflow => Overflow,
        Zero => Zero);

    PROCESS
    BEGIN

        Binvert <= '0';
        CarryIn <= '0';

        -- AND --
        Operation <= "00";      -- 00: AND, 01: OR, 10: ADDITION, 11: Less (slt)
        a <= "00111111111100000110000001101010";
        b <= "01011011110000001010010011110010";
        -- expect: "0001101111000000010000001100010" = '0x1bc02062'
        WAIT FOR PERIOD;

        -- OR --
        Operation <= "01";      -- 00: AND, 01: OR, 10: ADDITION, 11: Less (slt)
        a <= "00111111111100000110000001101010";
        b <= "01011011110000001010010011110010";
        -- expect: "0111111111100001110010011111010" = '0x7ff0e4fa'
        WAIT FOR PERIOD;

        -- ADDITION --
        -- A + B; A > 0, B > 0, no overflow

        Binvert <= '0';          -- A + B
        CarryIn <= '0';
        Operation <= "10";      -- 00: AND, 01: OR, 10: ADDITION, 11: Less (slt)

        a <= "00111111111100000110000001101010";
        b <= "00111111110000001010010011110010";
        -- expect: "01111111101100010000010101011100" = 0x7fb1055c

        WAIT FOR PERIOD;

        -- A + B; A > 0, B > 0, overflow

        Binvert <= '0';          -- A + B
        CarryIn <= '0';
        Operation <= "10";      -- 00: AND, 01: OR, 10: ADDITION, 11: Less (slt)

```

```

a          <= "0111111111110000011000001101010";
b          <= "001111111110000001010010011110010";
-- expect:  "10111111101100010000010101011100" = 0xbfb1055c

WAIT FOR PERIOD;

-- A + B; A < 0, B < 0, no overflow

Binvert <= '0';          -- A + B
CarryIn <= '0';
Operation <= "10";      -- 00: AND, 01: OR, 10: ADDITION, 11: Less (slt)

a          <= "11000100011001010011011000000000"; -- = 0xc4653600 = -1000000000
b          <= "10111011101000100010101101000000"; -- = 0xbba22b40 = -1147000000
-- expect:  "d1000000000001110110000101000000"; -- = 0x80076140 = -2147000000

WAIT FOR PERIOD;

-- A + B; A > 0, B < 0

Binvert <= '0';          -- A + B
CarryIn <= '0';
Operation <= "10";      -- 00: AND, 01: OR, 10: ADDITION, 11: Less (slt)

a          <= "01000100011001010011011000000000"; -- = 0x44653600 = 1147483648
b          <= "10111011101000100010101101000000"; -- = 0xbba22b40 = -1147000000
-- expect:  "?0000000000001110110000101000000"; -- = 0x00076140 = 483648

WAIT FOR PERIOD;

-- A + B; A < 0, B > 0

Binvert <= '0';          -- A + B
CarryIn <= '0';
Operation <= "10";      -- 00: AND, 01: OR, 10: ADDITION, 11: Less (slt)

a          <= "10111011101000100010101101000000"; -- = 0xbba22b40 = -1147000000
b          <= "01000100011001010011011000000000"; -- = 0x44653600 = 1147483648
-- expect:  "?0000000000001110110000101000000"; -- = 0x00076140 = 483648

WAIT FOR PERIOD;

-- A - B; A > 0, B > 0

Binvert <= '1';          -- A - B
CarryIn <= '1';
Operation <= "10";      -- 00: AND, 01: OR, 10: ADDITION, 11: Less (slt)

a          <= "0011111111110000011000001101010"; -- = 0x3ff0606a = 1072717930
b          <= "001111111110000001010011110010"; -- = 0x3fc0a4f2 = 1069589746
-- expect:  "0000000001011111011101101111000"      = 0x002fbb78 = 3128184

WAIT FOR PERIOD;

-- A - B; A > 0, B < 0, no overflow

Binvert <= '1';          -- A - B
CarryIn <= '1';
Operation <= "10";      -- 00: AND, 01: OR, 10: ADDITION, 11: Less (slt)

a          <= "0011111111110000011000001101010"; -- = 0x3ff0606a = 1072717930
b          <= "111111111111101100011110000000"; -- = 0xffffec780 = -80000
-- expect:  "00111111111100011001100011101010"      = 0x3ff198ea = 1072797930

WAIT FOR PERIOD;

```

```

-- A - B; A > 0, B < 0, overflow

Binvert <= '1';          -- A - B
CarryIn <= '1';
Operation <= "10";      -- 00: AND, 01: OR, 10: ADDITION, 11: Less (slt)

a          <= "01111111111100000110000001101010"; -- = 0x7ff0606a = 2146459754
b          <= "11111111110000101111011100000000"; -- = 0xffc2f700 = -4000000
-- expect: "10000000001011010110100101101010";      = 0x802d696a ; 2150459754

WAIT FOR PERIOD;

-- A - B; A < 0, B < 0

-- <input code for this test case>

-- A - B; A < 0, B > 0, no overflow

-- <input code for this test case>

-- A - B; A < 0, B > 0, overflow

Binvert <= '1';          -- A - B
CarryIn <= '1';
Operation <= "10";      -- 00: AND, 01: OR, 10: ADDITION, 11: Less (slt)

a          <= "11111111110000101111011100000000"; -- = 0xffc2f700 = -4000000
b          <= "01111111111100000110000001101010"; -- = 0x7ff0606a =
2146459754
-- expect: "?01111111110100101001011010010110";      = 0x7fd29696 ; -2150459754

WAIT FOR PERIOD;

-- LESS (slt) --

Operation <= "11";      -- 00: AND, 01: OR, 10: ADDITION, 11: Less (slt)

-- a < b
a          <= "00000000000000000000000000000101"; -- 5
b          <= "0000000000000000000000000000011100"; -- 28
WAIT FOR PERIOD;

-- a = b
a          <= "00000000000000000000000000000110110"; -- 54
b          <= "00000000000000000000000000000110110"; -- 54
WAIT FOR PERIOD;

-- a > b
a          <= "00000000000000000000000000000110110"; -- 54
b          <= "0000000000000000000000000000011100"; -- 28
WAIT FOR PERIOD;

-- a < b, a < 0, b < 0
a          <= "11111111111111111111110110111111"; -- -545
b          <= "1111111111111111111111011010100"; -- -300
WAIT FOR PERIOD;

-- a < b, a < 0, b > 0
a          <= "11111111111111111111110110111111"; -- -545
b          <= "0000000000000000000000000100101100"; -- 300
WAIT FOR PERIOD;

-- simulation time: 1600 + 100 ns

END PROCESS;

```

end Behavioral;

regfile_tb

```
-----  
-- Company:                comp. engr. KKU.  
-- Engineer:               TK  
--  
-- Create Date:           08:27:46 09/01/2011  
-- Design Name:           regfile_tb - Behavioral  
-- Module Name:           regfile_tb - Behavioral  
--  
-- Revision:                
-- Revision 0.01 - File Created  
-- Additional Comments:    
-- "Memory can change the shape of a room; it can change the color of a car.  
-- And memories can be distorted. They're just an interpretation, they're not a record,  
-- and they're irrelevant if you have the facts." - Leonard Shelby in Memento (2000)  
-----
```

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use ieee.numeric_std.ALL;
```

```
entity regfile_tb is  
end regfile_tb;
```

```
architecture Behavioral of regfile_tb is
```

```
component regfile is
```

```
port(  
    readreg1:          in std_logic_vector (4 downto 0);      -- index referring to a specific  
    register  
    readreg2:          in std_logic_vector (4 downto 0);      -- index referring to a specific  
    register  
    writereg:          in std_logic_vector (4 downto 0);      -- index referring to a specific  
    register  
    writedata:         in std_logic_vector (31 downto 0);     -- data to put in the specified  
    register's content  
    readdata1:         out std_logic_vector (31 downto 0);    -- data contained in register indexed by  
    readreg1  
    readdata2:         out std_logic_vector (31 downto 0);    -- data contained in register indexed by  
    readreg2  
    RegWrite:          in std_logic;  
    clock:             in std_logic  
);  
end component;
```

```
signal readreg1 : std_logic_vector (4 downto 0);      -- index referring to a specific register  
signal readreg2 : std_logic_vector (4 downto 0);      -- index referring to a specific register  
signal writereg : std_logic_vector (4 downto 0);      -- index referring to a specific register  
signal writedata: std_logic_vector (31 downto 0);     -- data to put in the specified register's content  
signal readdata1: std_logic_vector (31 downto 0);     -- data contained in register indexed by readreg1  
signal readdata2: std_logic_vector (31 downto 0);     -- data contained in register indexed by readreg2  
signal RegWrite : std_logic;  
signal clk      : std_logic;
```

```
constant PERIOD      : time := 100 ns;  
constant clkperiod   : time := 30 ns;
```

```
begin
```

```

regs: regfile
port map (
    readreg1      => readreg1,
    readreg2      => readreg2,
    writereg      => writereg,
    writedata     => writedata,
    readdata1     => readdata1,
    readdata2     => readdata2,
    RegWrite      => RegWrite,
    clock         => clk);

process
begin
    clk <= '0';
    wait for clkperiod;
    clk <= '1';
    wait for clkperiod;
end process;

process
variable regidx: integer :=0;

begin

    writedata      <= X"01FFAB00";
    writereg       <= "00001";
    wait for PERIOD/2;

    readreg1 <= "00000";
    readreg2 <= "00001";
    wait for PERIOD/2;

    RegWrite      <= '1';
    writedata     <= X"01FFAB00";
    writereg      <= "00001";
    wait for PERIOD/2;

    readreg1 <= "00000";
    readreg2 <= "00001";
    wait for PERIOD/2;

    readreg1 <= "10000";
    readreg2 <= "01000";
    wait for PERIOD/2;

    checkreg0: for regidx in 1 to 5 loop

        writereg <= std_logic_vector(to_unsigned(regidx, writereg'length));
        writedata <= std_logic_vector(to_unsigned(regidx*16, writedata'length));
        wait for PERIOD/2;

        readreg1 <= std_logic_vector(to_unsigned(regidx - 1, readreg1'length));
        readreg2 <= std_logic_vector(to_unsigned(regidx, readreg2'length));
        wait for PERIOD/2;

    end loop checkreg0;

    -- simulation time = 800 ns

end process;

end Behavioral;

```


nbitregister_tb

```
-----  
-- Company:          comp. engr. KKU.  
-- Engineer:         TK  
--  
-- Create Date:     12:15:13 08/29/2011  
-- Design Name:     nbitregister_tb - Behavioral  
-- Module Name:     nbitregister_tb - Behavioral  
-- Revision:          
-- Revision 0.01 - File Created  
-- Additional Comments:  
--  
-----  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
  
entity nbitregister_tb is  
end nbitregister_tb;  
  
architecture Behavioral of nbitregister_tb is  
  
constant Nbits : integer := 32;  
  
component nbitregister is  
    generic (n : integer := Nbits);  
    Port (  
        win:          in std_logic_vector (Nbits-1 downto 0);  
        clock:        in std_logic;  
        regload:      in std_logic;  
        regclear:     in std_logic;  
        wout:         out std_logic_vector (Nbits-1 downto 0));  
end component;  
  
signal win          : std_logic_vector (Nbits-1 downto 0);  
signal clk          : std_logic;  
signal regload      : std_logic;  
signal regclear     : std_logic;  
signal wout         : std_logic_vector (Nbits-1 downto 0);  
  
constant PERIOD : time := 50 ns;  
  
begin  
  
    reg: nbitregister  
    port map (  
        win => win,  
        clock => clk,  
        regload => regload,  
        regclear => regclear,  
        wout => wout);  
  
    PROCESS  
    BEGIN  
        clk <= '0';  
        wait for PERIOD/2;  
        clk <= '1';  
        wait for PERIOD/2;  
    END PROCESS;  
  
    PROCESS  
    BEGIN  
        win          <= "11111111000000100000000110100010";  
        regload <= '0';  
        regclear <= '0';  
    END PROCESS;  
end;
```

```

        wait for PERIOD/4;

        regload <= '1';
        wait for PERIOD;

        regload <= '0';
        regclear<= '1';
        wait for PERIOD;

        -- simulation time = 150 ns

    END PROCESS;

end Behavioral;
--

mux2_tb

--
-----
-- Company:                comp. engr. KKU.
-- Engineer:                TK
--
-- Create Date:            16:27:46 09/01/2011
-- Design Name:
-- Module Name:            mux2_tb - Behavioral
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
-- "Memory can change the shape of a room; it can change the color of a car.
-- And memories can be distorted. They're just an interpretation, they're not a record,
-- and they're irrelevant if you have the facts." - Leonard Shelby in Memento (2000)
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mux2_tb is
end mux2_tb;

architecture Behavioral of mux2_tb is

component mux2 is
port(
    sel:            in std_logic;
    ch1:            in std_logic_vector(31 downto 0);
    ch2:            in std_logic_vector(31 downto 0);
    muxout: out std_logic_vector (31 downto 0)
);
end component;

signal sel:            std_logic;
signal ch1:            std_logic_vector(31 downto 0);
signal ch2:            std_logic_vector(31 downto 0);
signal muxout: std_logic_vector (31 downto 0);

constant PERIOD      : time := 100 ns;

begin

    mux: mux2
    port map (
        sel => sel,

```

```

        ch1          => ch1,
        ch2          => ch2,
        muxout      => muxout);

process
begin
    ch1 <= X"0AAA00AA";
    ch2 <= X"0B00000B";

    sel <= '0';
    wait for PERIOD;
    ch1 <= X"1A1A11AA";
    wait for PERIOD/2;
    ch1 <= X"A00A00AA";
    wait for PERIOD/2;

    sel <= '1';
    wait for PERIOD;
    ch2 <= X"0C00000C";
    wait for PERIOD/4;
    ch2 <= X"0D00000D";
    wait for PERIOD/4;

    -- simulation time = 400 ns
end process;

end Behavioral;
--

```

mux4_tb

```

--
-----
-- Company:                comp. engr. KKU.
-- Engineer:                TK
--
-- Create Date:            12:34:46 09/02/2011
-- Design Name:
-- Module Name:            mux4_tb - Behavioral
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
-- "You cannot dream yourself into a character; you must hammer and forge yourself one."
-- - By the English historian, James Anthony Froude (1818-1894) from his book, The Nemesis of Faith.
-----

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mux4_tb is
end mux4_tb;

architecture Behavioral of mux4_tb is

component mux4 is
port(
    sel:          in std_logic_vector(1 downto 0);
    ch1:          in std_logic_vector(31 downto 0);
    ch2:          in std_logic_vector(31 downto 0);
    ch3:          in std_logic_vector(31 downto 0);
    ch4:          in std_logic_vector(31 downto 0);
    muxout:      out std_logic_vector (31 downto 0)

```

```

);
end component;

signal sel:          std_logic_vector(1 downto 0);
signal ch1:          std_logic_vector(31 downto 0);
signal ch2:          std_logic_vector(31 downto 0);
signal ch3:          std_logic_vector(31 downto 0);
signal ch4:          std_logic_vector(31 downto 0);
signal muxout: std_logic_vector (31 downto 0);

constant PERIOD      : time := 100 ns;

begin

    mux: mux4
    port map (
        sel          => sel,
        ch1          => ch1,
        ch2          => ch2,
        ch3          => ch3,
        ch4          => ch4,
        muxout       => muxout);

    process
    begin
        ch1 <= X"10A000AA";
        ch2 <= X"20B0000B";
        ch3 <= X"30C0000C";
        ch4 <= X"40D0000D";

        sel <= "00";
        wait for PERIOD;

        ch1 <= X"111000AA";
        wait for PERIOD/2;

        ch1 <= X"122000AA";
        wait for PERIOD/2;

        sel <= "01";
        wait for PERIOD;

        sel <= "10";
        wait for PERIOD;

        sel <= "11";
        wait for PERIOD;

        -- simulation time = 500 ns
    end process;
end Behavioral;
--

```

signextend_tb

```

--
-----
-- Company:
-- Engineer:
--
-- Create Date:    00:25:00 09/05/2011
-- Design Name:
-- Module Name:    C:/xilinx_tutorial/Ch05/signextend_tb.vhd

```

```

-- Project Name: Ch05
-- Target Device:
-- Tool versions:
-- Description:
--
-- VHDL Test Bench Created by ISE for module: signextend
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-- Notes:
-- This testbench has been automatically generated using types std_logic and
-- std_logic_vector for the ports of the unit under test. Xilinx recommends
-- that these types always be used for the top-level I/O of a design in order
-- to guarantee that the testbench will bind correctly to the post-implementation
-- simulation model.
-----
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

ENTITY signextend_tb IS
END signextend_tb;

ARCHITECTURE behavior OF signextend_tb IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT signextend
    PORT(
        halfword : IN  std_logic_vector(15 downto 0);
        fullword  : OUT std_logic_vector(31 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal halfword : std_logic_vector(15 downto 0) := (others => '0');

    --Outputs
    signal fullword : std_logic_vector(31 downto 0);
    -- No clocks detected in port list. Replace <clock> below with
    -- appropriate port name

    constant PERIOD : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: signextend PORT MAP (
        halfword => halfword,
        fullword => fullword
    );

    -- Stimulus process
    stim_proc: process
    begin

        halfword <= x"80AB";
        wait for 100 ns;
    end process;

```

```

        halfword <= x"4012";
    wait for 100 ns;

end process;

END;
--

```

ch5mem_tb

```

--
-----
-- Company:
-- Engineer:
--
-- Create Date:    21:05:13 09/04/2011
-- Design Name:
-- Module Name:    ch5mem_tb - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ch5mem_tb is
end ch5mem_tb;

architecture Behavioral of ch5mem_tb is

component ch5mem is
    port
    (
        clock                : in std_logic;
        datain                : in std_logic_vector(31 downto 0);
        memaddress            : in std_logic_vector(31 downto 0);
        memwrite              : in std_logic;
        memread               : in std_logic;
        dataout               : out std_logic_vector(31 downto 0);
        enable                : in std_logic;
        startup               : in std_logic -- to load pre-written data
    );
end component;

signal clk                : std_logic;
signal data               : std_logic_vector(31 DOWNTO 0);
signal addr               : std_logic_vector(31 DOWNTO 0);
signal memwrite           : std_logic;
signal memread            : std_logic;
signal q                  : std_logic_vector(31 DOWNTO 0);
signal en                 : std_logic;
signal startup            : std_logic;

constant PERIOD : time := 50 ns;

```

```

begin

mem: ch5mem
port map (
    clock          => clk,
    datain         => data,
    memaddress     => addr,
    memwrite       => memwrite,
    memread        => memread,
    dataout        => q,
    enable         => en,
    startup        => startup);

process
begin
    clk <= '0';
    wait for PERIOD/2;
    clk <= '1';
    wait for PERIOD/2;
end process;

PROCESS
BEGIN

    en      <= '1';

--
--
    startup <= '1';
    wait for PERIOD/10;
    startup <= '0';
    wait for PERIOD/20;
    startup <= '1';
    wait for PERIOD/10;
    startup <= '0';

    -- test read pre-written data --
    memread <= '1';
    memwrite <= '0';

    addr <= x"10000000";
    wait for PERIOD;

    addr <= x"10000004";
    wait for PERIOD;

    -- test write memory --
    memread <= '0';
    wait for PERIOD/4;

    memwrite <= '1';
    addr <= x"10000000";
    data <= x"00000028";
    wait for PERIOD * 3/4;

    -- test read memory after re-written --
    memwrite <= '0';
    wait for PERIOD/4;

    memread <= '1';
    addr <= x"10000000";
    wait for PERIOD * 3/4;

    -- test read pre-written program --
    memread <= '1';
    addr <= x"00400000";
    wait for PERIOD/2;

```

```

addr <= x"00400004";
wait for PERIOD;

addr <= x"00400008";
wait for PERIOD;

addr <= x"0040000C";
wait for PERIOD;

addr <= x"00400010";
wait for PERIOD;

addr <= x"00400014";
wait for PERIOD;

addr <= x"00400018";
wait for PERIOD;

addr <= x"0040001C";
wait for PERIOD;

addr <= x"00400020";
wait for PERIOD;

-- test overwrite program segment --
memread <= '0';

addr <= x"00400000";
data <= x"00000000";
wait for PERIOD/4;

memwrite <= '1';
wait for PERIOD * 3/4;

memwrite <= '0';
wait for PERIOD/4;

memread <= '1';
wait for PERIOD * 3/4;

addr <= x"00400004";
wait for PERIOD/2;

en <= '0';
wait for PERIOD/2;

-- set simulation time to 950ns

```

END PROCESS;

end Behavioral;

--

Components

regfile.vhd

--

```

-----
-- Company:          comp. eng. KKU.
-- Engineer:         TK
--
-- Create Date:     14:46:23 08/31/2011

```



```

-- Module Name:   regfile - Behavioral
-- Description:  register file
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

entity regfile is
port(
  readreg1:          in std_logic_vector (4 downto 0);      -- index referring to a specific
  register          register
  readreg2:          in std_logic_vector (4 downto 0);      -- index referring to a specific
  register          register
  writereg:          in std_logic_vector (4 downto 0);      -- index referring to a specific
  register          register
  writedata:         in std_logic_vector (31 downto 0);     -- data to put in the specified
  register's content
  readdata1:         out std_logic_vector (31 downto 0);    -- data contained in register indexed by
  readreg1
  readdata2:         out std_logic_vector (31 downto 0);    -- data contained in register indexed by
  readreg2
  RegWrite:          in std_logic;
  clock:             in std_logic
);
end regfile;

architecture Behavioral of regfile is
  TYPE registers IS ARRAY(0 TO 2 ** 5 - 1) OF std_logic_vector(31 DOWNT0 0);

  SIGNAL reg_block : registers := (
    0 => x"00000000",
    1 => x"FFFFFFFF",
    2 => x"FFFFFFFF",
    3 => x"FFFFFFFF",
    4 => x"FFFFFFFF",
    5 => x"FFFFFFFF",
    6 => x"FFFFFFFF",
    7 => x"FFFFFFFF",
    8 => x"FFFFFFFF",
    9 => x"FFFFFFFF",
    10 => x"FFFFFFFF",
    11 => x"FFFFFFFF",
    12 => x"FFFFFFFF",
    13 => x"FFFFFFFF",
    14 => x"FFFFFFFF",
    15 => x"FFFFFFFF",
    16 => x"10000000", -- base address for data segment
    17 => x"FFFFFFFF",
    18 => x"FFFFFFFF",
    19 => x"FFFFFFFF",
    20 => x"FFFFFFFF",
    21 => x"FFFFFFFF",
    22 => x"FFFFFFFF",
    23 => x"FFFFFFFF",
    24 => x"FFFFFFFF",
    25 => x"FFFFFFFF",
    26 => x"FFFFFFFF",
    27 => x"FFFFFFFF",

```

```

28 => x"FFFFFFFF",
29 => x"FFFFFFFF",
30 => x"FFFFFFFF",
31 => x"FFFFFFFF");

BEGIN
    PROCESS (clock, readreg1, readreg2)
    BEGIN

        readdata1 <= reg_block(to_integer(unsigned(readreg1)));
        readdata2 <= reg_block(to_integer(unsigned(readreg2)));

        IF (RegWrite = '1') THEN
            reg_block(to_integer(unsigned(writereg))) <= writedata;
        END IF;

    END PROCESS;
END Behavioral;

--

```

WordALU.vhd

```

--
-----
-- Company:
-- Engineer:
--
-- Create Date:    08:54:36 08/22/2011
-- Design Name:
-- Module Name:    WordALU - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity WordALU is
    Port ( a : in  STD_LOGIC_VECTOR (31 downto 0);
          b : in  STD_LOGIC_VECTOR (31 downto 0);
          Binvert : in  STD_LOGIC;
          CarryIn : in  STD_LOGIC;
          Operation : in  STD_LOGIC_VECTOR (1 downto 0);
          Result : out  STD_LOGIC_VECTOR (31 downto 0);
          Overflow : out  STD_LOGIC;
          Zero : out  STD_LOGIC);
end WordALU;

```

```

architecture Behavioral of WordALU is

    COMPONENT BitALU
    Port ( a, b, cin, Binvert, Lessin : in  STD_LOGIC;
          Qo, cout : out  STD_LOGIC;
          operation : in  STD_LOGIC_VECTOR (1 downto 0)
          );
    END COMPONENT;

    component MSBALU
        port (
            a, b, cin, Binvert, Lessin : in  STD_LOGIC;
            Qo, set, overflow : out  STD_LOGIC;
            operation : in  STD_LOGIC_VECTOR (1 downto 0)
        );
    end component;

    signal c: STD_LOGIC_VECTOR (31 downto 0);
    signal set : STD_LOGIC;
    signal qr: STD_LOGIC_VECTOR (31 downto 0);

begin

    c(0) <= CarryIn;

    bit0: BitALU port map(
        a => a(0),
        b => b(0),
        cin => c(0),
        Binvert => Binvert,
        Lessin => set,
        Qo => qr(0),
        cout => c(1),
        operation => Operation
    );

    bits1to30: for i in 1 to 30 generate
        ibit: BitALU port map(
            a => a(i),
            b => b(i),
            cin => c(i),
            Binvert => Binvert,
            Lessin => '0',
            Qo => qr(i),
            cout => c(i+1),
            operation => Operation
        );
    end generate;

    bit31: MSBALU port map (
        a => a(31),
        b => b(31),
        cin => c(31),
        Binvert => Binvert,
        Lessin => '0',
        Qo => qr(31),
        set => set,
        overflow => Overflow,
        operation => Operation
    );

    Result <= qr;

    Zero <= not (
        qr(0)   or qr(1)   or qr(2)   or qr(3)   or

```

```

qr(4) or qr(5) or qr(6) or qr(7) or
qr(8) or qr(9) or qr(10) or qr(11) or
qr(12) or qr(13) or qr(14) or qr(15) or
qr(16) or qr(17) or qr(18) or qr(19) or
qr(20) or qr(21) or qr(22) or qr(23) or
qr(24) or qr(25) or qr(26) or qr(27) or
qr(28) or qr(29) or qr(30) or qr(31) );

```

```
end Behavioral;
```

```
--
```

nbitregister.vhd

```
--
```

```

-----
-- Company:          comp. engr. KKU.
-- Engineer:         TK
--
-- Create Date:      11:53:57 08/29/2011
-- Design Name:
-- Module Name:      nbitregister - Behavioral
-- Description:
--   adapted from http://esd.cs.ucr.edu/labs/tutorial/register.vhd, retrieved on Aug, 29th, 2011.
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments: "Attitude is a little thing that makes a big difference." - Winston Churchill
--
-----

```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity nbitregister is
generic(n: integer := 32);
port(
win:          in std_logic_vector (n-1 downto 0);
clock:        in std_logic;
regload:      in std_logic;
regclear:     in std_logic;
wout:         out std_logic_vector (n-1 downto 0)
);
end nbitregister;
```

```
architecture Behavioral of nbitregister is
```

```
    signal wtmp : std_logic_vector (n-1 downto 0);
```

```
begin
```

```
    process(win, clock, regload, regclear)
    begin
        if regclear = '1' then
            wtmp <= (wtmp'range => '0');
        elsif (clock = '1' and clock'event) then
            if regload = '1' then
                wtmp <= win;
            end if;
        end if;
    end process;
```

```
end process;
```

```
wout <= wtmp;
```

```
end Behavioral;
```

```
--
```

mux4.vhd

```
--
-----
-- Company:          comp. engr. KKU.
-- Engineer:         TK
--
-- Create Date:      11:58:12 09/02/2011
-- Design Name:
-- Module Name:      mux - Behavioral
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
-- "The idea of wilderness needs no defense. It only needs more defenders."
-- - Edward Abbey
--
-----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
--use IEEE.NUMERIC_STD.ALL;

entity mux4 is
port(
    sel:          in std_logic_vector(1 downto 0);
    ch1:          in std_logic_vector(31 downto 0);
    ch2:          in std_logic_vector(31 downto 0);
    ch3:          in std_logic_vector(31 downto 0);
    ch4:          in std_logic_vector(31 downto 0);
    muxout: out std_logic_vector (31 downto 0)
);
end mux4;

architecture Behavioral of mux4 is
begin
    SEL_PROCESS: process (sel,ch1,ch2,ch3,ch4)
    begin
        case sel is
            when "00" => muxout <= ch1;
            when "01" => muxout <= ch2;
            when "10" => muxout <= ch3;
            when "11" => muxout <= ch4;
            when others => muxout <= (muxout'range => 'Z');
        end case;
    end process SEL_PROCESS;
end Behavioral;
--
```

mux2.vhd

```
--
-----
-- Company:          comp. engr. KKU.
-- Engineer:         TK
--
-- Create Date:      15:50:12 09/01/2011
-- Design Name:
-- Module Name:      mux - Behavioral
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
```

```

--
-----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
--use IEEE.NUMERIC_STD.ALL;

entity mux2 is
port(
    sel:          in std_logic;
    ch1:          in std_logic_vector(31 downto 0);
    ch2:          in std_logic_vector(31 downto 0);
    muxout: out std_logic_vector (31 downto 0)
);
end mux2;

architecture Behavioral of mux2 is

begin
    SEL_PROCESS: process (sel,ch1,ch2)
    begin
        case sel is
            when '0' => muxout <= ch1;
            when '1' => muxout <= ch2;
            when others => muxout <= (muxout'range => 'Z');
        end case;
    end process SEL_PROCESS;
end Behavioral;
--

```

signextend.vhd

```

--
-----
-- Company:
-- Engineer:
--
-- Create Date:    00:19:34 09/05/2011
-- Design Name:
-- Module Name:    signextend - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity signextend is
    Port ( halfword : in  STD_LOGIC_VECTOR (15 downto 0);

```

```

        fullword : out STD_LOGIC_VECTOR (31 downto 0));
end signextend;

architecture Behavioral of signextend is

signal upperhalf : STD_LOGIC_VECTOR (15 downto 0);

begin

    fullword <= upperhalf & halfword;
    upperhalf <= (upperhalf'range => halfword(15));

end Behavioral;

```

--

ALUControl.vhd

--

```

-----
-- Company:          comp. eng. KKU.
-- Engineer:         TK
--
-- Create Date:      08:48:11 09/06/2011
-- Design Name:
-- Module Name:      ALUControl - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--

```

```

-----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

```

```

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

```

```
entity ALUControl is
```

```

    port(
        ALUOp           : in std_logic_vector(1 downto 0);
        funct           : in std_logic_vector(5 downto 0); -- IRout(5 downto 0)
        Binvert         : out std_logic;
        Operation       : out std_logic_vector(1 downto 0) );

```

```
end ALUControl;
```

```
architecture Behavioral of ALUControl is
```

```
begin
```

```
    ALUControl: process(ALUOp, funct)
```

```

begin

    case ALUop is
    when "00" =>
        -- lw/sw: add --
        Binvert <= '0';
        Operation <= "10";
    when "01" =>
        -- beq: sub --
        Binvert <= '1';
        Operation <= "10";
    when "10" =>
        -- R-type --
        case funct is
        when "100000" =>
            -- add --
            Binvert <= '0';
            Operation <= "10";

            when "10010" =>
                -- sub --
                Binvert <= '1';
                Operation <= "10";

            when "100100" =>
                -- and --
                Binvert <= '0';
                Operation <= "00";

            when "100101" =>
                -- or --
                Binvert <= '0';
                Operation <= "01";

            when "101010" =>
                -- slt --
                Binvert <= '1';
                Operation <= "11";

            when others => Binvert <= '0'; Operation <= "00";
        end case;
    when others =>
        -- default case --
        Binvert <= '0';
        Operation <= "00";
    end case;

end process;

end Behavioral;

--

```

maincontrol.vhd

```

--
-----
-- Company:          comp. engr. KKU.
-- Engineer:         TK
--
-- Create Date:      07:41:53 09/06/2011
-- Design Name:
-- Module Name:      maincontrol - Behavioral
-- Project Name:

```



```

-- Target Devices:
-- Tool versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--      "Truth will set you free." - James A. Garfield
-----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity maincontrol is

    port(
        PCWriteCond : out  std_logic;
        PCWrite      : out  std_logic;
        PCSrc        : out  std_logic_vector(1 downto 0);
        MemRead      : out  std_logic;
        MemWrite     : out  std_logic;
        IorD         : out  std_logic;
        IRWrite      : out  std_logic;
        ALUOp        : out  std_logic_vector(1 downto 0);
        ALUSrcB      : out  std_logic_vector(1 downto 0);
        ALUSrcA      : out  std_logic;
        RegWrite     : out  std_logic;
        RegDst       : out  std_logic;
        MemtoReg     : out  std_logic;
        stagein      : in   std_logic_vector(2 downto 0);
        opcode       : in   std_logic_vector(5 downto 0); -- IRout(31 downto 26)
        stageout     : out  std_logic_vector(2 downto 0)    );

end maincontrol;

architecture Behavioral of maincontrol is

begin

    MainControl: process(stagein)

    begin

        case stagein is
            when "000" =>
                -- boot up --
                PCWrite <= '1'; PCSrc <= "11";
                MemRead <= '0'; MemWrite <= '0'; IRWrite <= '0'; RegWrite <= '0';

                stageout <= "001";

            when "001" =>
                -- Instruction Fetch --
                PCWriteCond <= '0';    PCWrite <= '1'; IorD <= '0';
                MemRead <= '1';        MemWrite <= '0'; MemtoReg <= '0';
                IRWrite <= '1';        PCSrc <= "00";
        end case;
    end process;
end;

```

```

ALUOp <= "00";          ALUSrcB <= "01";          ALUSrcA <= '0';
RegWrite <= '0';       RegDst <= '0';

    stageout <= "010";
when "010" =>
    -- Instruction Decode & Branch Address Calculation --
    PCWriteCond <= '0';   PCWrite <= '0'; IorD <= '0';
    MemRead <= '0';      MemWrite <= '0'; MemtoReg <= '0';
    IRWrite <= '0';     PCSrc <= "00";
    ALUOp <= "00";       ALUSrcB <= "11";          ALUSrcA <= '0';
    RegWrite <= '0';     RegDst <= '0';

    stageout <= "011";
when "011" =>

    case opcode is
    when "000000" =>
        -- r-type --
        PCWriteCond <= '0';   PCWrite <= '0'; IorD <= '0';
        MemRead <= '0';      MemWrite <= '0'; MemtoReg <= '0';
        IRWrite <= '0';     PCSrc <= "00";
        ALUOp <= "10";       ALUSrcB <= "00";          ALUSrcA <= '1';
        RegWrite <= '0';     RegDst <= '0';

        stageout <= "100";

    when "100011" =>
        -- lw --
        PCWriteCond <= '0';   PCWrite <= '0'; IorD <= '0';
        MemRead <= '0';      MemWrite <= '0'; MemtoReg <= '0';
        IRWrite <= '0';     PCSrc <= "00";
        ALUOp <= "00";       ALUSrcB <= "10";          ALUSrcA <= '1';
        RegWrite <= '0';     RegDst <= '0';

        stageout <= "100";

    when "101011" =>
        -- sw --
        PCWriteCond <= '0';   PCWrite <= '0'; IorD <= '0';
        MemRead <= '0';      MemWrite <= '0'; MemtoReg <= '0';
        IRWrite <= '0';     PCSrc <= "00";
        ALUOp <= "00";       ALUSrcB <= "10";          ALUSrcA <= '1';
        RegWrite <= '0';     RegDst <= '0';

        stageout <= "100";

    when "000100" =>
        -- beq --
        PCWriteCond <= '1';   PCWrite <= '0'; IorD <= '0';
        MemRead <= '0';      MemWrite <= '0'; MemtoReg <= '0';
        IRWrite <= '0';     PCSrc <= "01";
        ALUOp <= "01";       ALUSrcB <= "00";          ALUSrcA <= '1';
        RegWrite <= '0';     RegDst <= '0';

        stageout <= "001";

    when "000010" =>
        -- j --
        PCWriteCond <= '0';   PCWrite <= '1'; IorD <= '0';
        MemRead <= '0';      MemWrite <= '0'; MemtoReg <= '0';
        IRWrite <= '0';     PCSrc <= "10";
        ALUOp <= "00";       ALUSrcB <= "00";          ALUSrcA <= '0';
        RegWrite <= '0';     RegDst <= '0';

        stageout <= "001";

```

```

        when others =>
            -- unknown operation --
            stageout <= "000";
        end case;
    when "100" =>
        case opcode is
            when "000000" =>
                -- r-type --
                PCWriteCond <= '0';      PCWrite <= '0'; IorD <= '0';
                MemRead <= '0';          MemWrite <= '0'; MemtoReg <= '0';
                IRWrite <= '0';          PCSource <= "00";
                ALUOp <= "00";           ALUSrcB <= "00";      ALUSrcA <= '0';
                RegWrite <= '1';        RegDst <= '1';

                stageout <= "001";

            when "100011" =>
                -- lw --
                PCWriteCond <= '0';      PCWrite <= '0'; IorD <= '1';
                MemRead <= '1';          MemWrite <= '0'; MemtoReg <= '0';
                IRWrite <= '0';          PCSource <= "00";
                ALUOp <= "00";           ALUSrcB <= "00";      ALUSrcA <= '0';
                RegWrite <= '0';        RegDst <= '0';

                stageout <= "101";

            when "101011" =>
                -- sw --
                PCWriteCond <= '0';      PCWrite <= '0'; IorD <= '1';
                MemRead <= '0';          MemWrite <= '1'; MemtoReg <= '0';
                IRWrite <= '0';          PCSource <= "00";
                ALUOp <= "00";           ALUSrcB <= "00";      ALUSrcA <= '0';
                RegWrite <= '0';        RegDst <= '0';

                stageout <= "001";

            when others =>
                -- unknown operation --
                stageout <= "000";
            end case;
        when "101" =>

            if opcode = "100011" then
                -- lw --
                PCWriteCond <= '0';      PCWrite <= '0'; IorD <= '0';
                MemRead <= '0';          MemWrite <= '0'; MemtoReg <= '1';
                IRWrite <= '0';          PCSource <= "00";
                ALUOp <= "00";           ALUSrcB <= "00";      ALUSrcA <= '0';
                RegWrite <= '1';        RegDst <= '0';

            end if;

            stageout <= "001";
        when others =>
            -- default --
            stageout <= "000";
        end case;

    end process;

end Behavioral;
--

```

ch5mem.vhd

```

--
-----
-- Company:
-- Engineer:
--
-- Create Date:    19:18:21 09/04/2011
-- Design Name:
-- Module Name:   ch5mem - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:   to provide interface of 32-bit address/data
--
--                                     It allows only addresses:
--                                     1000 0000 to 1000 00FF for the data segment
--                                     and 0040 0000 to 0040 00FF for the program segment (full range:
0040 0000-0FFF FFFF)
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
--use IEEE.STD_LOGIC_ARITH.ALL;

entity ch5mem is
    port
    (
        clock                : in std_logic;
        datain                : in std_logic_vector(31 downto 0);
        memaddress            : in std_logic_vector(31 downto 0);
        memwrite              : in std_logic;
        memread               : in std_logic;
        dataout               : out std_logic_vector(31 downto 0);
        enable                : in std_logic;
        startup               : in std_logic -- to load pre-written data
    );
end ch5mem;

architecture Behavioral of ch5mem is
    type RAMROM is array(0 TO 2 ** 8 - 1) of std_logic_vector(31 downto 0);
    signal data_block : RAMROM;
    signal program_block: RAMROM;

begin

    process(enable, clock, memread, memwrite, memaddress, startup)

        variable index: integer range 0 to 7;
        begin

            if startup = '1' then
                -- initialize the ROM contents
                program_block(0) <= x"8e080000"; -- [00400000]          lw $t0,
0($s0)
                program_block(1) <= x"8e090004"; -- [00400004]          lw $t1,
4($s0)
                program_block(2) <= x"0109502a"; -- [00400008]          slt $t2,
$t0, $t1
                program_block(3) <= x"11400003"; -- [0040000C]          beq $t2,
$zero, LAB_t1ELTt0
            end if;
        end process;
    end architecture;

```

```

                                program_block(4) <= x"01285822"; -- [00400010]                                sub $t3,
$t1, $t0
                                program_block(5) <= x"08100007"; -- [00400014]                                j
LAB_SAVE
                                program_block(6) <= x"01095822"; -- [00400018] LAB_t1ELTt0:    sub $t3, $t0, $t1
                                program_block(7) <= x"ae0b0008"; -- [0040001C] LAB_SAVE:      sw $t3, 8($s0)
                                program_block(8) <= x"8e080008"; -- [00400020]                                lw $t0,
8($s0) # to check if it is well-saved in memory

                                -- initialize the data content
                                -- This may not sound practical, but since we don't have any instruction dealing with a
constant yet.
                                -- So, it is for simplicity sake of homework.
                                data_block(0) <= x"00000019";                                -- [10000000]
                                data_block(1) <= x"00000037";                                -- [10000004]

-- [10000008]

-- after run, it should has a value, abs( data_block(0) - data_block(1) ) = x"0000001E"

                                end if;

                                -- 0x10000xXX [0001 0000 0000 0000 0000 00xx xxxx xx--]=> data segment;
                                -- 0x00400xXX [0000 0000 0100 0000 0000 00xx xxxx xx--]=> program segment

                                index := to_integer(unsigned( memaddress(9 downto 2) ));

                                if (enable = '1' and memread = '1') then

                                    if memaddress(31 downto 10) = "00010000000000000000" then
                                        dataout <= data_block(index);
                                    elsif memaddress(31 downto 10) = "00000000010000000000" then
                                        dataout <= program_block(index);
                                    else
                                        dataout <= (dataout'range => 'Z');
                                    end if;

                                elsif (enable = '1' and memwrite = '1' and clock'event and clock = '0') then

                                    if memaddress(31 downto 10) = "00010000000000000000" then
                                        data_block(index) <= datain;
                                    elsif memaddress(31 downto 10) = "00000000010000000000" then
                                        program_block(index) <= datain;
                                    end if;

                                    dataout <= (dataout'range => 'Z');

                                else
                                    dataout <= (dataout'range => 'Z');
                                end if;

                                end process;

end Behavioral;
--

```